

332:221 Principles of Electrical Engineering I – Fall 2003

Hourly Exam 2 – November 13, 2003

NAME OF THE STUDENT:

Last four digits of Student ID #:

Solution

Section # 1 (TTh4) or # 2 (W3,F4)

Circle one

Please make sure that there are 6 pages in this booklet excluding this cover page.

This is a closed-book closed-notes exam. Do all your work on these sheets. If more space is required, ask the instructor.

Problem #	Pages	Maximum Points	Points earned	Description
1	1 & 2	30		<i>Chapter 4, Thevenin equivalent Circuit</i>
2	3	20		<i>Chapter 5, Ideal Op – Amp Circuit</i>
3	4	22		<i>Chapter 5, Non – Ideal Op – Amp Circuit</i>
4	5	14		<i>Chapter 6, Behavior of L</i>
5	6	14		<i>Class Notes: Op–Amps, Integrators & Differentiators</i>

Total points earned by the student =


Note: Most of the problems, if not all, are directly taken from Home-work problems with perhaps numbers changed and slightly modified. My goal in doing so is to encourage you to do Home-work problems. If you simply read the solutions of Home-work problems without doing them, it would not help you.

Curriculum revision: Both the curricula of Electrical option and Computer option have been revised for class year 2006 and onwards. The details are on the ECE website .

Problem 1: This is HW problem 4.74 re-phrased.

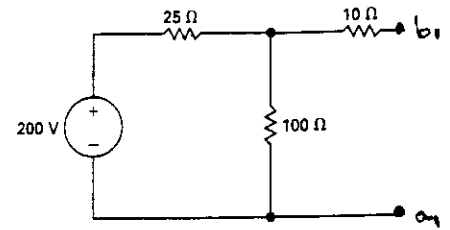Problem 1a: Construct the Thevenin equivalent circuit with respect to the terminals a_1 and b_1 .


Let the Thevenin voltage be denoted by V_{Th-1} and Thevenin resistance by R_{Th-1} .



When there is no load at the terminals a_1 and b_1 , there is no current in 10Ω . Thus open circuit voltage at the terminals a_1 and b_1 is given by (Voltage division rule),



$$V_{OC} = V_{Th-1} = 200 \frac{100}{100+25} = 160V$$

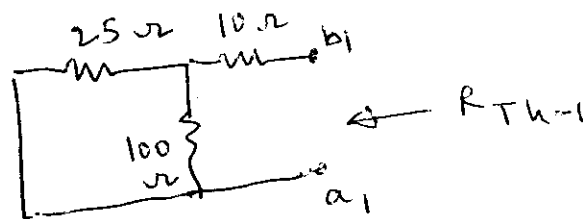Thevenin resistance is the resistance at terminals a_1 and b_1 when all the independent sources are set to zero.




$$R_{Th-1} = 10 + \frac{(100)(25)}{100+25} = 10 + 20 = 30\Omega$$

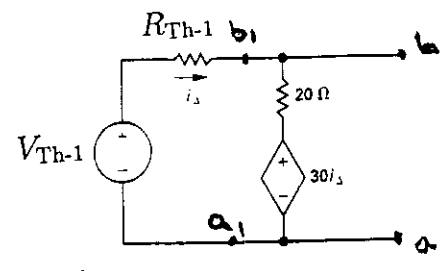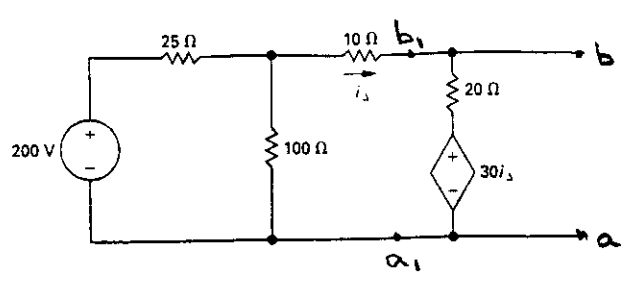Problem 1b: We are given the circuit drawn on the left side. However, utilizing the results of Problem 1a, we can equivalently redraw it as the one shown on the right side. Construct the Thevenin equivalent circuit with respect to the terminals *a* and *b*.



Determination of open circuit voltage

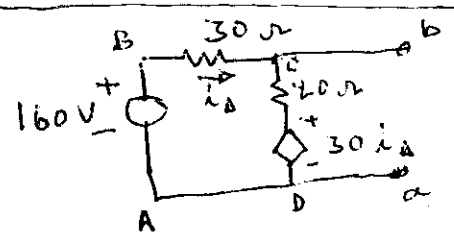

By writing the KCL for the loop ABCDA, we get


$$160 = 30i_A + 20i_A + 30i_A$$

$$\therefore i_A = 2A$$

V_{Th} is the voltage across *c* and *d* (same as *b* and *a*)

$$= 20i_A + 30i_A = 50i_A = 100V$$

Determination of short circuit current

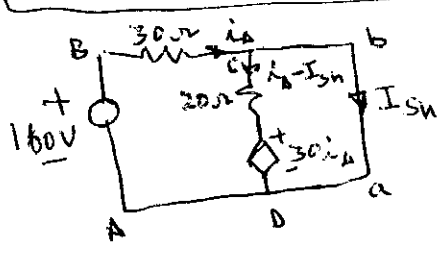

By mesh analysis,


$$160 = 30i_A \quad (\text{loop } ABCb a DA)$$

$$30i_A + 20(i_A - I_{sh}) = 0 \quad (\text{loop } DCb a D)$$

$$\therefore i_A = \frac{160}{30}, \quad I_{sh} = \frac{50i_A}{20} = \frac{50}{20} \frac{160}{30} = \frac{40}{3} A$$

Thevenin resistance = $\frac{V_{oc}}{I_{sh}} = \frac{100 \times 3}{40} = 7.5 \Omega$

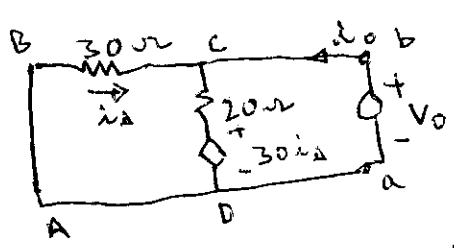Determination of Thevenin resistance by looking for the resistance at terminals *a* and *b* when all the independent sources are set to zero!



Let $i_0 = 1A$.

$$V_0 = -30i_A \quad (\text{loop } ABCb a DA)$$

$$\therefore i_A = -\frac{V_0}{30}$$


$$V_0 = 20(1+i_A) + 30i_A \quad (\text{loop } DCb a D)$$

$$= 50\left(\frac{-V_0}{30}\right) + 20$$

$$\therefore V_0 = \frac{(20)(30)}{80} = 7.5V$$

Thevenin resistance = $\frac{V_0}{i_0} = \frac{V_0}{1} = 7.5 \Omega$

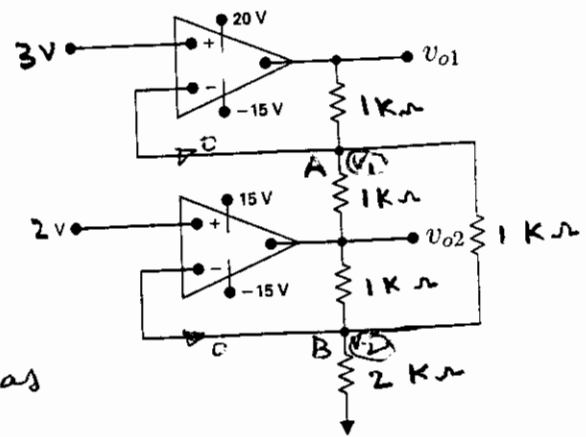Problem 2: This is HW problem 5.33 re-phrased. Assuming that the Op-Amps are ideal, determine v_{o1} and v_{o2} .



As usual we take the ground as the reference node.

$V_1 =$ Voltage at A = 3V (Input terminals of TOP OP-Amp are virtual short).

$V_2 =$ Voltage at B = 2V (Input terminals of lower OP-Amp are virtual short).

Node equation at A: $\frac{3 - v_{o1}}{1K} + \frac{3 - v_{o2}}{1K} + \frac{3 - 2}{1K} = 0$

$$\therefore 7 - v_{o1} - v_{o2} = 0$$

Node equation at B: $\frac{2 - 0}{2K} + \frac{2 - v_{o2}}{1K} + \frac{2 - 3}{1K} = 0$

$$\therefore v_{o2} = 2V$$


$$7 - v_{o1} - 2 = 0$$

$$\therefore v_{o1} = 5V$$

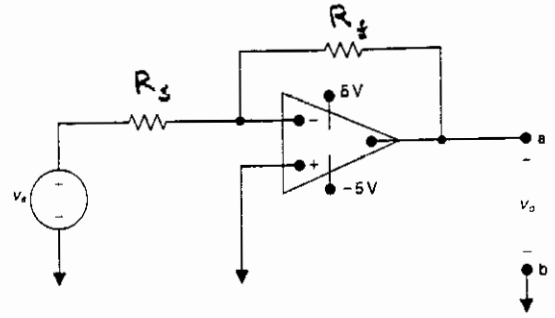Problem 3: This is HW problem 5.43 re-phrased. The Op-Amp in the given circuit is non-ideal with its input resistance $R_{in} = 500\text{ K}\Omega$, its output resistance $R_o = 0.5\text{ K}\Omega$, and its gain $A = 10^5$. Also, let $R_s = 50\text{ K}\Omega$, and $R_f = 50\text{ K}\Omega$. Determine the output resistance R_{out} of the circuit. An answer of $R_{out} = 0$ is not acceptable. At least one significant bit of non-zero value of R_{out} should be indicated.


Be careful with your algebra.

A term can be neglected only if it is small compared to another term which is added or subtracted from it.



By using a model for OP-Amp, the output resistance

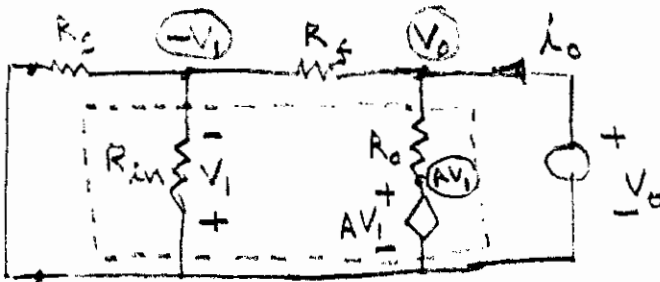R_{out} is given by the ratio $\frac{V_o}{i_o}$ in the following circuit:



We will use the nodal analysis. Nodes are marked as shown.

$$\frac{-V_1}{50\text{K}} - \frac{V_1}{500\text{K}} - \frac{V_1 + V_o}{50\text{K}} = 0$$

$$-2.1V_1 - V_o = 0 \quad \therefore V_1 = -\frac{1}{2.1}V_o$$

$$\frac{V_o + V_1}{50\text{K}} + \frac{V_o - 10^5 V_1}{0.5\text{K}} = i_o \quad \text{Substituting for } V_1 = -\frac{1}{2.1}V_o$$

$$V_o \left[\frac{1}{50\text{K}} + \frac{1}{0.5\text{K}} - \frac{1}{(2.1)50\text{K}} + \frac{10^5}{(2.1)(0.5)\text{K}} \right] = i_o$$

$$V_o \left[(0.2)10^{-4} + 2(10^{-3}) - (0.476)10^{-4} + (0.952)10^2 \right] = i_o$$

Negligible in comparison with $(0.952)10^2$.

$$\therefore R_{out} = \frac{V_o}{i_o} \approx \frac{1}{(0.952)10^2} \approx (1.05)10^{-2} \approx 0.0105 \Omega$$

Problem 4: This is HW problem 6.10 re-phrased.


Consider the circuit on the right in which

$v = 250 \sin(1000t)$ V, $L = 50$ mH, and $i(0) = -5$ A.

Find an expression for the inductor current $i(t)$.

Also, sketch v , i , power consumed p , and energy stored w

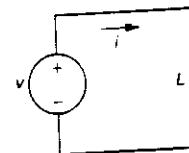in the inductance L with respect to time t . Label the axes appropriately and show at least one cycle of each variable on your sketch.



$$i = \frac{1000}{50} \int_0^t 250 \sin 1000x \, dx - 5$$

$$= 5000 \int_0^t \sin 1000x \, dx - 5$$

$$= 5000 \left[\frac{-\cos 1000x}{1000} \right]_0^t - 5$$

$$= 5(1 - \cos 1000t) - 5$$

$$i = -5 \cos 1000t \text{ A}$$

$$p = vi = (250 \sin 1000t)(-5 \cos 1000t)$$

$$= -1250 \sin 1000t \cos 1000t$$





$$p = -625 \sin 2000t \text{ W}$$

$$w = \frac{1}{2} Li^2$$

$$= \frac{1}{2} (50 \times 10^{-3}) 25 \cos^2 1000t$$

$$= 625 \cos^2 1000t \text{ mJ}$$

$$w = [312.5 + 312.5 \cos 2000t] \text{ mJ.}$$

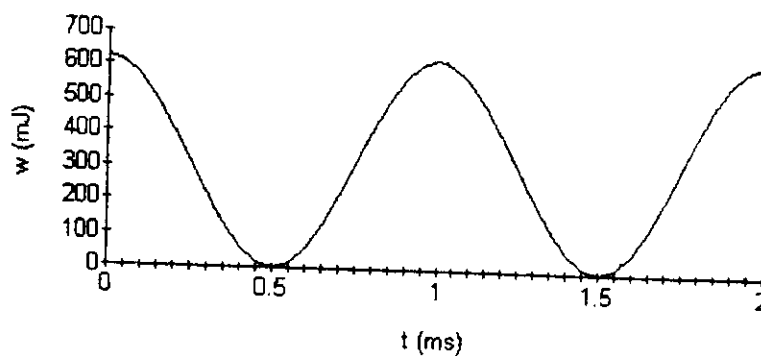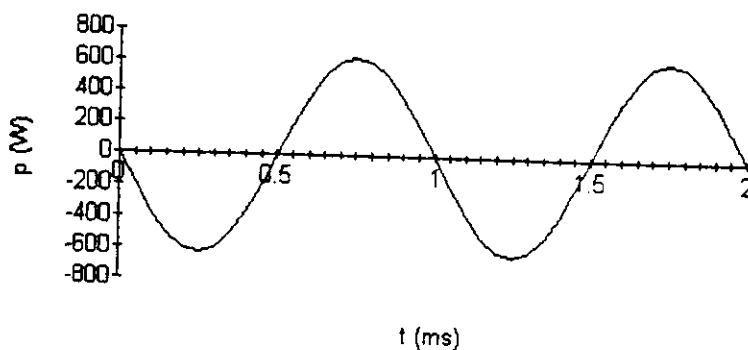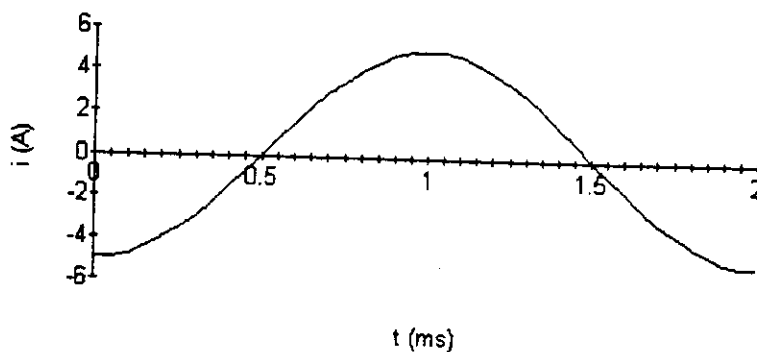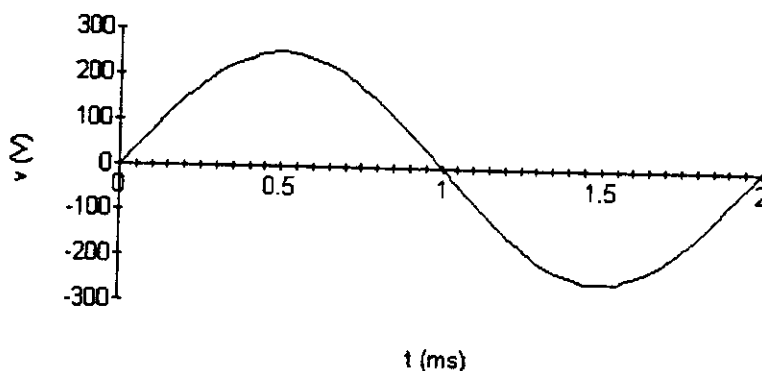


Problem 5: Consider the circuits shown. Explain how and when each circuit acts as a differentiator or an integrator. If proper explanation is lacking, no credit will be given.

The circuit is approximately an integration if $RC \gg 1$.

$$i = C \frac{dV_0}{dt}$$
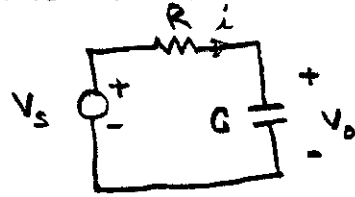
$$V_s = Ri + V_0 = RC \frac{dV_0}{dt} + V_0$$



If RC is large, then

$$V_s \approx RC \frac{dV_0}{dt} \quad \therefore \frac{dV_0}{dt} = \frac{1}{RC} V_s$$

$$V_0(t) = V_0(0) + \frac{1}{RC} \int_0^t V_s(t) dt$$


Assume an ideal OP-Amp.

Node equation at the negative input terminal:

$$-\frac{V_s}{R} - C \frac{dV_0}{dt} = 0$$

$$\therefore \frac{dV_0}{dt} = -\frac{1}{RC} V_s \quad \text{Hence } V_0(t) = V_0(t) - \frac{1}{RC} \int_0^t V_s(t) dt$$

It is an integrator circuit.

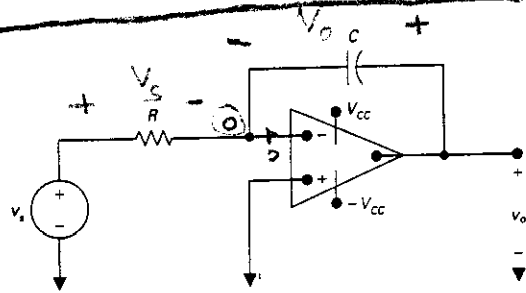

Assume an ideal OP-Amp

Node equation at the negative input terminal:

$$-C \frac{dV_s}{dt} - \frac{V_0}{R} = 0$$

$$\therefore V_0 = -RC \frac{dV_s}{dt}$$

It is a differentiator circuit.

