

Abstract

In 1955, two engineers at the Radio Corporation of America built the first electronic sound synthesizer. It was a primitive design, relying on punch-card input and delivering only a small range of sounds. Since then, many improvements to the design have been made. In this project, we have built an analog synthesizer. Our model takes advantage of a modular design, with each module realized as a circuit that affects the signal in a unique, customizable way. Our synthesizer delivers a wide-range of sounds due to user's ability to control attack, delay, sustain, pitch, echo, and wave shape.

Motivations and Objectives

Motivations

- A modular design allows the user to configure the synthesizer in many different ways, therefore achieving a unique sound which allows us to distinguish ourselves as musicians.
- Building the synthesizer will provide us an in-depth understanding of how circuits of a synthesizer work.

Objectives

- Build a synthesizer that creates sound through a network or free-floating, interchangeable modules.

Challenges

Debugging

- The modules consist of highly-complex circuits, thus increasing the capacity to make errors in construction.

Keyboard

- The keyboard required a changing resistance value to produce different notes. This was a mechanical design challenge.

Acknowledgement

We would like to thank... Ray Wilson of Music From Outer Space for his design work and Professor Bajwa for keeping us responsible


Methodology

Voltage Controlled Amplifier

- Controls ring modulation, vibrato, and stereo panning

Keyboard Sample and Hold

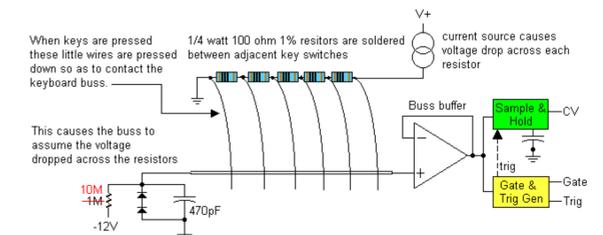- Sends voltages to the Voltage Controlled Oscillator to determine pitch.




Echo Module

- Creates an echo effect. The user can define the delay time, number of repetitions, and echo frequency.

Noise Generator

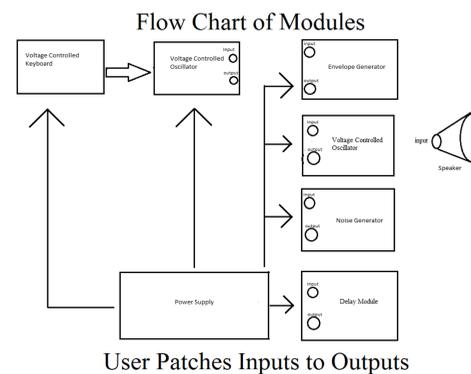- Adds noise to the signal to create a distorted sound.




Voltage Controlled Oscillator

- Creates waveform of desired frequency

Envelope Generator

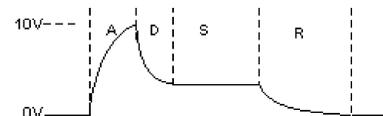
- Controls attack, sustain, delay, and release



Results

See our demonstration for a stronger visualization of results.


Ramp wave output

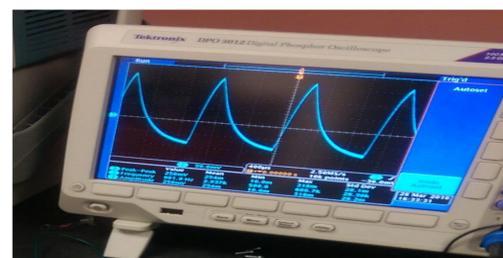

Keyboard Controller Resistance Chain



Voltage Controlled Oscillator Circuit

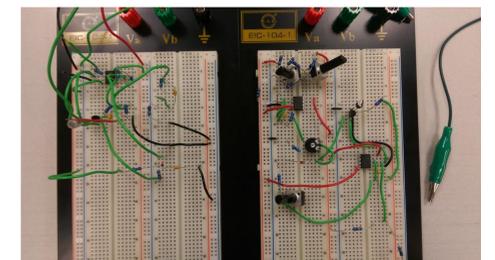

Future Work

- Add and take away modules as we see fit.
- Make casings more aesthetically pleasing

References

- <http://musicfromouterspace.com/>
- <http://www.edparadis.com/keyboard/>
- Make: Analog Synthesizer by Ray Wilson