

Rutgers University
School of Engineering

Fall 2022

332:231 – Digital Logic Design

Sophocles J. Orfanidis
ECE Department
orfanidi@rutgers.edu

Unit 1 – Introduction to DLD

How to Succeed in DLD

**“I hear and I forget,
I see and I remember,
I do and I understand”**

Confucius

“The purpose of computing is insight, not numbers”

Richard Hamming

The keys to success in DLD are the above two quotes from Confucius and Hamming, that is, practice by **doing** a lot of problems on your own, including their computer implementations, **without looking at solutions**.

Passive reading of the textbook (or lecture notes) usually conveys a false sense of understanding and does not result in a good grasp of the material.

DLD Course & Lab Organization

see **course syllabus** on Canvas Files for details on:

course topics (additional web resources on Canvas)

textbook options (additional references on Canvas)

course prerequisites – DLD lab is a **corequisite**

recitations (beginning in the week of **September 12, 2022**)

course requirements

exam dates (exams are administered **online** through **Canvas Quizzes**)

course grading (exam weights & letter-grade thresholds)

homework assignments (assigned but not graded)

instructor & TA contact information

academic integrity office

office of disability services

see **DLD lab syllabus** on Canvas Files for details on **login info** and:


Emona FPGA board (manual & training videos on Canvas Files)

lab sections (labs begin in the week of **September 12, 2022**)

lab procedures (**lab reports, declaration of authorship, screenshots**)

Emona netCIRCUITlabs FPGA board (residing in ECE-207)

 netCIRCUITlabs CONTROL UNIT with MULTIPLE PLUG-IN BOARDS




- ▶ The netCIRCUITlabs Control Unit, located in your lab or office, and will accept any netCIRCUITlabs Lab Experiment board.
- ▶ Fast and easy implementation. No software to install and no setting up required.
- ▶ Secure access for professor to all ADMIN functions including student records and tracking.

The experiments boards plugs into the *netCIRCUITlabs* Control Unit

DLD Lab

 REL 3.0 DIGITAL LOGIC board - student wired experiments



All the logic functions and connections are implemented in an FPGA.

REL3.0 FUNCTIONALITY & EXPERIMENT CAPABILITIES

SIGNAL SOURCES:

- HI/LO Logic Switches x 8
- 8 bit Binary Counter
- 4 bit Gray Counter
- 4 bit Johnson Counter

OVER 60 GATES & FLIP-FLOPS:

- 2, 3 & 4-input OR gates
- X-OR gates
- 2, 3 & 4-input AND gates
- Inverters
- S/R, D & J/K Flip-Flops,
- Inverters
- Finite State Machines

STUDY:

- Boolean logic and algebra
- Combinatorial circuits
- Truth tables
- Karnaugh Maps
- Quine-McCluskey method
- Designing Synch & Asynch sequential circuits
- Flip flops
- State diagrams
- Design of FSM
- Registers, Counters, Multiplexers, Encoders etc
- Introduction to HDL (Verilog)

student login: <http://ece-emonal.engr.rutgers.edu/>

Course Topics

units




1. Introduction to DLD, Verilog HDL, MATLAB/Simulink
2. Number systems
3. Analysis and synthesis of combinational circuits
4. Decoders/encoders, multiplexers/demultiplexers
5. Arithmetic systems, comparators, adders, multipliers
6. Sequential circuits, latches, flip-flops
7. Registers, shift registers, counters, LFSRs
8. Finite state machines, analysis and synthesis

Text: J. F. Wakerly, *Digital Design Principles and Practices*, 5/e, Pearson, 2018
additional references on Canvas Files > References

Digital Design: Principles and Practices

Fifth Edition With Verilog

 

see syllabus for ordering options

4th edition OK, but the material has been rearranged in the 5th edition, and you would need to figure out the correct mapping of the sections and problems between the two editions

References

main text:

J. F. Wakerly, *Digital Design Principles and Practices*, 5/e, Pearson, 2018.

supplementary texts:

S. Brown and Z. Vranesic, *Fundamentals of Digital Logic with Verilog Design*, 3/e, McGraw-Hill, 2014.

D. M. Harris and S. L. Harris, *Digital Design and Computer Architecture*, 2/e, Elsevier, 2013.

M. Mano, C. R. Kime, and T. Martin, *Logic and Computer Design Fundamentals*, 5/e, Pearson, 2016.

E. O. Hwang, *Digital Logic and Microprocessor Design with Interfacing*, 2/e, Cengage, 2018.

Additional References

A. F. Kana, *Digital Logic Design*, [on Canvas].

B. J. Mealy & J. T. Mealy, *Digital McLogic Design*, 2012 [on Canvas].

E. Peasley, *An Introduction to Using Simulink*, 2018 [on Canvas].

H. Moore, *Ch.16 – Simulink – A Brief Introduction*, from *MATLAB for Engineers*, 3/e, Pearson, 2011.

S. A. Edwards, *Verilog Language*, 2001 [on Canvas].

B. Izadi, *Verilog Tutorial*, 2016 [on Canvas].


C. Maxfield, *Bebop to the Boolean Boogie*, 2/e, Newnes, 2009.

Minecraft-Logic-Gates.pdf [on Canvas], see also, [Redstone Logic Gates](#)

Unit-1 Contents: (current reading: Wakerly Chapter 1)


1. Functional and truth-table representations of logic circuits
2. Basic logic gates, AND, OR, NOT, NAND, NOR
3. Analysis & synthesis of combinational circuits – design example
4. Integrated circuits: SSI, MSI, VLSI, CPLD, FPGA, 74x family
5. CMOS realizations of logic gates
6. Design levels:
 - (a) functional definition level
 - (b) transistor level
 - (c) truth-table level, FPGA look-up tables
 - (d) logic-gate level
 - (e) Verilog HDL, structural or behavioral models
 - (f) MATLAB and Simulink implementations
7. Design example – multiplexer function
8. Using Simulink for logic circuits
9. Moore's law

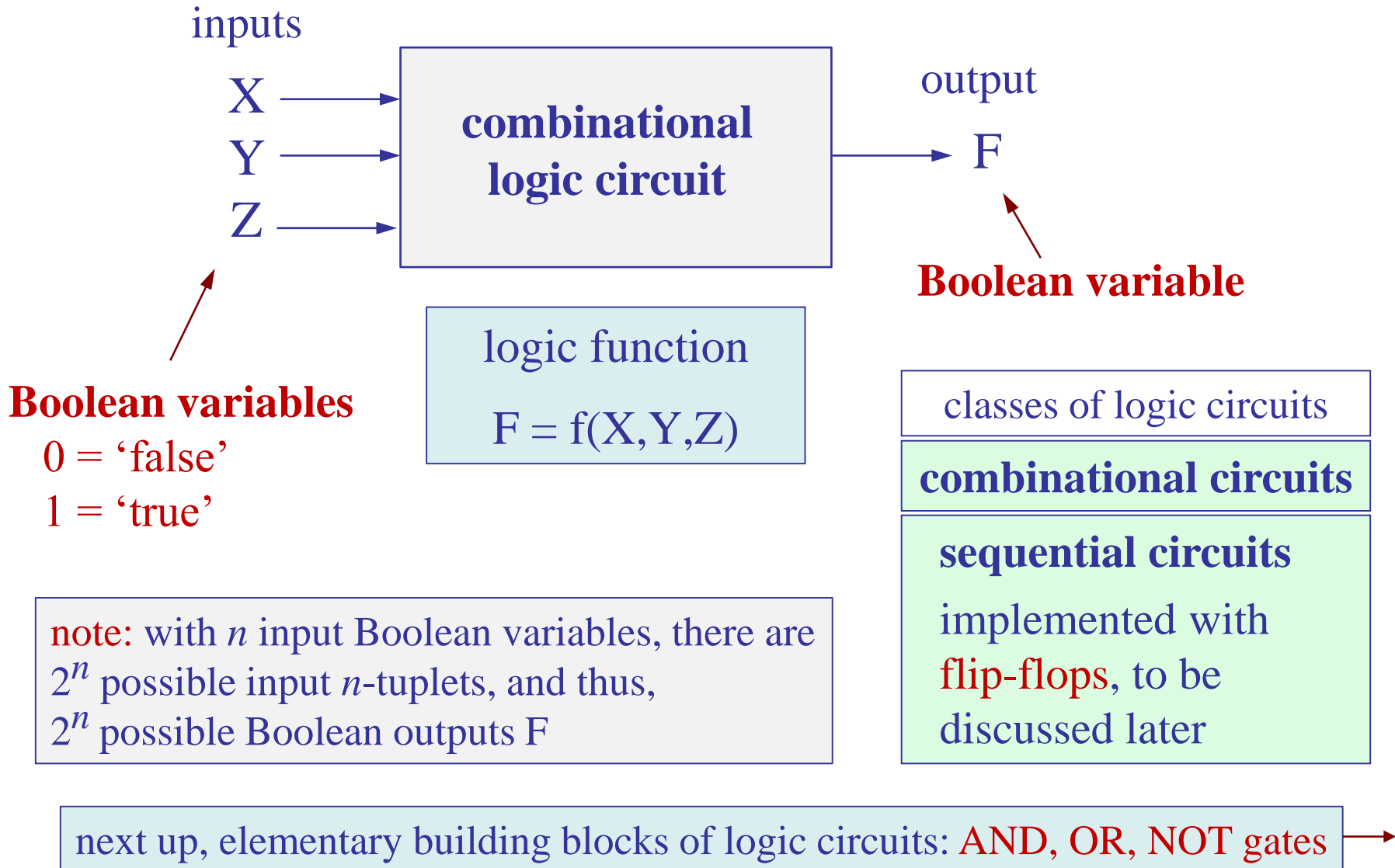Example - representation of a 3-input / 1-output logic circuit




Basic Logic Gates: AND, OR, NOT elementary building blocks of logic circuits

standardized
IEEE symbols

 


X	Y	X AND Y
0	0	0
0	1	0
1	0	0
1	1	1

Boolean variables 0 = 'false'
1 = 'true'

 

X	Y	X OR Y
0	0	0
0	1	1
1	0	1
1	1	1

 

X	NOT X
0	1
1	0

AND, OR, NOT operations in MATLAB and Verilog notation:


& | ~ e.g., X & Y, X | Y, ~X
 (X and Y) (X or Y) (not X)

Logic gates with all possible input values and outputs

(a) AND

(b) OR

(c) NOT or Inverter

 

Inverting gates
(a) NAND
(b) NOR
are discussed next

Inverting Gates

(a) NAND (b) NOR

bubble transformations

$$X' + Y' = (X \cdot Y)'$$



NAND equivalent

equivalent forms based on De Morgan's theorem – see **unit-3**


$$X' \cdot Y' = (X + Y)'$$



NOR equivalent



X	Y	X NAND Y
0	0	1
0	1	1
1	0	1
1	1	0

 

X	Y	X NOR Y
0	0	1
0	1	0
1	0	0
1	1	0

Truth table, analysis & synthesis
combinational circuit example
Wakerly - Table 1.2

Objectives:

- (a) start with a truth-table specification
- (b) construct the logic function $F=f(X,Y,Z)$
- (c) construct gate-level realizations
- (d) implement them with MATLAB
- (e) realize them in Simulink, and on
- (f) the Emona FPGA board

these steps are reversible – one could start with any of them and derive the rest

	X	Y	Z	F
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	0
5	1	0	1	0
6	1	1	0	1
7	1	1	1	1

logic function
 $F = f(X,Y,Z)$

with 3 input variables, there are $2^3=8$
possible input triplets, and 2^3 outputs F

Example - constructing a logic function from a truth table (Table 1.2)

logic function
 $F = f(X, Y, Z)$

X	Y	Z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

→ $X' . Y' . Z$

main technique:
focus on the 1's at the output

→ $X . Y . Z'$

→ $X . Y . Z$ → $X . Y$

there are at least 7 other mathematically **equivalent** formulas for realizing this logic function (see p.24)

→ $F = (X . Y) + (X' . Y' . Z)$

Example - constructing a logic function from a truth table (Table 1.2)

logic function
 $F = f(X, Y, Z)$

X	Y	Z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$X' . Y' . Z$	$X . Y . Z'$	$X . Y . Z$	$X . Y$
0	0	0	0
1	0	0	0
0	0	0	0
0	0	0	0
0	0	0	0
0	0	0	0
0	1	0	1
0	0	1	1

$$F = (X.Y) + (X' . Y' . Z)$$

note: $X.Y.Z + X.Y.Z' = X.Y$
 $Z + Z' = 1$
 $A.Z + A.Z' = A$

Truth table, analysis & synthesis
combinational circuit example
Wakerly - Table 1.2

Objectives:

- (a) start with a truth-table specification
- (b) construct the logic function $F=f(X,Y,Z)$
- (c) construct gate-level realizations
- (d) implement them with MATLAB
- (e) realize them in Simulink, and on
- (f) the Emona FPGA board

these steps are reversible – one could start with any of them and derive the rest

	X	Y	Z	F
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	0
5	1	0	1	0
6	1	1	0	1
7	1	1	1	1

logic function
 $F = f(X,Y,Z)$

with 3 input variables, there are $2^3=8$
possible input triplets, and 2^3 outputs F

Example - constructing a logic function from a truth table (Table 1.2)

logic function
 $F = f(X, Y, Z)$

X	Y	Z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$F = (X.Y) + (X'.Y'.Z)$$

simplified form
 harder to guess

full form
 easy to guess

→ $X'.Y'.Z$


→ $X.Y.Z'$

→ $X.Y.Z$ → $X.Y$

$$F = (X'.Y'.Z) + (X.Y.Z') + (X.Y.Z)$$

Gate-level realization
of the logic circuit of Table 1.2
(Wakerly / Fig.1-5)

 
$$F = (X \cdot Y) + (X' \cdot Y' \cdot Z)$$




two-level, AND-OR, realization

Timing Diagrams

 ideal timing diagram
with X,Y,Z derived
from 3-bit binary counter



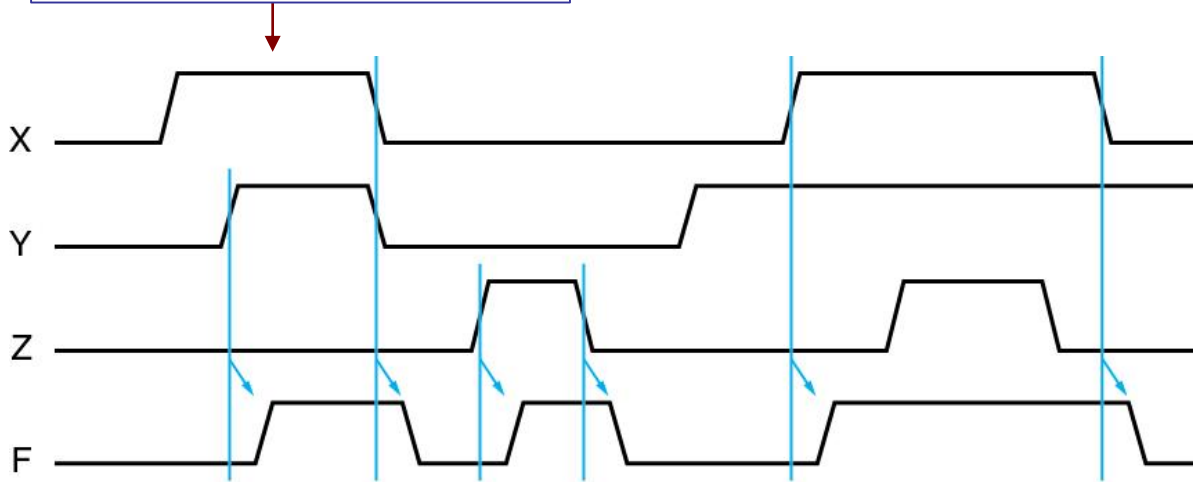realistic timing diagram
with arbitrary X,Y,Z
and small output delays



X	Y	Z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Wakerly / Fig.1-6


TIME →

Alternative, gate-level realization of the logic circuit of Table 1.5 using NAND gates

$$F = XY + X'Y'Z$$
$$F = ((XY)' (X'Y'Z)')'$$

De Morgan's theorem

bubble-to-bubble transformations

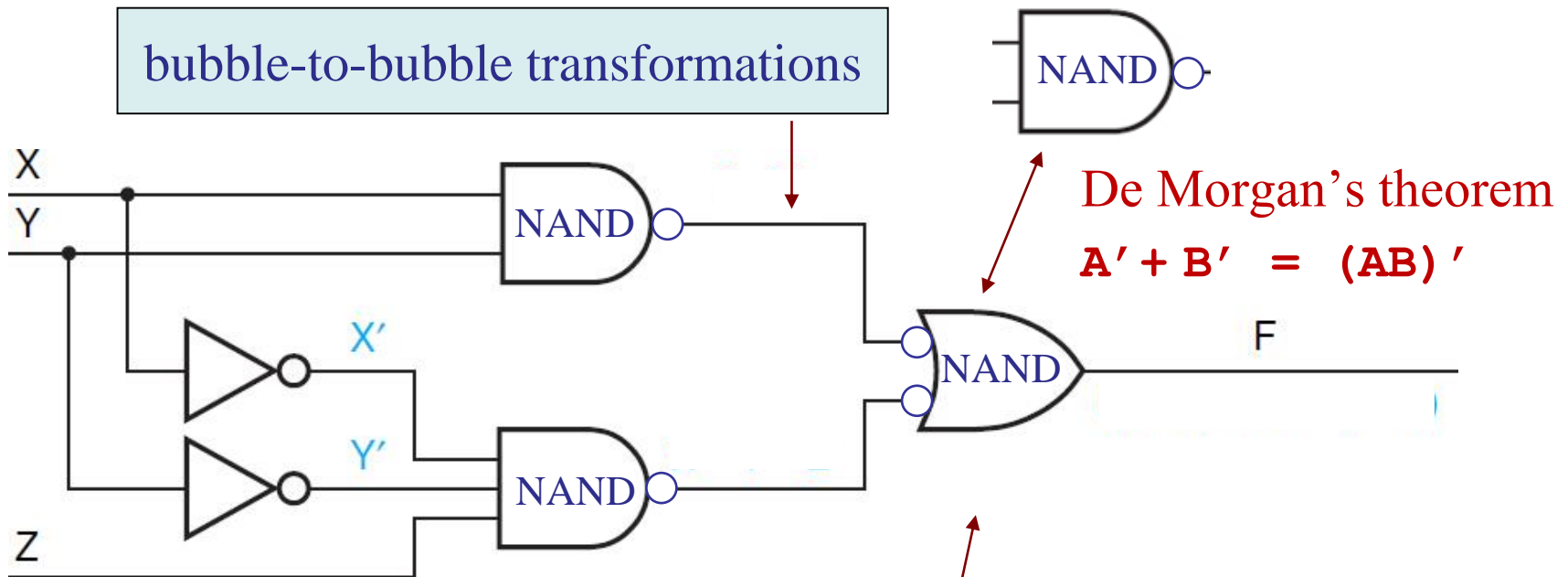


two-level, NAND-NAND, realization

Alternative, gate-level realization of the logic circuit of Table 1.5 using NAND gates

$$F = XY + X'Y'Z$$
$$F = ((XY)' (X'Y'Z)')'$$

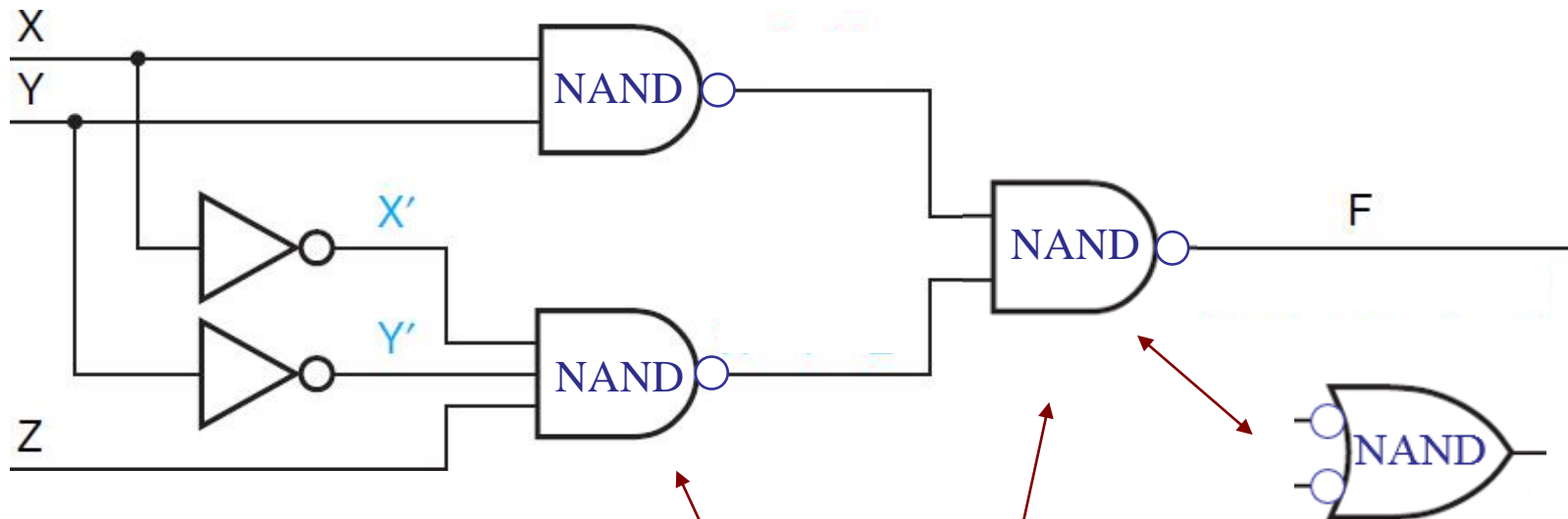equivalent expressions
from De Morgan's theorem
 $A + B = (A'B')'$



two-level, NAND-NAND, realization

other equivalent expressions
to be justified later in unit-3 and Ch.3

$$\begin{aligned}
 F &= XY + X'Y'Z && = \text{AND-OR} \\
 & && \updownarrow \text{De Morgan} \\
 &= ((XY)' (X'Y'Z)')' && = \text{NAND-NAND} \\
 &= (X+Y')(X'+Y)(Y+Z) && = \text{OR-AND} \\
 &= (X+Y')(X'+Y)(X+Z) && = \text{OR-AND} \\
 & && \updownarrow \text{De Morgan} \\
 &= ((X+Y')' + (X'+Y)' + (Y+Z)')' && = \text{NOR-NOR} \\
 &= ((X+Y')' + (X'+Y)' + (X+Z)')' && = \text{NOR-NOR} \\
 &= X'Y'Z + XYZ' + XYZ \\
 &= \text{canonical minterm sum-of-products (SOP) form} \\
 &= (X+Y+Z)(X+Y'+Z)(X+Y'+Z')(X'+Y+Z)(X'+Y+Z') \\
 &= \text{canonical maxterm product-of-sums (POS) form}
 \end{aligned}$$

MATLAB implementation - truth-table computation and timing diagram

```
n = (0:7)'; % input integers
```

```
[X,Y,Z] = a2d(n,3);
```

```
F = (X & Y) | (~X & ~Y & Z);
```

$$F = XY + X'Y'Z$$


&, |, ~ are vectorized in MATLAB

```
[n, X,Y,Z,F]
```

0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	0
5	1	0	1	0
6	1	1	0	1
7	1	1	1	1

```
% a2d in Canvas
```

```
% M-files folder
```

 

```
[X,Y,Z] = a2d(0:7,3);
```

plotting the timing diagram

```
F = (X & Y) | (~X & ~Y & Z);
```

```
t = (0:8); % last bit goes from t=7 to t=8
```

```
x = [X; X(end)]; % extend duration of last bit to t=8
```

```
y = [Y; Y(end)];
```

```
z = [Z; Z(end)];
```

```
f = [F; F(end)];
```

a2d, xaxis, yaxis
are in Canvas M-files

```
figure;
```

```
subplot(4,1,1); stairs(t,x,'b-');
```

```
    yaxis(0,2,0:1); xaxis(0,8,0:8); ylabel('X');
```

```
subplot(4,1,2); stairs(t,y,'b-');
```

```
    yaxis(0,2,0:1); xaxis(0,8,0:8); ylabel('Y');
```

```
subplot(4,1,3); stairs(t,z,'b-');
```

```
    yaxis(0,2,0:1); xaxis(0,8,0:8); ylabel('Z');
```

```
subplot(4,1,4); stairs(t,f,'r-');
```

```
    yaxis(0,2,0:1); xaxis(0,8,0:8); ylabel('F');
```

```
xlabel('\itt');
```

verify truth-table in full minterm SOP form

$$F = X'Y'Z + XYZ' + XYZ$$

simplified form

$$F = XY + X'Y'Z$$

```
n = (0:7)';
```

```
[X,Y,Z] = a2d(n,3);
```

```
F = (~X & ~Y & Z) | (X & Y & ~Z) | (X & Y & Z);
```


```
[n, X, Y, Z, F, ~X&~Y&Z, X&Y&~Z, X&Y&Z]
```

0	0	0	0	0	0	0	0
1	0	0	1	1	1	0	0
2	0	1	0	0	0	0	0
3	0	1	1	0	0	0	0
4	1	0	0	0	0	0	0
5	1	0	1	0	0	0	0
6	1	1	0	1	0	1	0
7	1	1	1	1	0	0	1

F = OR-ing of the three individual minterm columns

Simulink implementation - AND-OR version

$$F = XY + X'Y'Z$$

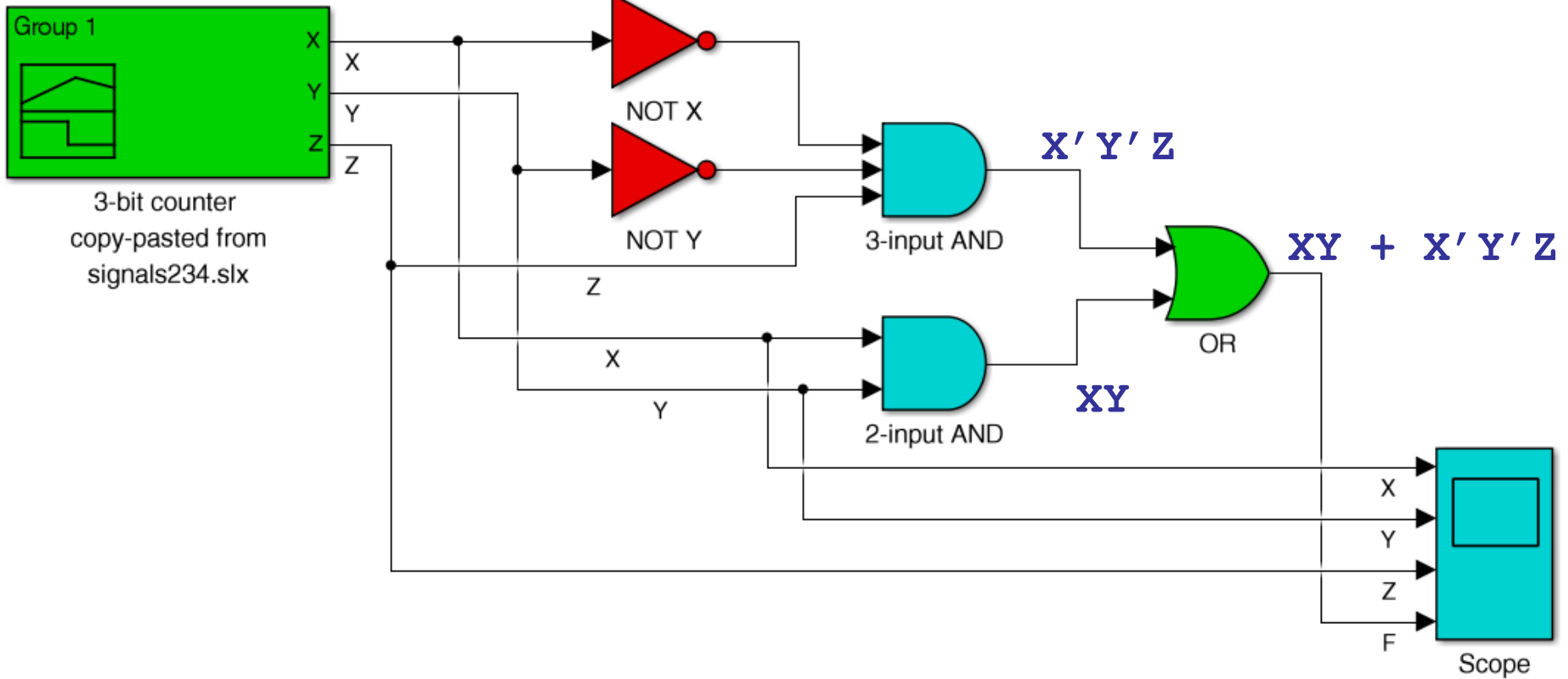

see file **fig1_5.slx** included in Canvas M-files folder


→
scope output


Simulink implementation

$$F = XY + X'Y'Z$$

X	Y	Z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1


scope output

 

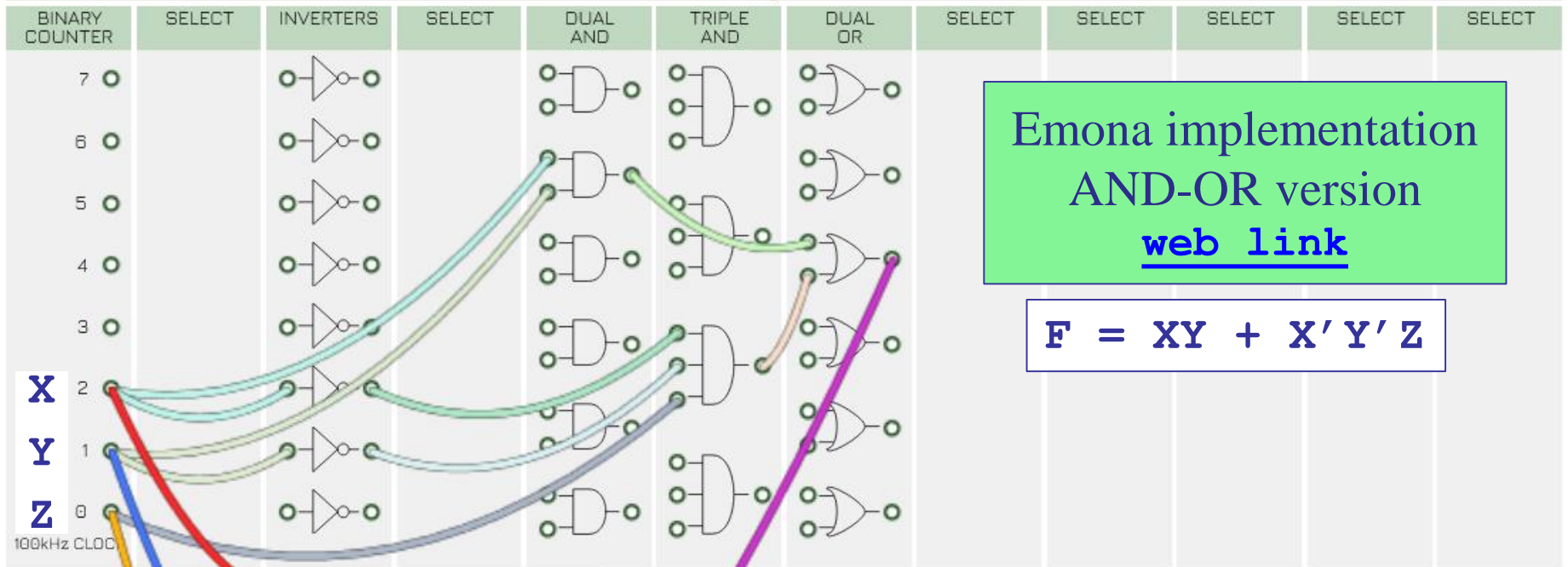

Emona implementation
AND-OR version
[web link](#)

$$F = XY + X'Y'Z$$

 

Example Summary:

- (a) we started with a truth-table specification
- (b) and constructed the logic function, $F = f(X,Y,Z)$
- (c) then, obtained a gate-level realization (and variants)
- (d) implemented it with MATLAB
- (e) and realized it in Simulink and on the Emona board

more general procedures

- Design Levels:**
- (a) functional definition level
 - (b) transistor level
 - (c) truth-table level, FPGA look-up tables
 - (d) gate-level realizations
 - (e) Verilog HDL, structural or behavioral models
 - (f) MATLAB, Simulink, Emona implementations


integrated circuit complexity

complexity	gates/chip	application examples
small scale integration (SSI)	10	logic gates, flip flops
medium scale integration (MSI)	10-100	adders, counters
large scale integration (LSI)	100-10,000	ROM, RAM, 8-bit processors
very large scale integration (VLSI)	10,000-100,000	16- and 32-bit processors










[web link - Wikipedia - Integrated Circuits](#)

Integrated Circuits (ICs)
LSI, MSI, VLSI
Moore's Law



Fig. 1-8 Dual Inline Pin (DIP) Packages:
(A) 14-Pin; (B) 20-Pin; (C) 28-Pin

 



Examples of ICs

      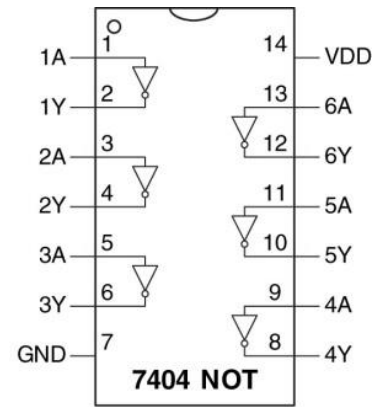  

NAND gate

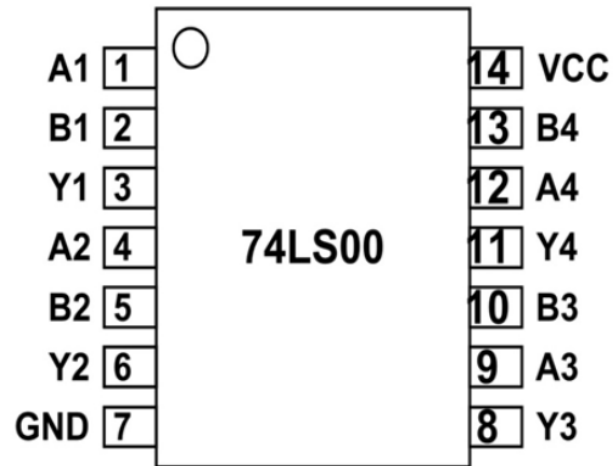 


NOR gate

  

CMOS NOT gate

<https://en.wikipedia.org/wiki/CMOS>

PMOS transistor

 


NMOS transistor

(b)


V_{IN}	Q1	Q2	V_{OUT}
0.0 (LOW)	off	on	3.3 (HIGH)
3.3 (HIGH)	on	off	0.0 (LOW)

(c)

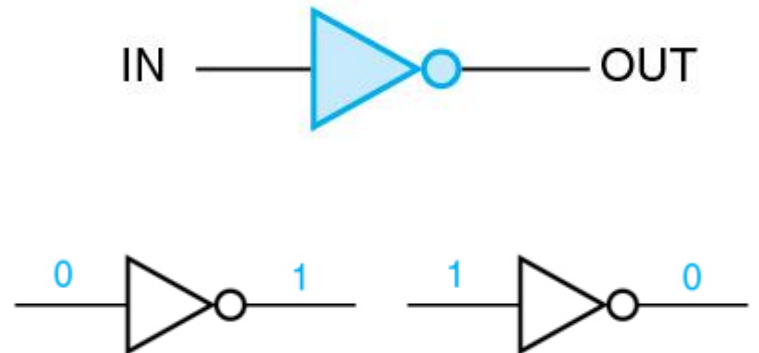

CMOS NAND gate

(a)

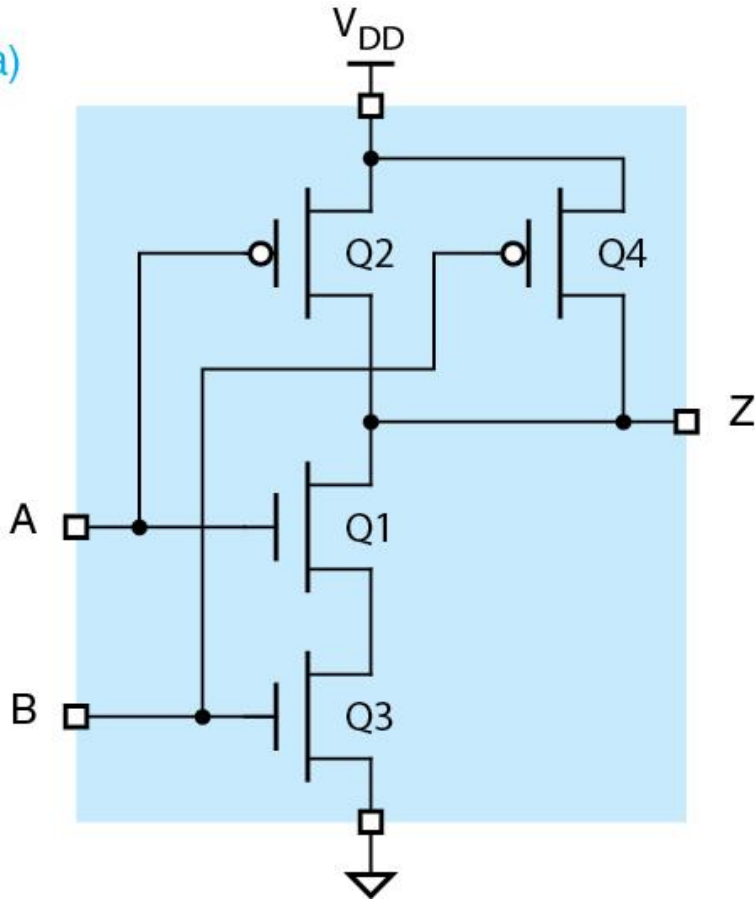

(b)

A	B	Q1	Q2	Q3	Q4	Z
LOW	LOW	off	on	off	on	HIGH
LOW	HIGH	off	on	on	off	HIGH
HIGH	LOW	on	off	off	on	HIGH
HIGH	HIGH	on	off	on	off	LOW


(c)



X	Y	X NAND Y
0	0	1
0	1	1
1	0	1
1	1	0

CMOS NOR gate

(a)

 

(b)


A	B	Q1	Q2	Q3	Q4	Z
LOW	LOW	off	on	off	on	HIGH
LOW	HIGH	off	on	on	off	LOW
HIGH	LOW	on	off	off	on	LOW
HIGH	HIGH	on	off	on	off	LOW

(c)




X	Y	X NOR Y
0	0	1
0	1	0
1	0	0
1	1	0

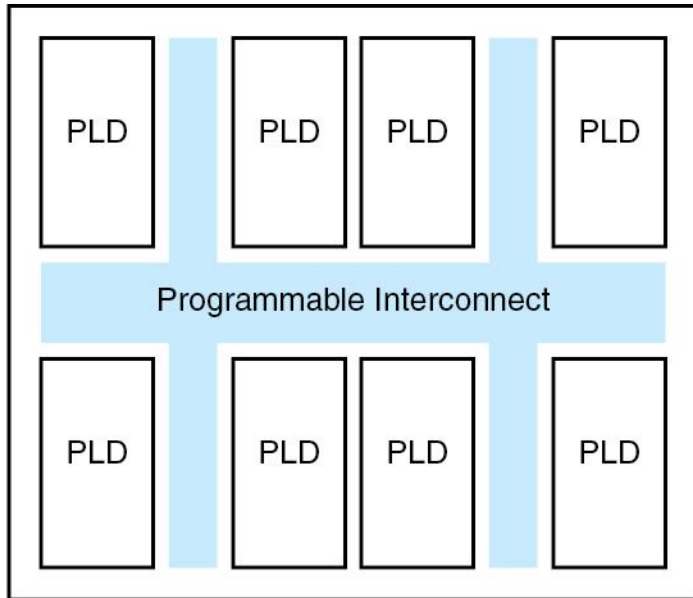(A) Complex Programmable Logic Device (CPLD)
(B) Field-Programmable Gate Array (FPGA)



(a)

 


(b)

□ = logic block

- Design Levels:**
- (a) functional definition level
 - (b) transistor level
 - (c) truth-table level, FPGA look-up tables
 - (d) gate level
 - (e) Verilog HDL, structural or behavioral models
 - (f) MATLAB and Simulink implementations

Example: switch model for a **multiplexer** function

Wakerly / Sect. 1.13


 


some multiplexer applications:

- network lines
- telephone lines
- communication systems
- memory controllers


MSI quad package for a multiplexer chip - TI SN74F157

S
A
B
Z

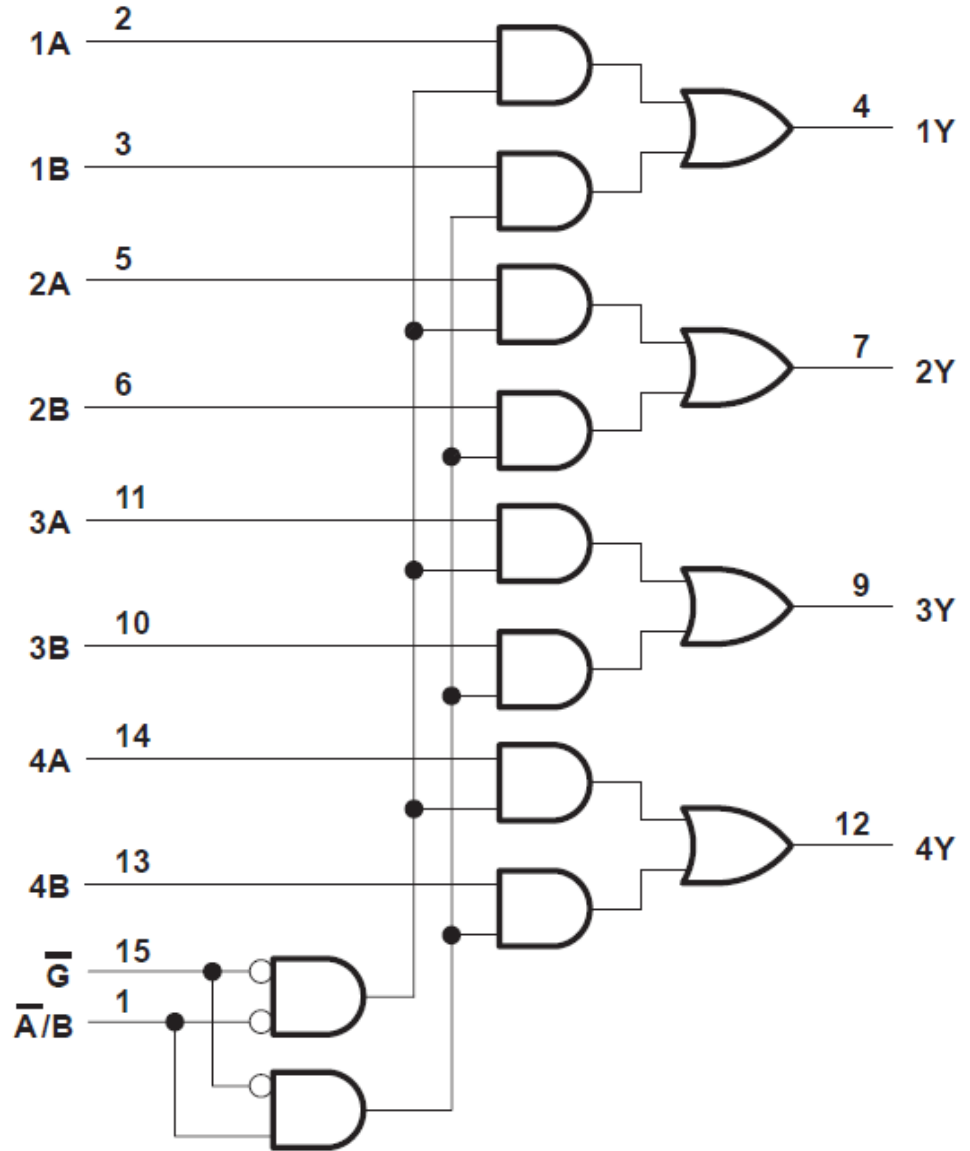 


CMOS transistor model for multiplexer function
 
<https://en.wikichip.org/wiki/multiplexer>



CMOS transmission gate

 

truth table for multiplexer function

S	A	B	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

$$Z = S'AB' + S'AB + SA'B + SAB$$

full minterm sum-of-products (SOP) form

$$S'AB' + S'AB = S'A$$

$$SA'B + SAB = SB$$

simplified form

$$Z = S'A + SB$$

used properties

$$A' + A = 1$$

$$B' + B = 1$$

truth table for multiplexer function

S	A	B	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

$$Z = S'AB' + S'AB + SA'B + SAB$$

full minterm sum-of-products (SOP) form

$$S'AB' + S'AB = S'A$$

$$SA'B + SAB = SB$$

simplified form


$$Z = S'A + SB$$

K-map derivation

		AB			
		00	01	11	10
S	0			1	1
	1		1	1	

K-maps are 2-D versions of truth tables and are fully discussed in unit-3, Ch.3

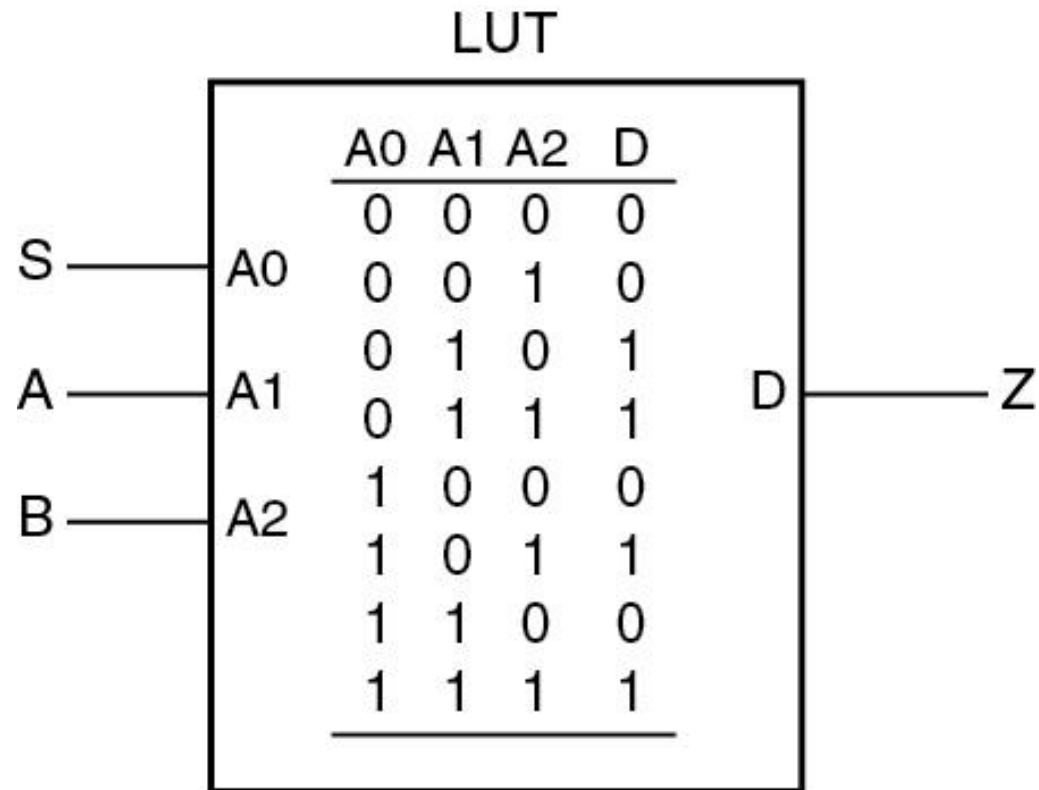multiplexer function implemented on
FPGA look-up table (LUT)




gate-level logic diagram for multiplexer function

$$Z = S'A + SB = ((S'A)' (SB)')'$$

AND-OR

NAND-NAND

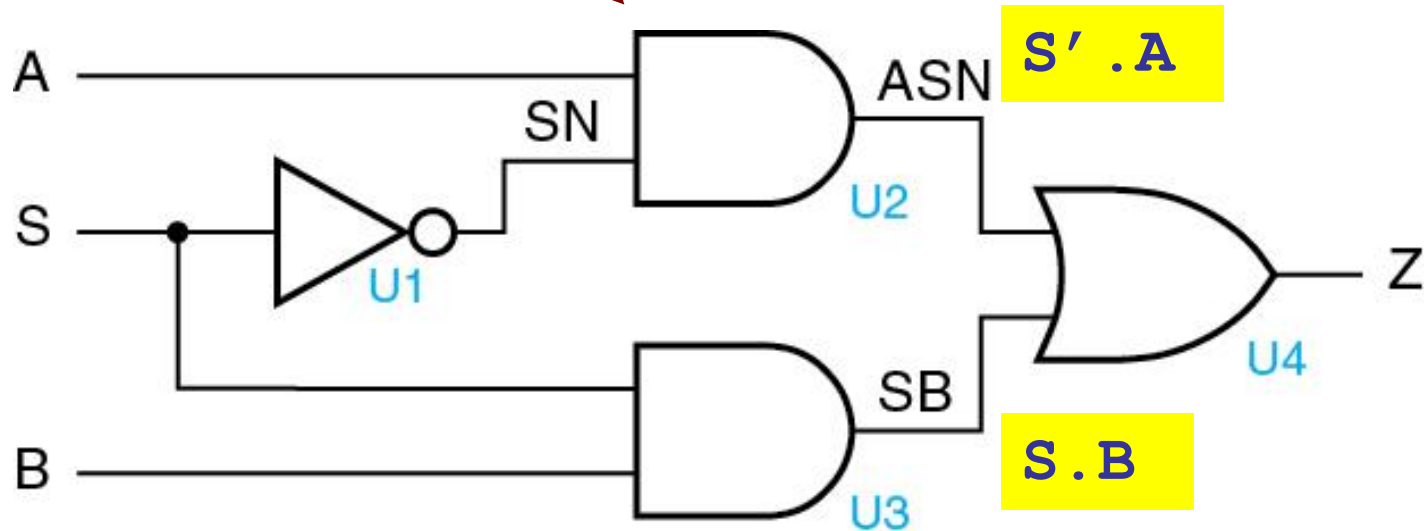


two-level, AND-OR, realization

gate-level logic diagram for multiplexer function

$$Z = S'A + SB = ((S'A)' (SB)')'$$

AND-OR

NAND-NAND

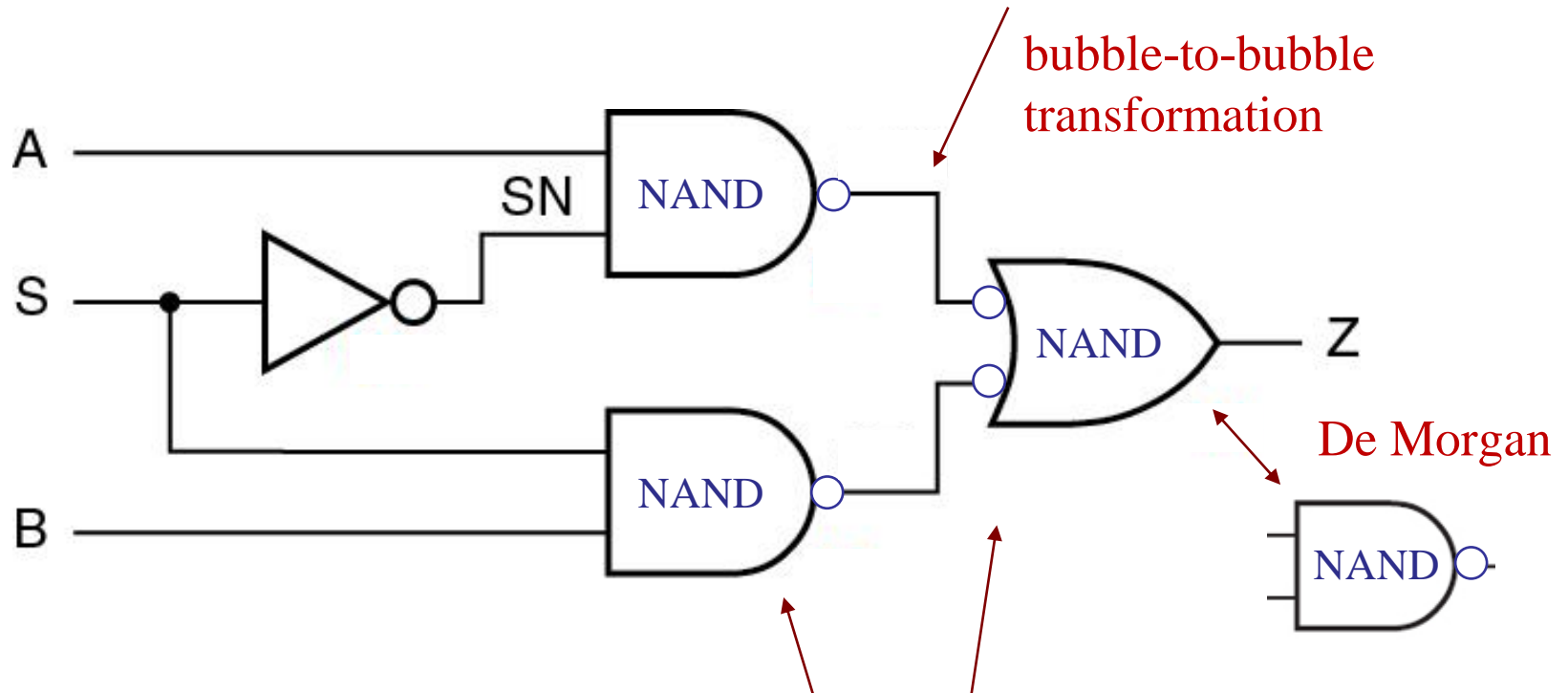


two-level, NAND-NAND, realization

Verilog HDL – structural model

see also Wikipedia article on [hardware description languages](#)
 
```
// 2-input multiplexer  
  
module Ch1mux_s(A, B, S, Z);  
  
    input A, B, S;  
    output Z;  
    wire SN, ASN, SB;  
  
    not U1 (SN, S);  
    and U2 (ASN, A, SN);  
    and U3 (SB, B, S);  
    or U4 (Z, ASN, SB);  
  
endmodule
```



© 2018 Pearson Education, J. F. Wakerly, *Digital Design Principles and Practices*, 5/e

see also <https://nandland.com/> for tutorials on HDLs


Verilog HDL – behavioral model

```
// 2-input multiplexer
```

```
module Ch1mux_b(A, B, S, Z);  
  input A, B, S;  
  output reg Z;
```

```
  always @ (A, B, S) if (S==1) Z = B; else Z = A;
```

```
endmodule
```

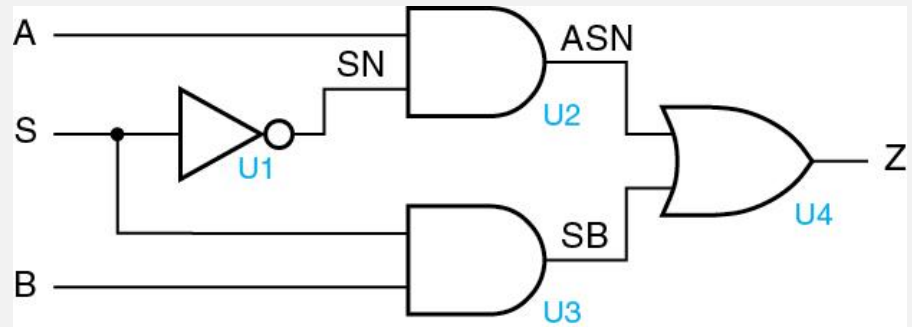

MATLAB implementation with M-file

$$Z = S'A + SB$$

```
% mux.m - 2-input multiplexer function
```

```
function Z = mux(S,A,B)  
    Z = ((~S) & A) | (S & B);
```

```
% alternatively,  
% Z = or(and(not(S),A), and(S,B));
```

or, and, not,
are built-in
functions

anonymous MATLAB function version

```
mux = @(S,A,B) ((~S) & A) | (S & B);
```

```
% Usage: Z = mux(S,A,B);
```

```

mux = @(S,A,B) ((~S) & A) | (S & B);

[S,A,B] = a2d(0:7,3);    % all possible S,A,B values
                        % a2d to be discussed in Unit-2

Z = mux(S,A,B);

[S,A,B,Z]                % print the truth table


%   S   A   B   Z        % S,A,B,Z are columns
%   ---
%   0   0   0   0
%   0   0   1   0
%   0   1   0   1
%   0   1   1   1
%   1   0   0   0
%   1   0   1   1
%   1   1   0   0
%   1   1   1   1

```


note:

the operations **&** and **|** are vectorized in MATLAB

MATLAB / Simulink implementation

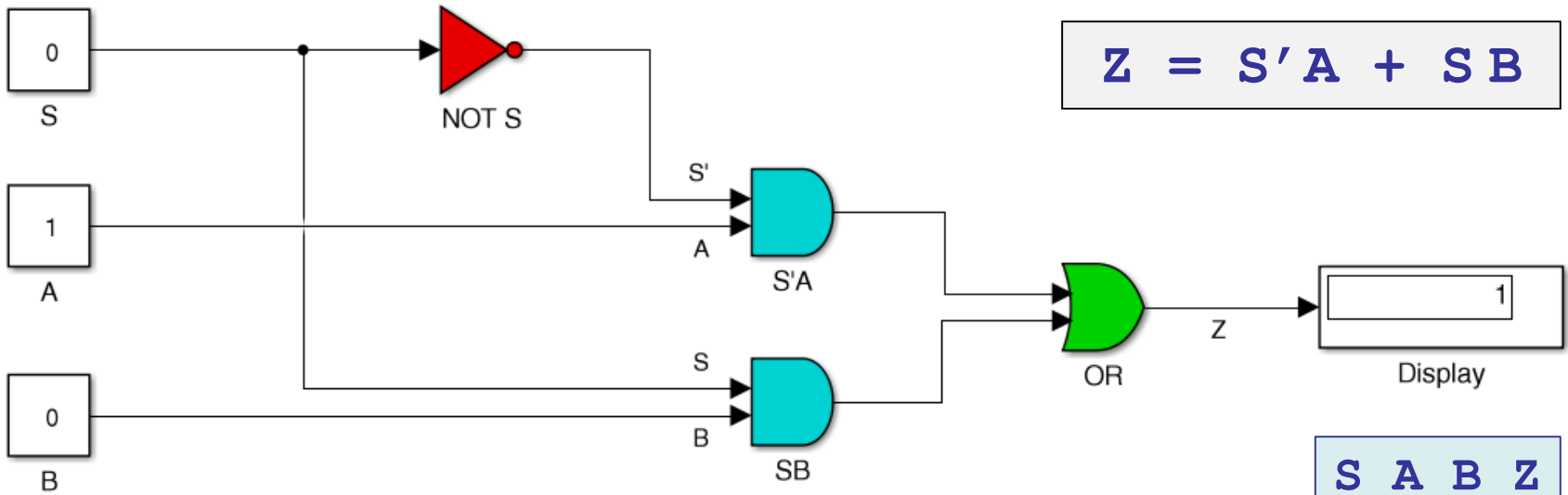

simulink implementation

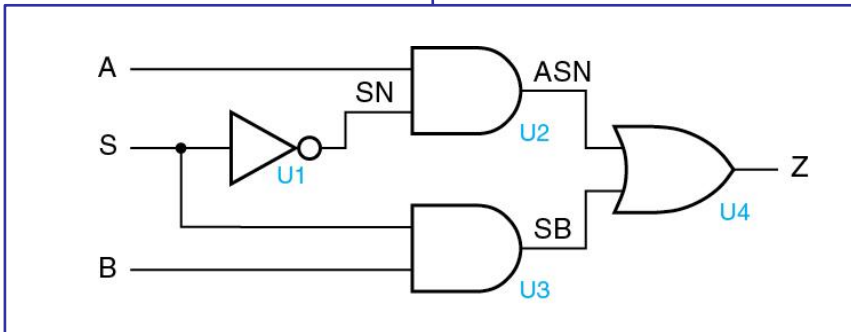


S	A	B	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

open library


run button

time range

Simulink desktop

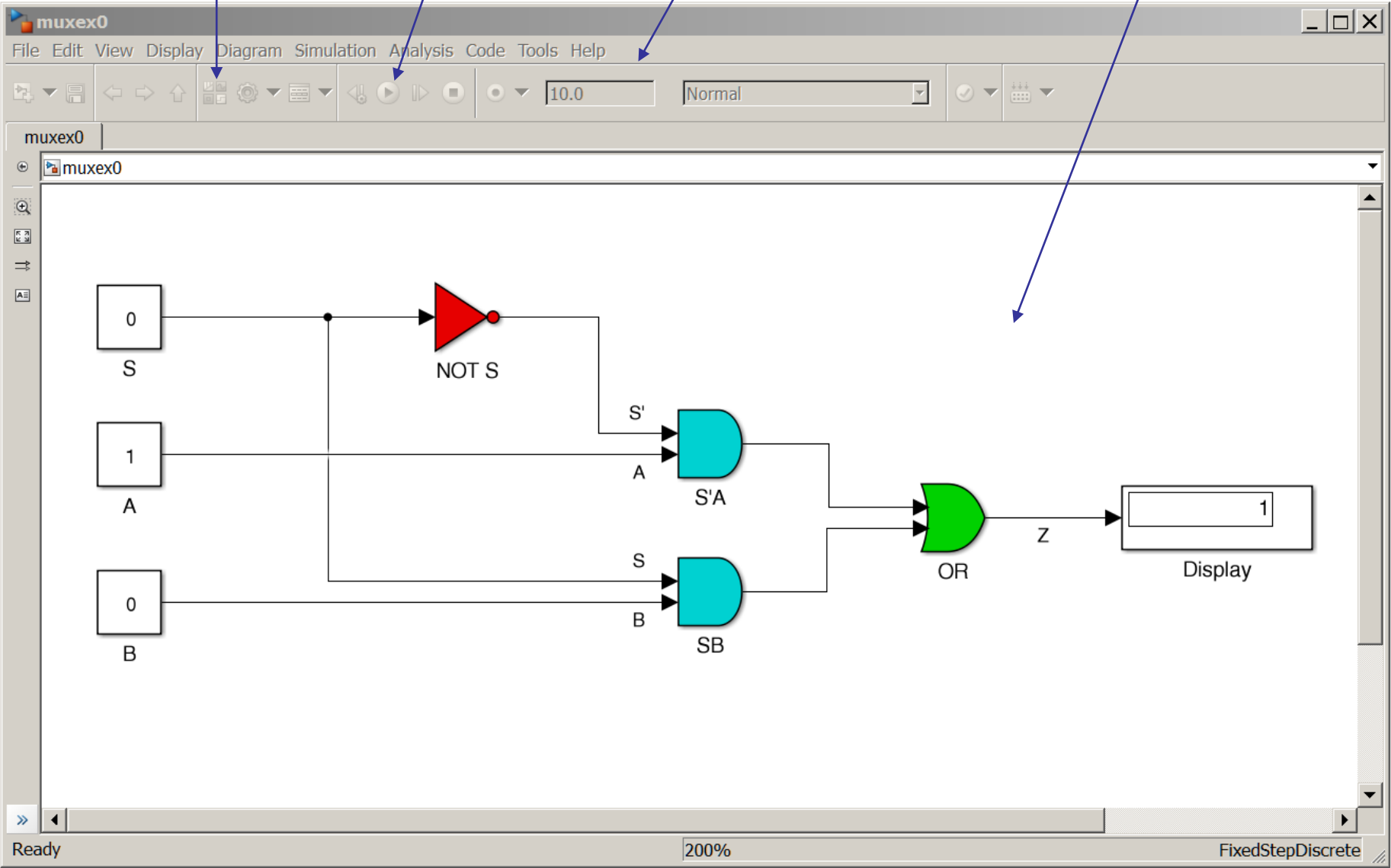

Simulink library – commonly used blocks

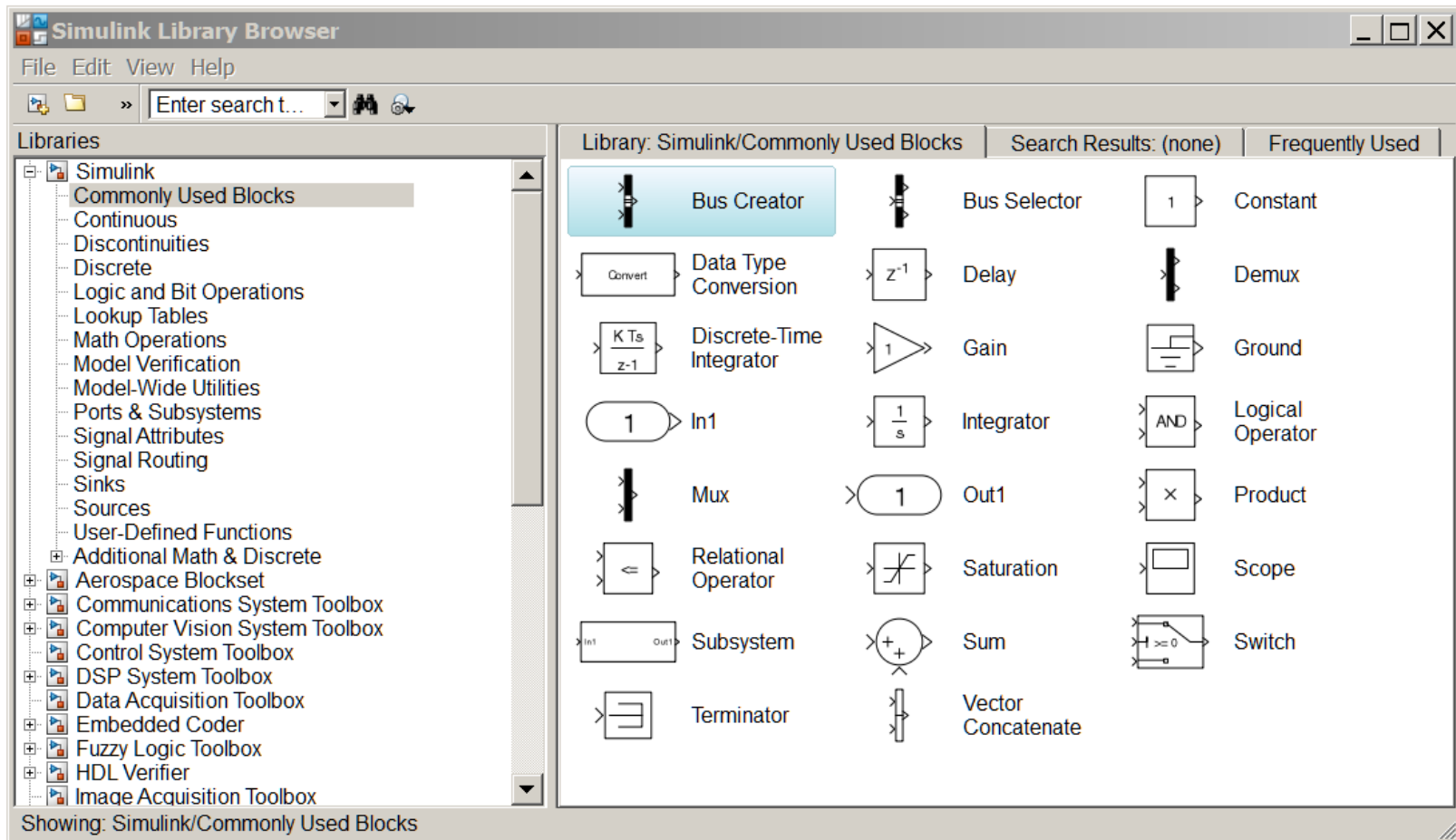

Simulink library – logic and bit operations

The screenshot displays the Simulink Library Browser interface. The left pane shows a tree view of libraries, with "Logic and Bit Operations" selected. The right pane shows a grid of blocks from the "Simulink/Logic and Bit Operations" library. The blocks are arranged in a grid with columns for "Library: Simulink/Logic and Bit Operations", "Search Results: (none)", and "Frequently Used".

Library: Simulink/Logic and Bit Operations	Search Results: (none)	Frequently Used
Bit Clear	Bit Set	Bitwise AND Operator
Combinatorial Logic	Compare To Constant	Compare To Zero
Detect Change	Detect Decrease	Detect Fall Negative
Detect Fall Nonpositive	Detect Increase	Detect Rise Nonnegative
Detect Rise Positive	Extract Bits Upper Half	Interval Test
Interval Test Dynamic	Logical Operator	Relational Operator
Shift Arithmetic		

Showing: Simulink/Logic and Bit Operations

Simulink library – sources

The screenshot displays the Simulink Library Browser interface. The left pane shows a tree view of libraries, with 'Sources' selected under the 'Simulink' library. The main area is divided into three columns: 'Library: Simulink/Sources', 'Search Results: (none)', and 'Frequently Used'. The 'Library' column lists various source blocks with their respective icons. The 'Search Results' column is currently empty. The 'Frequently Used' column lists blocks that are commonly used in models.

Library: Simulink/Sources	Search Results: (none)	Frequently Used
Band-Limited White Noise	Chirp Signal	Clock
1 Constant	Counter Free-Running	Counter Limited
12.34 Digital Clock	Enumerated Constant	untitled.mat From File
simin From Workspace	Ground	1 In1
Pulse Generator	Ramp	Random Number
Repeating Sequence	Repeating Sequence Inter...	Repeating Sequence Stair
Group 1 Signal 1 Signal Builder	Signal Generator	Sine Wave
Step	Uniform Random Number	

Showing: Simulink/Sources


Simulink library – sinks

The screenshot shows the Simulink Library Browser interface. The left pane lists various libraries, with 'Sinks' selected. The main pane displays a grid of sink blocks under the 'Library: Simulink/Sinks' tab. The search results are empty, and the 'Frequently Used' section is also empty. The blocks shown are:

Library: Simulink/Sinks	Search Results: (none)	Frequently Used
Display	Floating Scope	Out1
Scope	Stop Simulation	Terminator
untitled.mat To File	simout To Workspace	XY Graph

Showing: Simulink/Sinks

MATLAB / Simulink implementation

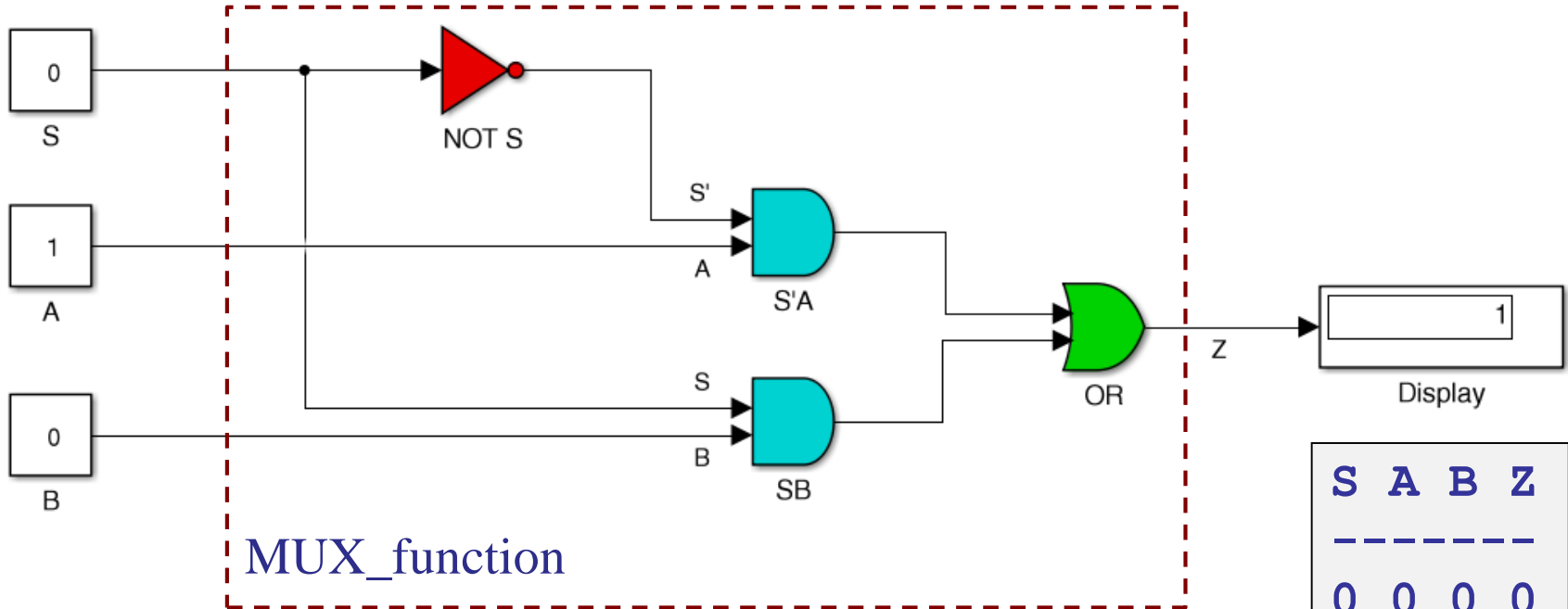



MUX_function

subsystem model can be exported into Verilog HDL, or VHDL, from Simulink

$$Z = S'A + SB$$

S	A	B	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1


MATLAB / Simulink implementation

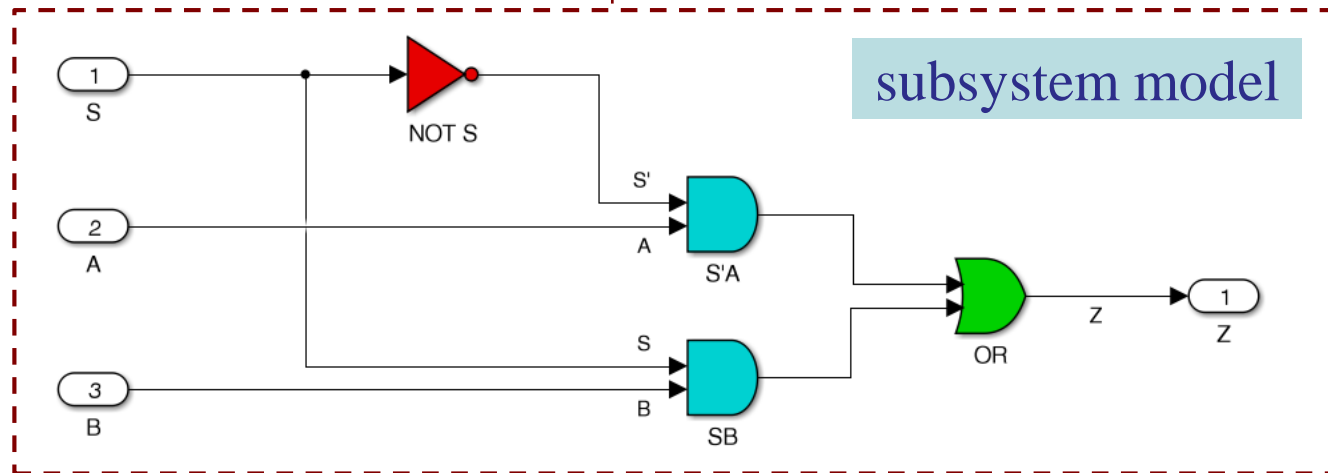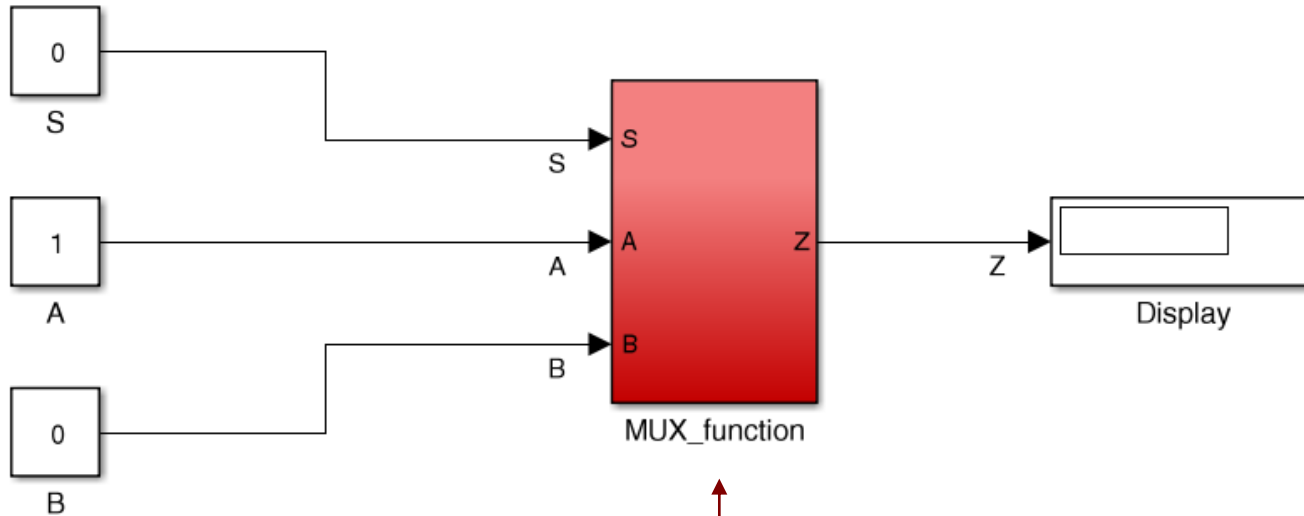


$$Z = S' A + S B$$

Verilog code generated by Simulink

```
module MUX_function(S,A,B,Z);  
  
    input    S, A, B;  
    output   Z;  
  
    wire S_1, S_2, S_3, S_4, S_A_out1;  
  
    assign S_1 = ~ S;  
    assign S_2 = S_1;  
    assign S_3 = S_2 & A;  
    assign S_4 = S & B;  
    assign S_A_out1 = S_3 | S_4;  
    assign Z = S_A_out1;  
  
endmodule
```

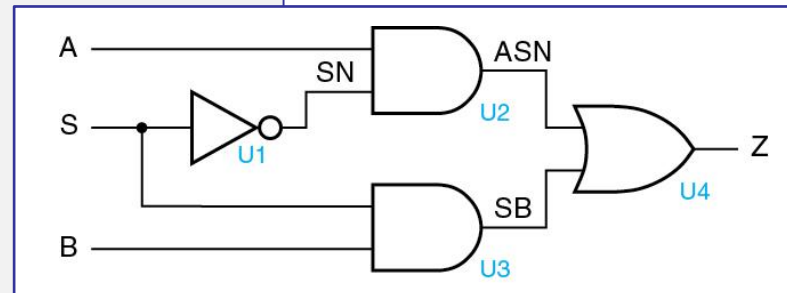


MATLAB / Simulink implementation

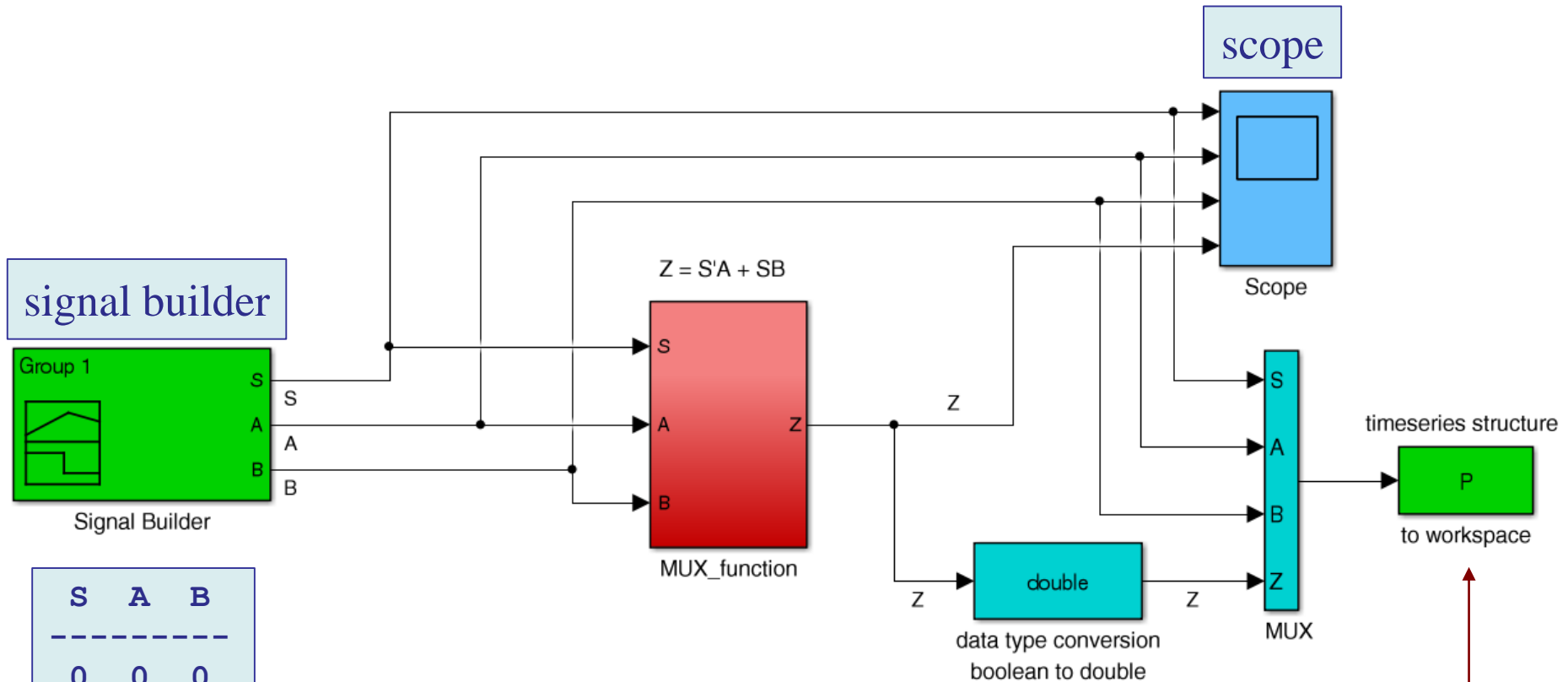

S	A	B
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1


see **muxdem3.slx**
on Canvas Files
M-files folder

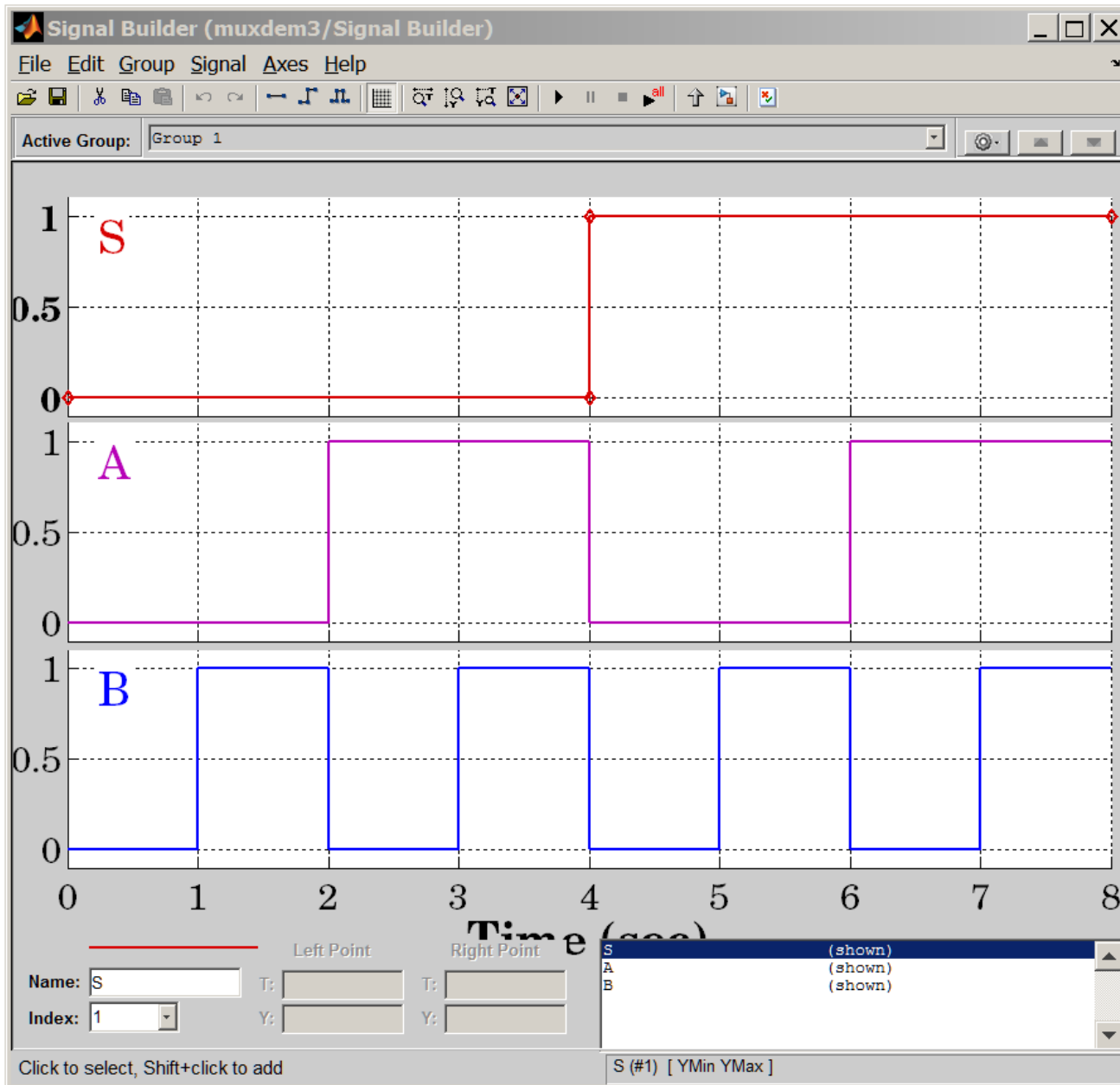inputs and output saved as a **timeseries structure** into the workspace block, and brought into MATLAB for plotting



signal builder

S	A	B
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

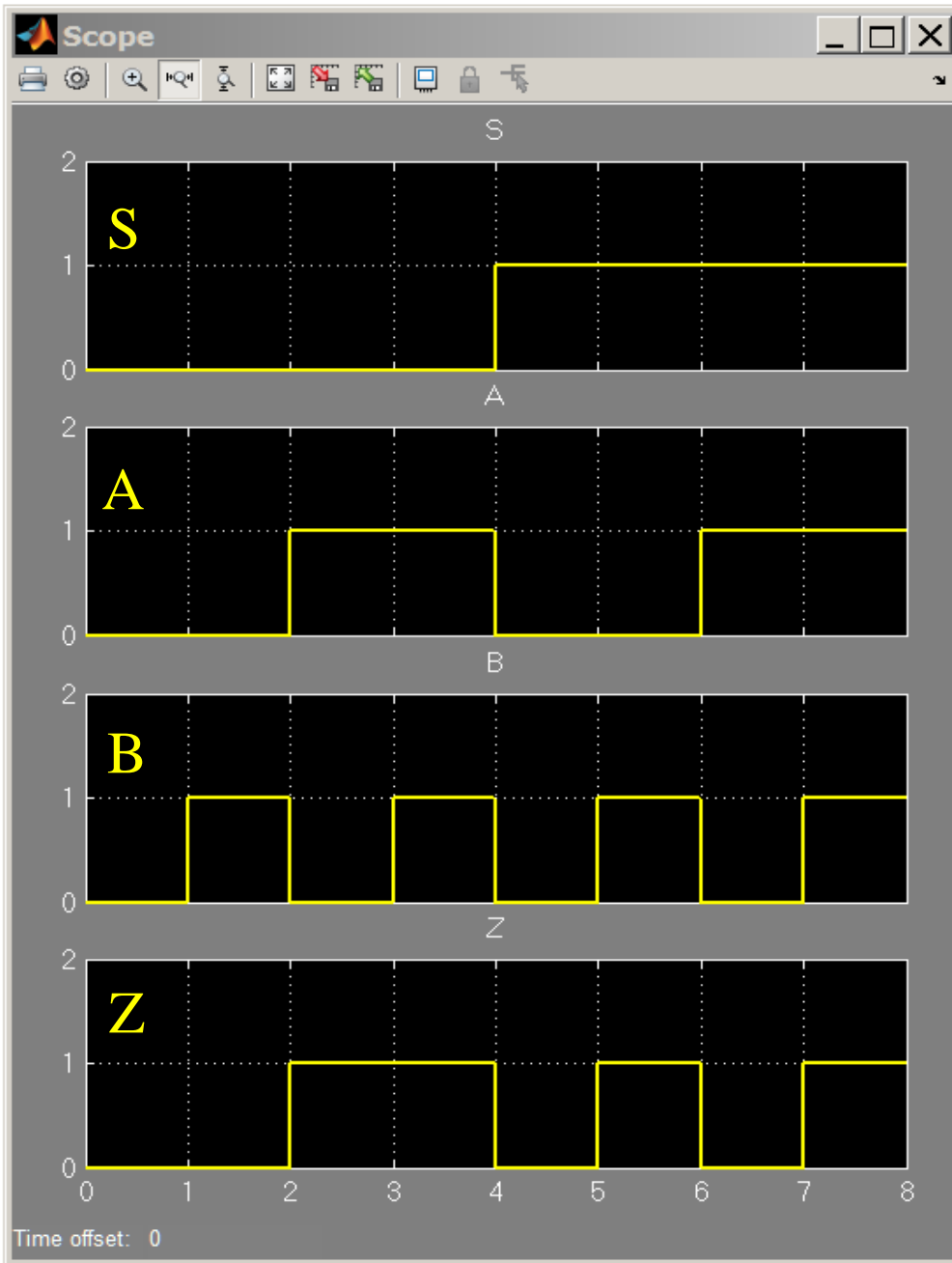

timing diagram from scope

S	A	B	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

```

% extract data from timeseries structure P

t = P.time;           % equivalent to t = 0:0.01:8
S = P.data(:,1);     % array lengths = 801 by default
A = P.data(:,2);
B = P.data(:,3);
Z = P.data(:,4);

figure;
subplot(4,1,1); stairs(t,S,'m-');
ylabel('S'); xaxis(0,8,0:8); yaxis(0,2,0:2);

subplot(4,1,2); stairs(t,A,'b-');
ylabel('A'); xaxis(0,8,0:8); yaxis(0,2,0:2);

subplot(4,1,3); stairs(t,B,'b-');
ylabel('B'); xaxis(0,8,0:8); yaxis(0,2,0:2);


subplot(4,1,4); stairs(t,Z,'r-');
ylabel('Z'); xaxis(0,8,0:8); yaxis(0,2,0:2);
xlabel('\itt');

% axis() and yaxis() are on Canvas Resources;

```

staircase
plot

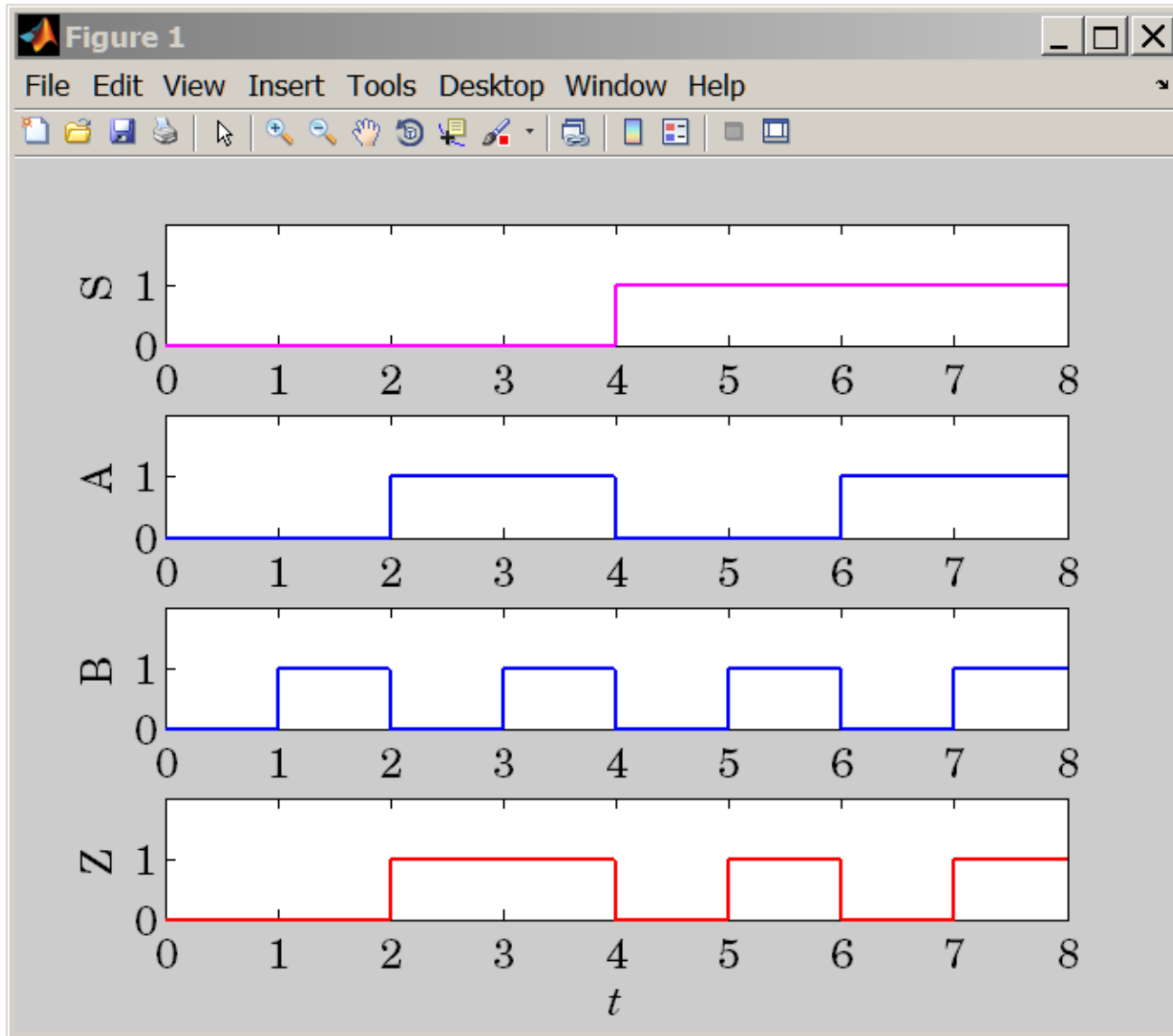timing diagram from timeseries structure P



S	A	B	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

$$Z = S'A + SB$$

```
% calculate and plot timing diagram
```

```
t = (0:8); % last bit t=7 to t=8  
[S,A,B] = a2d(0:7,3); % 3-bit counter  
  
S = [S; S(end,:)]; % extend last bit to t=8  
A = [A; A(end,:)]; % extend last bit to t=8  
B = [B; B(end,:)]; % extend last bit to t=8  
  
Z = (~S & A) | (S & B); % output
```

```
figure;
```

```
subplot(4,1,1); stairs(t,S,'m-');  
ylabel('S'); xaxis(0,8,0:8); yaxis(0,2,0:1);
```

```
subplot(4,1,2); stairs(t,A,'b-');  
ylabel('A'); xaxis(0,8,0:8); yaxis(0,2,0:1);
```


```
subplot(4,1,3); stairs(t,B,'b-');  
ylabel('B'); xaxis(0,8,0:8); yaxis(0,2,0:1);
```

```
subplot(4,1,4); stairs(t,Z,'r-');  
ylabel('Z'); xaxis(0,8,0:8); yaxis(0,2,0:1);  
xlabel('\itt');
```

&, | are vectorized operations

staircase
plot

timing diagram from plain MATLAB

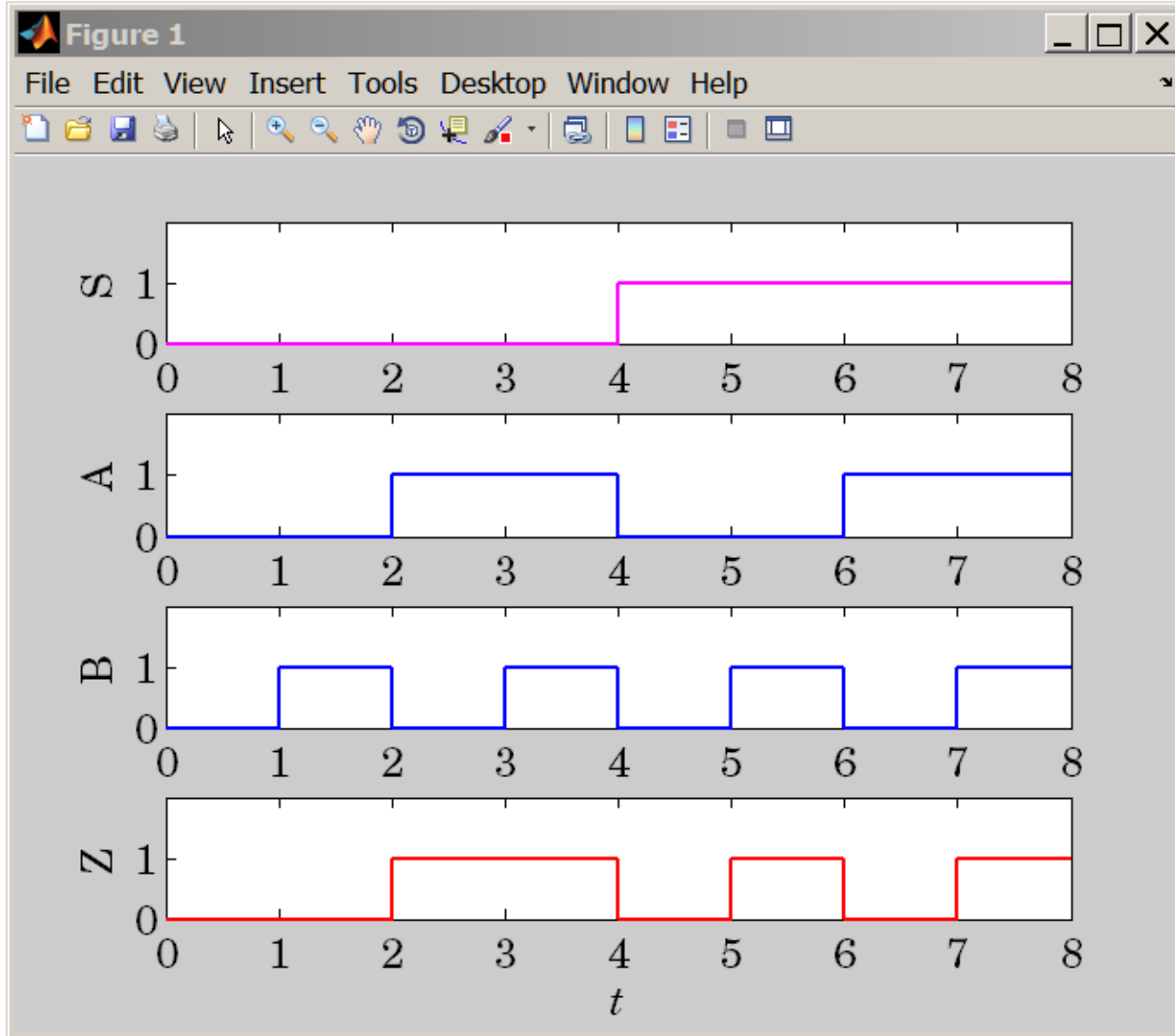


staircase
plot

S	A	B	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

$$Z = S'A + SB$$

using `plot()` instead of `stairs()`

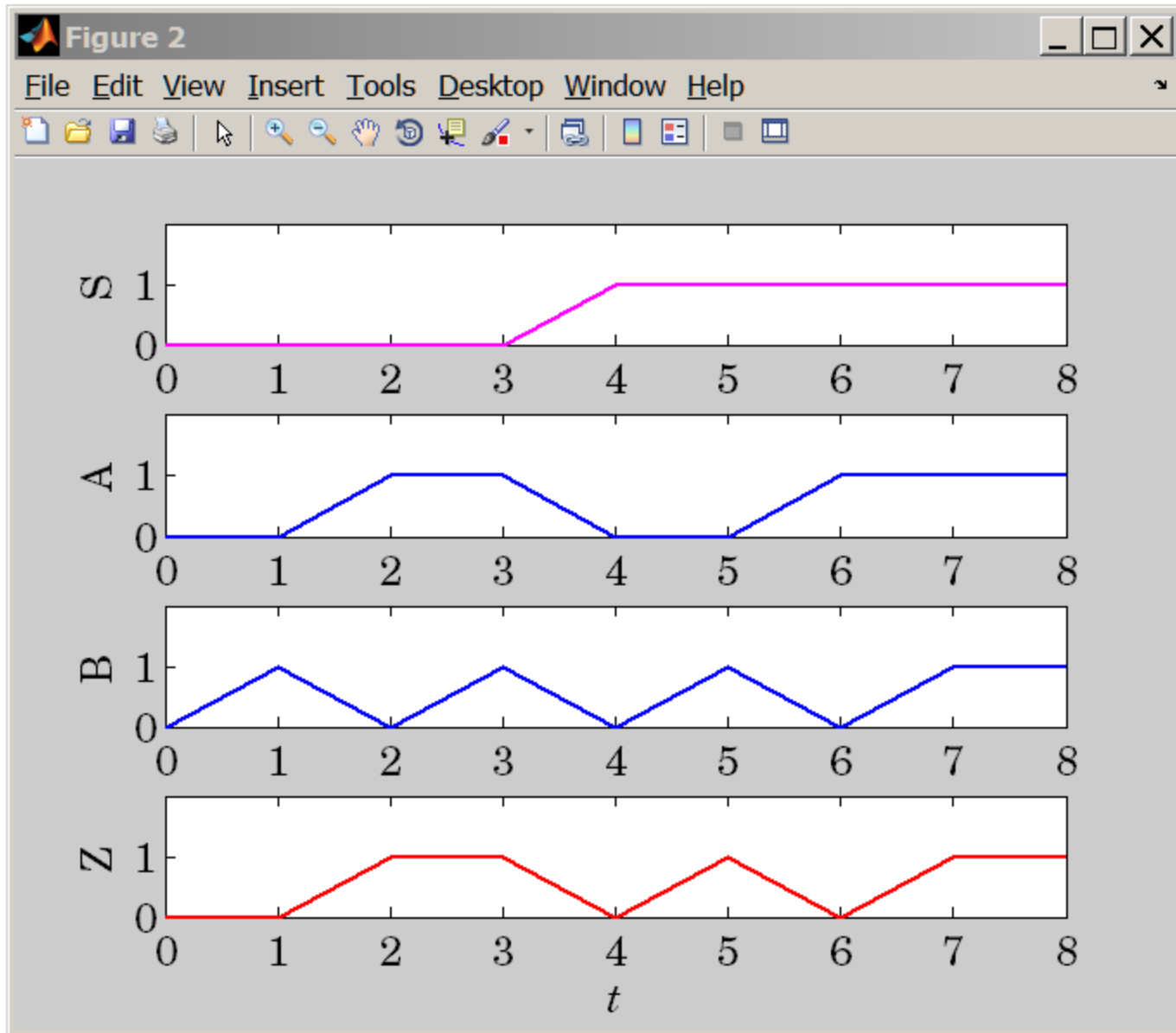

note: here, array lengths = 9


$$Z = S' A + S B$$

Additional notes on Simulink


see **muxdem3.slx**
on Canvas Files
M-files folder

click here to open
Simulink Library

set simulation duration to
8 time units


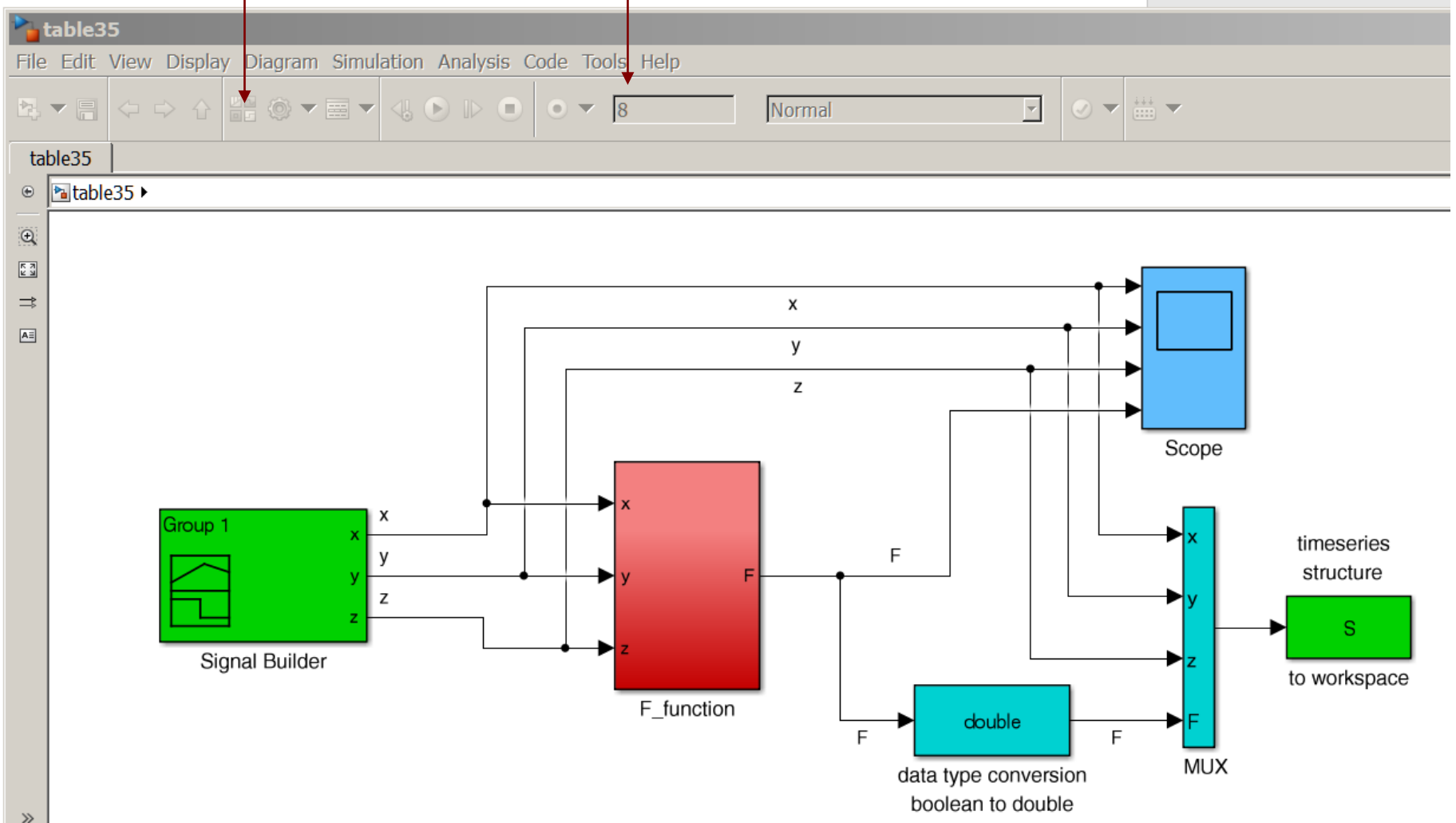


 click here to open scope parameters and select 4 axes (for X,Y,X,F) and time range of 8 units




drag the signal edges to change the shape of the signals

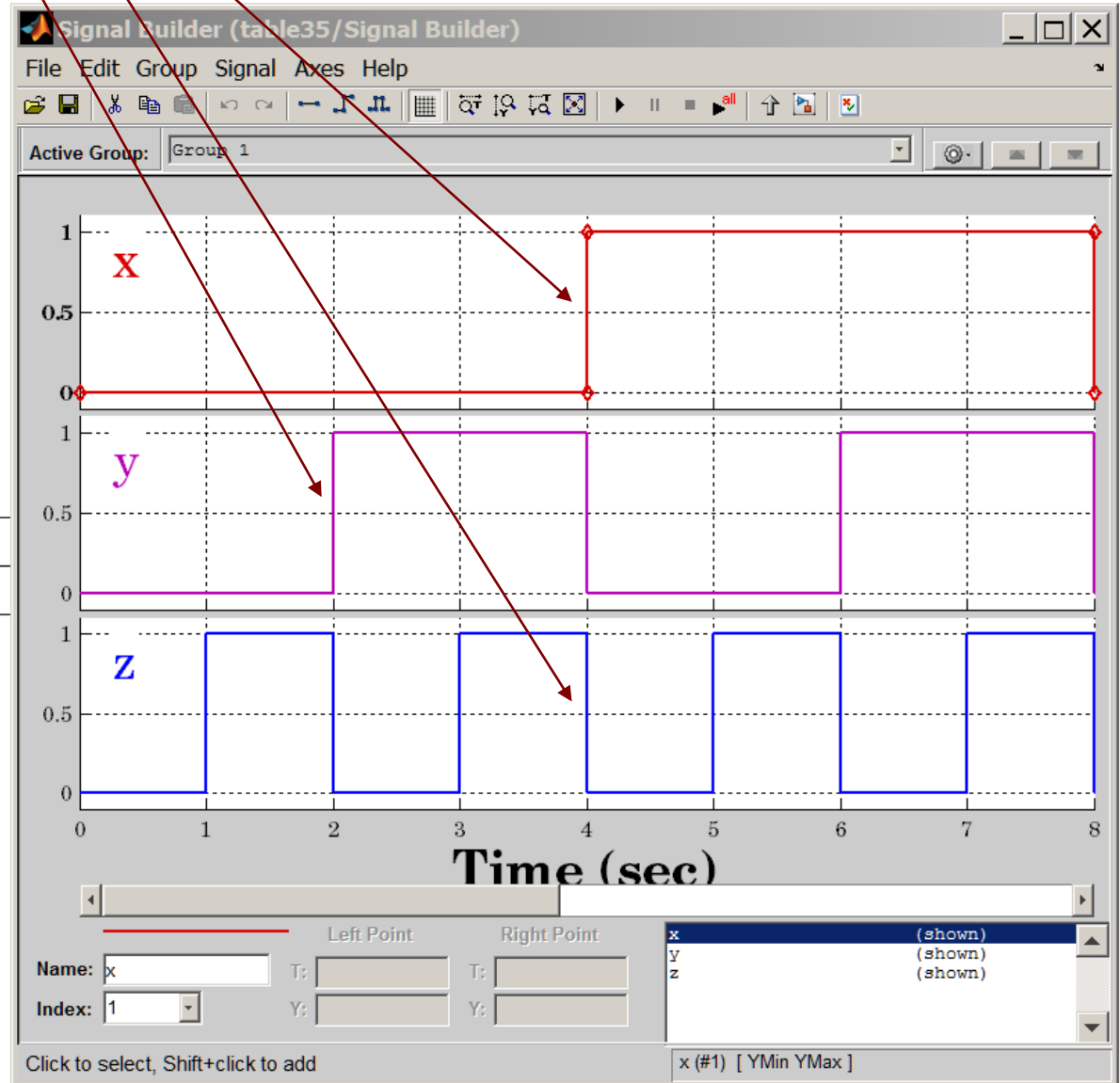 double-click on the Signal Builder block to view the signals X,Y,Z over the time range of 8 units



before exporting into Verilog, save the subfunction into a separate SLX Simulink file, then set the data types of the input/output ports to Boolean

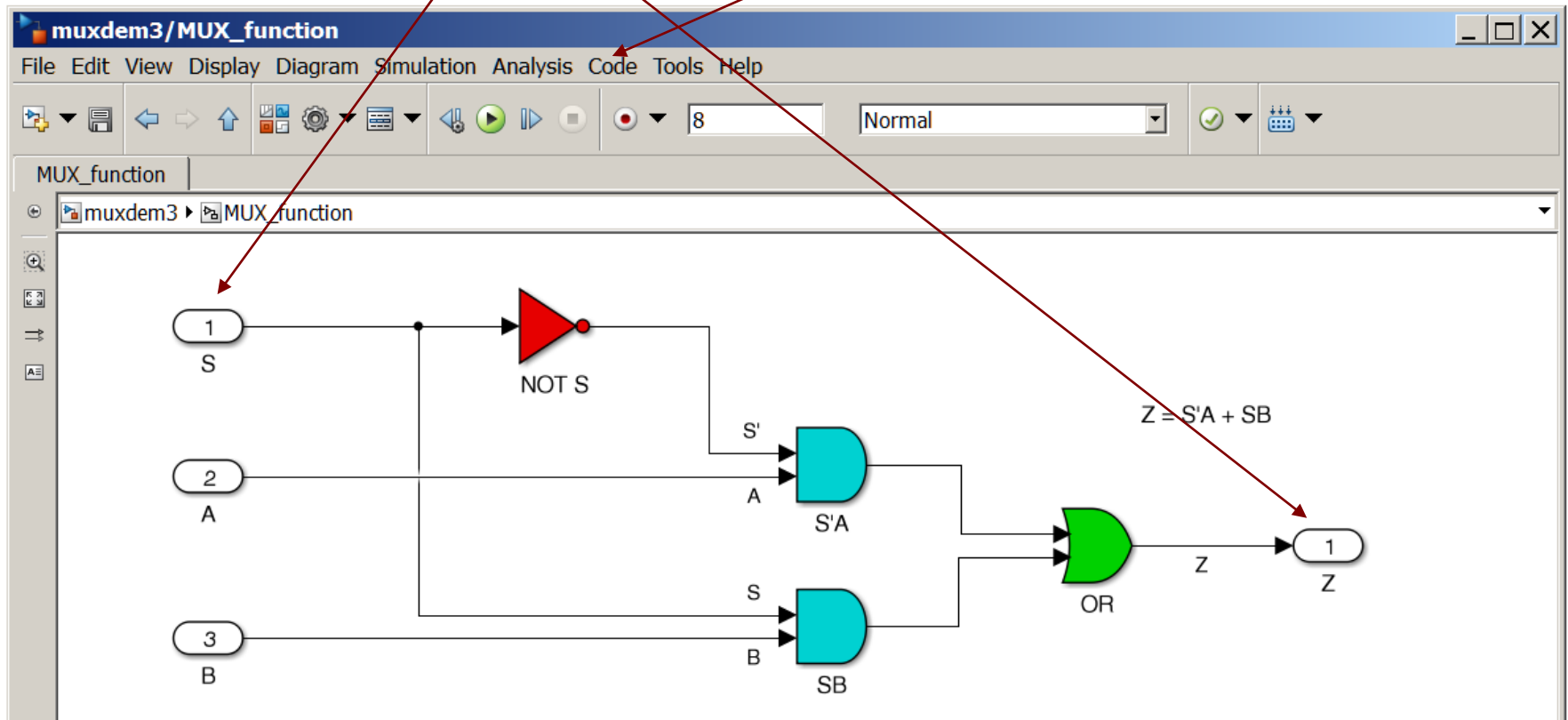
select Code, then HDL code, Options, and Verilog



to set the data types, double-click on each port, select signal attributes, and set data type to Boolean

Emona netCIRCUITlabs board

 
netCIRCUITlabs CONTROL UNIT with MULTIPLE PLUG-IN BOARDS



- ▶ The netCIRCUITlabs Control Unit, located in your lab or office, and will accept any netCIRCUITlabs Lab Experiment board.
- ▶ Fast and easy implementation. No software to install and no setting up required.
- ▶ Secure access for professor to all ADMIN functions including student records and tracking.

The experiments boards plugs into the *netCIRCUITlabs* Control Unit

 REL 3.0 DIGITAL LOGIC board - student wired experiments



All the logic functions and connections are implemented in an FPGA.

REL3.0 FUNCTIONALITY & EXPERIMENT CAPABILITIES

SIGNAL SOURCES:

- HI/LO Logic Switches x 8
- 8 bit Binary Counter
- 4 bit Gray Counter
- 4 bit Johnson Counter

OVER 60 GATES & FLIP-FLOPS:

- 2, 3 & 4-input OR gates
- X-OR gates
- 2, 3 & 4-input AND gates
- Inverters
- S/R, D & J/K Flip-Flops,
- Inverters
- Finite State Machines

STUDY:

- Boolean logic and algebra
- Combinatorial circuits
- Truth tables
- Karnaugh Maps
- Quine-McCluskey method
- Designing Synch & Asynch sequential circuits
- Flip flops
- State diagrams
- Design of FSM
- Registers, Counters, Multiplexers, Encoders etc
- Introduction to HDL (Verilog)


Multiplexer function implemented on the Emona board

User: orfanidis2 - Uid: 56 7/31/2020, 1:56:19 PM

username
must be clearly visible

time stamp
must be clearly visible

 scope settings – load the file ‘blank’ for default settings




user manual on Canvas

<http://ece-emonal.engr.rutgers.edu/>

Multiplexer function implemented on the Emona board

User: orfanidis2 - Uid: 56

7/31/2020, 1:56:19 PM

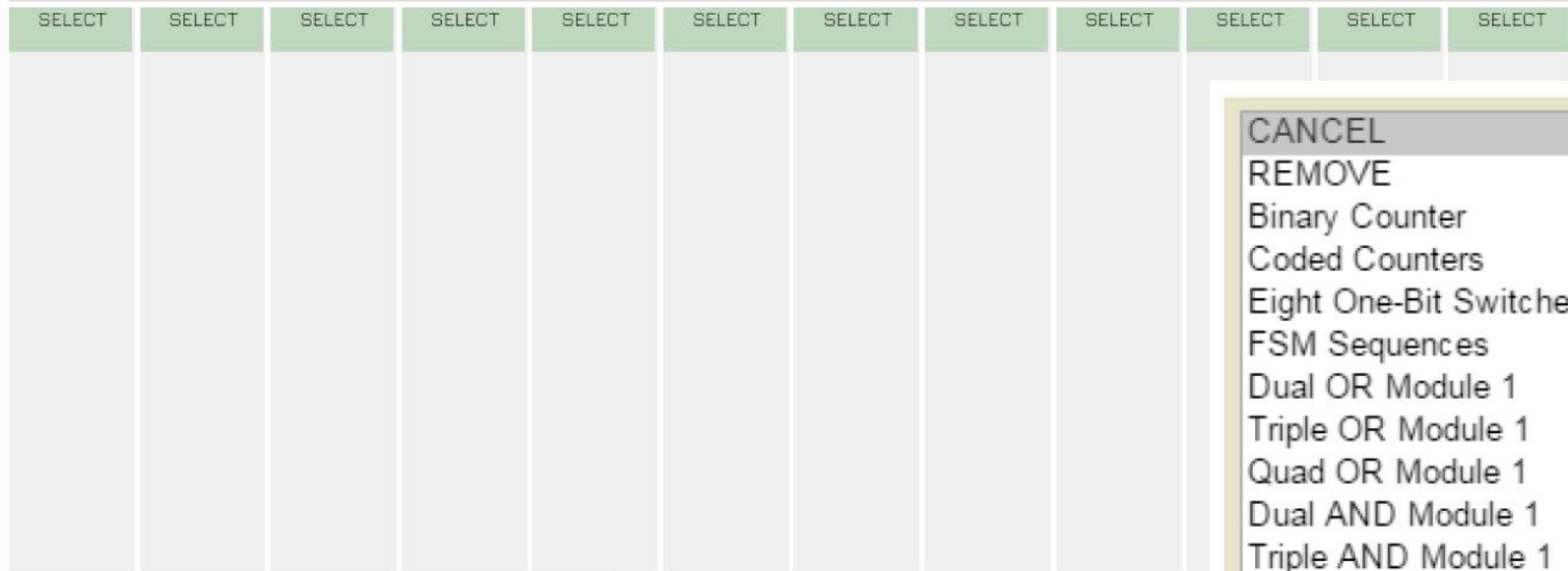

- CANCEL
- REMOVE
- Binary Counter
- Coded Counters
- Eight One-Bit Switches
- FSM Sequences
- Dual OR Module 1
- Triple OR Module 1
- Quad OR Module 1
- Dual AND Module 1
- Triple AND Module 1
- Quad AND Module 1
- Dual NAND Module 1
- Dual NAND Module 2
- XOR Module 1
- Gate Medley 1
- Inverters
- D Flip Flops 1
- D Flip Flops 2
- JK Flip Flops 1
- JK Flip Flops 2
- SR Flip Flop And Half Adder 1

1 users

Load Save Capture Help Watch Refresh Lite Dark elasticity

TIMEBASE 50us/div

TRIGGER Rise Fall

FFT Single Avg Rect Gauss B-H

ChA 4V/div TIME TRIG FREQ

ChB 4V/div TIME TRIG FREQ

ChC 4V/div TIME TRIG FREQ

ChD 4V/div TIME TRIG FREQ

t:	[50us/div]		
A:	[4V/div] 4.74 Vrms	81.36 kHz	
B:	[4V/div] 4.70 Vrms	83.17 kHz	
C:	[4V/div] 4.85 Vrms	173.4 kHz	
D:	[4V/div] 4.76 Vrms	0 Hz	

user manual on Canvas

<http://ece-emonal.engr.rutgers.edu/>



Multiplexer function implemented on the Emona board

User: orfanidis2 - Uid: 56

7/31/2020, 1:56:19 PM

AND-OR implementation




$$Z = S'A + SB$$

  

user manual on Canvas

<http://ece-emon1.engr.rutgers.edu/>

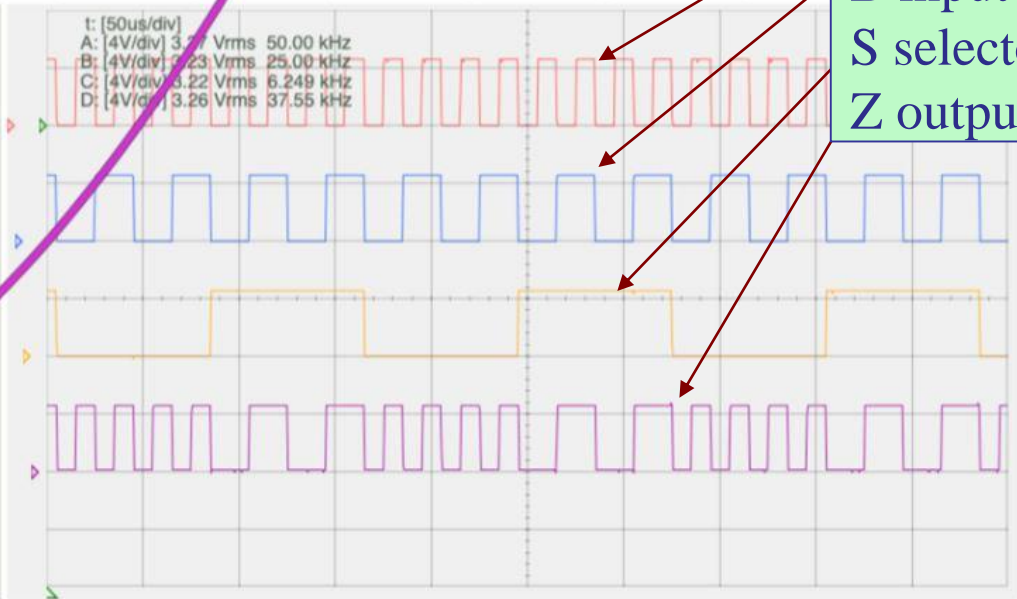
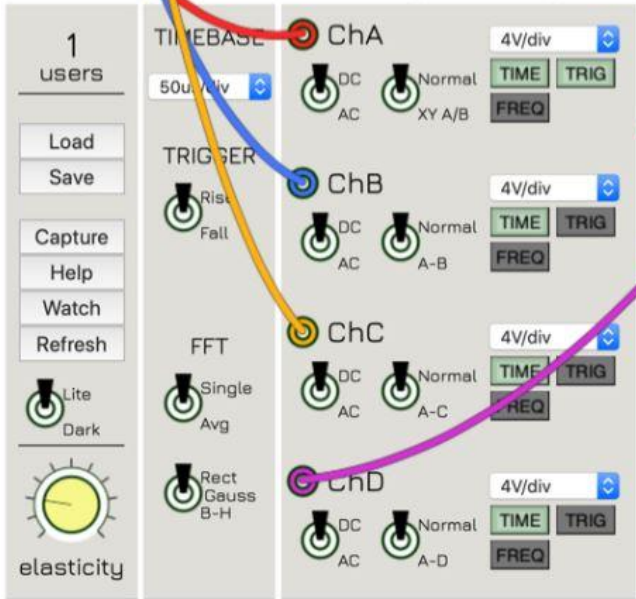
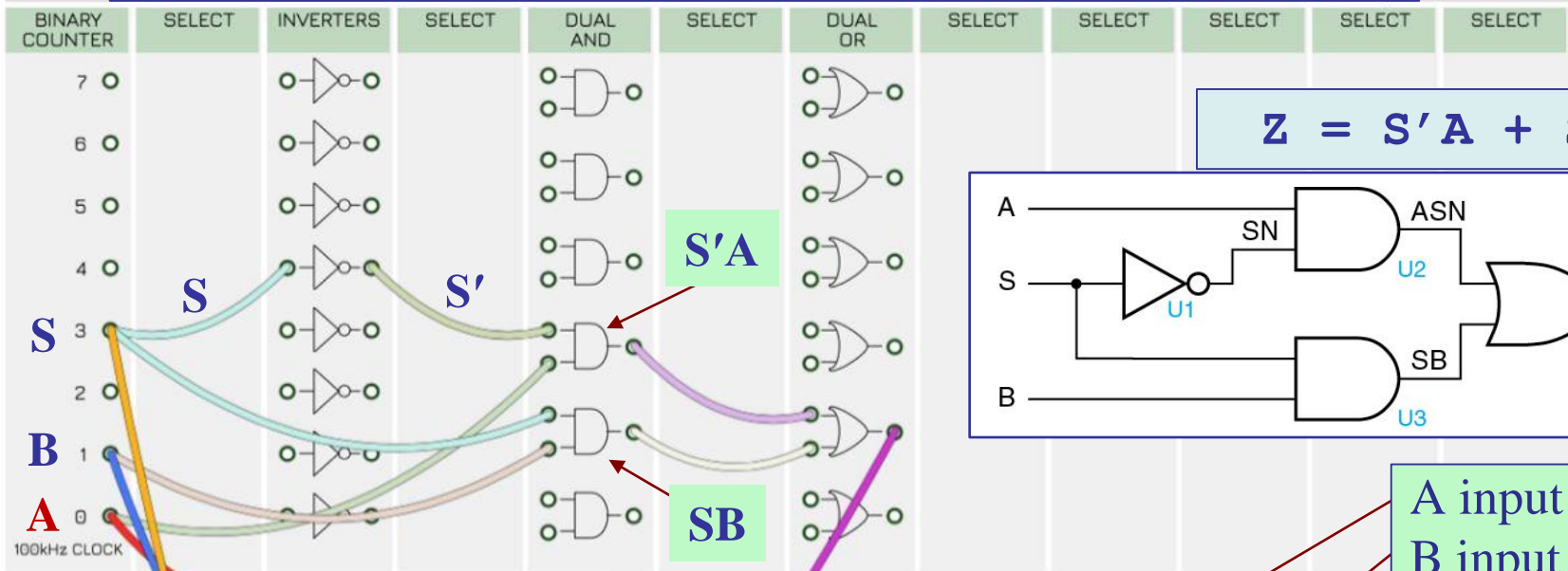
Multiplexer function implemented on the Emona board



user manual on Canvas

<http://ece-emonal.engr.rutgers.edu/>

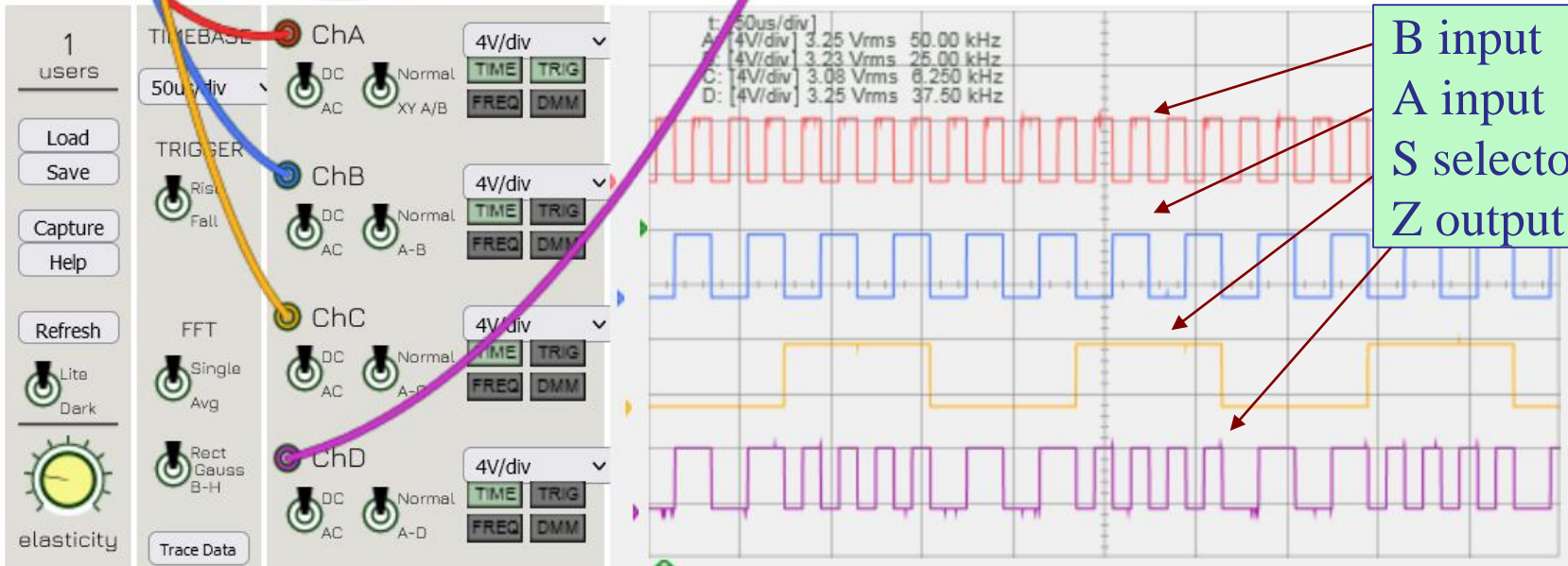 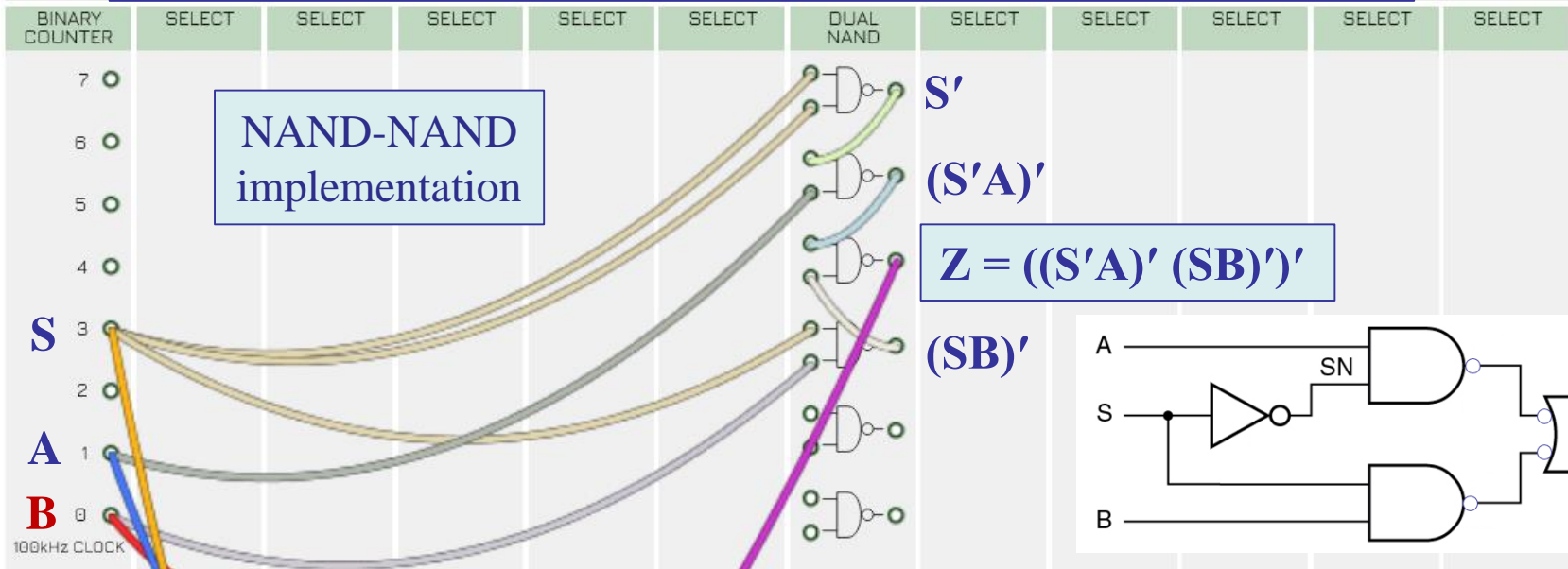Multiplexer function implemented on the Emona board




user manual on Canvas

<http://ece-emonal.engr.rutgers.edu/>

Moore's law – data fitting

 CPU Transistor Counts 1971-2008 & Moore's Law




Moore's law

fitted model $f(t) = b 2^{a(t-t_1)}$

$$\log_2 f(t) = \log_2 b + a(t - t_1)$$

yi	ti
2.300e+003	1971
2.500e+003	1972
4.500e+003	1974
2.900e+004	1979
1.340e+005	1982
2.750e+005	1985
1.200e+006	1989
3.100e+006	1993
4.300e+006	1996
7.500e+006	1997
8.800e+006	1997
9.500e+006	1999
2.130e+007	1999
2.200e+007	1999
4.200e+007	2000
5.430e+007	2003
1.059e+008	2003
2.200e+008	2003
5.920e+008	2004
2.410e+008	2006
2.910e+008	2006
5.820e+008	2006
6.810e+008	2006
7.890e+008	2007
1.700e+009	2006
2.000e+009	2008

 

```

Y = load('transistor_count.dat'); % MATLAB textbook
y = Y(:,1); t = Y(:,2);
t1 = t(1); % t1 = 1971
p = polyfit(t-t1, log2(y), 1);
% p =
% 0.5138 10.5889 % b = 2^p(2) = 1.5402e+003
f = 2.^(polyval(p,t-t1));
semilogy(t,f,'r-', t,y,'b.', 'markersize',18)

```

should be 0.5
according to
Moore's law

fitted model:

$$f(t) = b * 2.^{(a*(t-t1))} = 2.^{(a*(t-t1)+\log_2(b))};$$

$$\% a = p(1), \log_2(b) = p(2) \rightarrow b = 2^{(p(2))}$$

$$\% a = 0.5139, b = 1.5402e+03$$