

Rutgers University  
School of Engineering

Fall 2022

332:231 – Digital Logic Design

Sophocles J. Orfanidis  
ECE Department  
orfanidi@rutgers.edu

Unit 3 – Combinational Circuits


## Course Topics

1. Introduction to DLD, Verilog HDL, MATLAB/Simulink
2. Number systems
- 3. Analysis and synthesis of combinational circuits
4. Decoders/encoders, multiplexers/demultiplexers
5. Arithmetic systems, comparators, adders, multipliers
6. Sequential circuits, latches, flip-flops
7. Registers, shift registers, counters, LFSRs
8. Finite state machines, analysis and synthesis

**Text:** J. F. Wakerly, *Digital Design Principles and Practices*, 5/e, Pearson, 2018  
additional references on Canvas Files > References
 
## Analysis and Synthesis of Combinational Circuits

**Analysis Problem:** Given a combinational circuit made up of logic gates, determine the output  $F$  as a function of the input variables,  $X, Y, Z, \dots$



**Synthesis/Design Problem:** Given a combinational circuit defined by its I/O mapping,  $F = f(X, Y, Z, \dots)$ , typically stated as a truth table, synthesize the circuit with logic gates, preferably using the minimum number of gates, as well as trying to minimize propagation delays.

**Unit-3 Contents:** (current reading:, Wakerly Chapter 3)

1. Boolean algebra, axioms, theorems, properties
2. Standard logic gates, AND, OR, NOT, NAND, NOR, XOR, XNOR
3. Operator precedence ( $\cdot$  has higher precedence than  $+$ )
4. Duality
5. One-, two-, and three-variable theorems and their duals
6. De Morgan's theorems, De Morgan duality
7. De Morgan's theorems for NAND/NOR and AND/OR gates
8. NAND and NOR universal gates
9. NAND-NAND and NOR-NOR implementations
10. Bubble-to-bubble transformations, bubble-pushing operations
11. Proofs using truth tables, or using the basic theorems
12. Algebraic simplification of logic expressions

## Contents, continued:

13. Combinational circuit synthesis from truth table – example
14. Simulink implementations, exporting Verilog code
15. Standard representations of combinational circuits
16. Canonical minterm/SOP and maxterm/POS representations
17. Combinational circuit analysis – examples
18. Combinational circuit synthesis – examples
19. Combinational circuit minimization – Karnaugh maps
20. Timing hazards

# 1. Boolean Algebra, Axioms, Theorems, Properties

**Boolean algebra**, or **switching algebra**, is a branch of mathematical logic in which variables take only two values:

**TRUE, FALSE**, or, alternatively, **1, 0**, or, **HIGH, LOW**

It was invented by George Boole and its relevance to electrical engineering originated with Claude Shannon. See the Wikipedia resources below.

[George Boole](#)

[Claude Shannon](#)

The algebraic system is defined by certain axioms involving the **AND, OR**, and **NOT** operations and the constants **0,1**.

but see also, [Fuzzy Logic](#), in which TRUE is relative in the range (0,1]

The **AND**, **OR**, and **NOT** operations between any two Boolean variables  $X, Y$  are denoted by the dot  $\cdot$  and plus  $+$  operations, and by prime  $'$  for the complement or inverse,

$$\text{AND}(X, Y) = X \cdot Y = \text{logical AND}$$

$$\text{OR}(X, Y) = X + Y = \text{logical OR}$$

$$\text{NOT}(X) = X' = \text{logical NOT, or complement, or inverse}$$

Alternative notations are those used in computer languages, such as MATLAB and Verilog, using the symbols, **&** **|** **~**

$$\text{AND}(X, Y) = X \& Y = \text{logical AND}$$

$$\text{OR}(X, Y) = X | Y = \text{logical OR}$$

$$\text{NOT}(X) = \sim X = \text{logical NOT, or complement, or inverse}$$

NOT is also denoted by an overbar, **NOT**( $X$ ) =  $\overline{X}$

Also, the dot,  $\cdot$ , is often omitted in AND operations, provided it would not cause an ambiguity in the name of the variable,

for example, if A,B,C are **three** distinct variables, then we can write,

$$A \cdot B \cdot C = ABC$$

On the other hand, if AB and C are **two** distinct variables, then, it would be better to use the dot to avoid ambiguity, that is, write,


$$AB \cdot C$$

or, use parentheses, (AB)C, instead of the more ambiguous ABC




## 2. Standard logic gates


## AND, OR, and NOT operations

 

X	Y	$X \cdot Y$
0	0	0
0	1	0
1	0	0
1	1	1

 


X	Y	$X + Y$
0	0	0
0	1	1
1	0	1
1	1	1

 


X	$X'$
0	1
1	0

## 2. Standard logic gates

## NAND and NOR operations

 

		AND	NAND
X	Y	$X \cdot Y$	$(X \cdot Y)'$
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

 


		OR	NOR
X	Y	$X+Y$	$(X+Y)'$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

## 2. Standard logic gates


## XOR and XNOR operations

exclusive OR

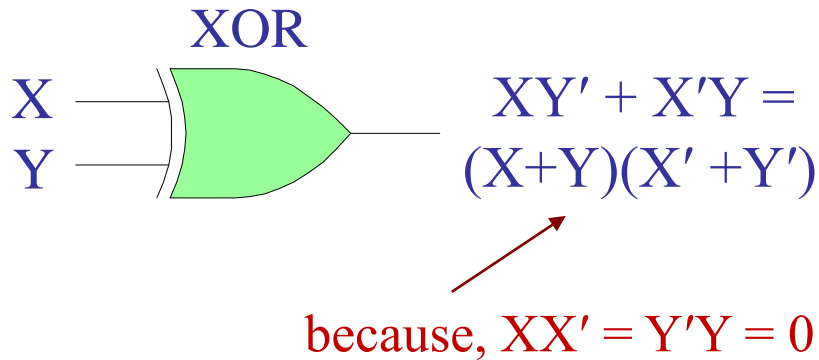

XOR

X	Y	$XY' + X'Y$
0	0	0
0	1	1
1	0	1
1	1	0

 

XNOR

X	Y	$XY + X'Y'$
0	0	1
0	1	0
1	0	0
1	1	1

$(XY' + X'Y)' = XY + X'Y'$  from De Morgan

useful for testing equality

### 3. Operator precedence

**Note:** As in programming languages, “multiplication”, or AND operation,  $\cdot$ , has higher precedence than “addition”, or OR operation,  $+$

e.g.,  $A \cdot B + C \cdot D = (A \cdot B) + (C \cdot D)$

but, use of parentheses is always recommended.

More generally, the **NOT** operation has higher precedence than **AND** and **OR**.

MATLAB has similar order of precedence, from higher to lower:

$\sim$ ,  $\&$ ,  $|$

## 4. Duality

Every relationship, axiom, equation, or theorem among Boolean variables  $X, Y, \dots$ , and constants 0 and 1, has a **dual** obtained by interchanging the roles of the AND and the OR operations (i.e., interchanging,  $\cdot$  and  $+$  ), while also interchanging 0 and 1.

The dual and original relationships are not necessarily equivalent to each other, but they are both separately valid.

For example, the basic axioms relating 0 and 1 (TRUE and FALSE) come in **dual** pairs:

<u>AND</u>	<u>OR</u>
$0 \cdot 0 = 0$	$1 + 1 = 1$
$1 \cdot 1 = 1$	$0 + 0 = 0$
$0 \cdot 1 = 0$	$1 + 0 = 1$
$1 \cdot 0 = 0$	$0 + 1 = 1$

## 5. Boolean algebra theorems and their duals

### one-variable theorems and their duals:

$$X + 0 = X$$

$$X + 1 = 1$$

$$X + X = X$$

$$X + X' = 1$$

$$(X')' = X$$

$$X \cdot 1 = X$$

$$X \cdot 0 = 0$$

$$X \cdot X = X$$

$$X \cdot X' = 0$$

(identities)

(null elements)

(idempotency)

(complements)

(involution)

## two-variable and three-variable theorems and their duals

$X + Y = Y + X$		(commutative)
$(X + Y) + Z = X + (Y + Z)$		(associative)
$X \cdot A + X \cdot B = X \cdot (A + B)$		(distributive)
$X + X \cdot A = X$		(covering)
$X \cdot A + X \cdot A' = X$	consensus term ↓	(combining)
$X \cdot A + X' \cdot B = X \cdot A + X' \cdot B + A \cdot B$		(consensus theorem)

$X \cdot Y = Y \cdot X$		(commutative)
$(X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$		(associative)
$(X + A) \cdot (X + B) = X + (A \cdot B)$		(distributive)
$X \cdot (X + A) = X$		(covering)
$(X + A) \cdot (X + A') = X$	consensus term ↓	(combining)
$(X + A) \cdot (X' + B) = (X + A) \cdot (X' + B) \cdot (A + B)$		(consensus theorem)

**duals**



see Wakerly/Table 3-3 for  $n$ -variable theorems and their duals

## Boole/Shannon expansion theorem:

$$F(X,Y,Z) = X \cdot F(1,Y,Z) + X' \cdot F(0,Y,Z)$$

dual



$$F(X,Y,Z) = [X + F(0,Y,Z)] \cdot [X' + F(1,Y,Z)]$$

## Example:

$$F(X,Y,Z) = X \cdot Y + Y \cdot Z + Z \cdot X$$

$$F(1,Y,Z) = Y + Y \cdot Z + Z = Y + Z$$

$$F(0,Y,Z) = Y \cdot Z$$

$$F(X,Y,Z) = X \cdot F(1,Y,Z) + X' \cdot F(0,Y,Z) = X \cdot (Y+Z) + X' \cdot (Y \cdot Z)$$

$$\begin{aligned} F(X,Y,Z) &= [X + F(0,Y,Z)] \cdot [X' + F(1,Y,Z)] = \\ &= [X + (Y \cdot Z)] \cdot [X' + Y + Z] \end{aligned}$$



additional clarification & direct derivation:

$$\begin{aligned} F(X,Y,Z) &= XY + YZ + ZX \quad \text{note: } X + X' = 1 \\ &= XY + (X + X')YZ + ZX \\ &= X(Y + YZ + Z) + X'YZ \end{aligned}$$

$$F(1,Y,Z) = Y + YZ + Z = Y + Z$$

$$F(0,Y,Z) = YZ$$

$$\begin{aligned} Y + YZ + Z &= Y + YZ + YZ + Z = \\ &= Y(1 + Z) + (Y + 1)Z = \\ &= Y + Z \end{aligned}$$

## 6. De Morgan's theorems, De Morgan duality

[De Morgan's laws - Wikipedia](#)

$$(X \cdot Y)' = X' + Y' \quad (\text{NAND})$$

$$(X + Y)' = X' \cdot Y' \quad (\text{NOR})$$

$$X \cdot Y = (X' + Y')' \quad (\text{AND})$$

$$X + Y = (X' \cdot Y')' \quad (\text{OR})$$

### Generalized De Morgan theorems – De Morgan duality:

The **complement** of an expression is the **dual** of the expression with all variables replaced by their complements, or, equivalently, the expression is equal to the **complement of its dual** with all variables complemented,

$$F(X, Y, Z, \dots)' = F_{\text{dual}}(X', Y', Z', \dots)$$

$$F(X, Y, Z, \dots) = F_{\text{dual}}(X', Y', Z', \dots)'$$

## De Morgan examples

$$[X + (Y \cdot Z)]' = X' \cdot (Y' + Z')$$

$$[X \cdot (Y + Z)]' = X' + (Y' \cdot Z')$$

$$(X + Y + Z)' = X' \cdot Y' \cdot Z'$$

$$(X \cdot Y \cdot Z)' = X' + Y' + Z'$$

## De Morgan duality:

$$F(X,Y,Z) = X + (Y \cdot Z), \quad F_{\text{dual}}(X,Y, Z) = X \cdot (Y + Z)$$

$$F(X,Y,Z)' = [X + (Y \cdot Z)]' = X' \cdot (Y' + Z') = F_{\text{dual}}(X',Y', Z')$$


---

$$F(X,Y,Z) = X \cdot (Y + Z), \quad F_{\text{dual}}(X,Y, Z) = X + (Y \cdot Z)$$


$$F(X,Y,Z)' = [X \cdot (Y + Z)]' = X' + (Y' \cdot Z') = F_{\text{dual}}(X',Y', Z')$$

Using De Morgan's theorems, show that,  $XOR' = XNOR$ , defined by,
 
$$XOR(X,Y) = X \cdot Y' + X' \cdot Y = (X + Y) \cdot (X' + Y')$$


 
$$XNOR(X,Y) = X \cdot Y + X' \cdot Y' = (X + Y') \cdot (X' + Y)$$



$$\begin{aligned} XOR' &= (X \cdot Y' + X' \cdot Y)' \\ &= (X \cdot Y')' \cdot (X' \cdot Y)' \\ &= (X' + Y) \cdot (X + Y') \\ &= X \cdot Y + X' \cdot Y' \\ &= XNOR \end{aligned}$$

note, XOR, XNOR  
are invariant under  
the substitutions:

$$\begin{aligned} X &\rightarrow X' \\ Y &\rightarrow Y' \end{aligned}$$


or more simply, using De Morgan duality:

$$XOR_{\text{dual}}(X,Y) = (X + Y') \cdot (X' + Y)$$


$$XOR(X,Y)' = XOR_{\text{dual}}(X',Y') = (X' + Y) \cdot (X + Y') = XNOR(X,Y)$$
 
## 7. De Morgan's theorems for NAND and NOR gates


$$(X \cdot Y)' = X' + Y'$$
$$\text{NAND}(X, Y) = \text{OR}(X', Y')$$




≡

 
 
$$(X + Y)' = X' \cdot Y'$$
$$\text{NOR}(X, Y) = \text{AND}(X', Y')$$




≡

 

 
# 7. De Morgan's theorems for AND and OR gates


$$X \cdot Y = (X' + Y)'$$
$$\text{AND}(X, Y) = \text{NOR}(X', Y')$$




≡

 
 
$$X + Y = (X' \cdot Y)'$$
$$\text{OR}(X, Y) = \text{NAND}(X', Y')$$



≡





 


## De Morgan's laws for sets



[De Morgan's laws - Wikipedia](#)

The Boolean algebra equivalents of the AND, OR, and NOT operations in the **theory of sets** are the **Union** and **Intersection** of two sets, and the **Complement** of a set.

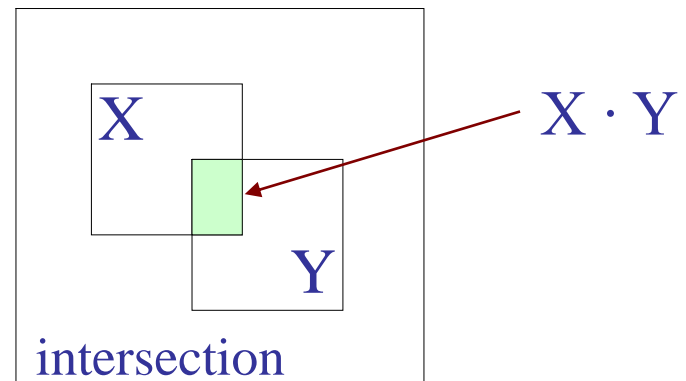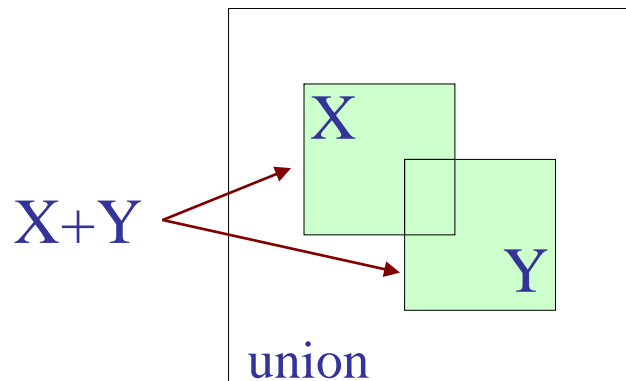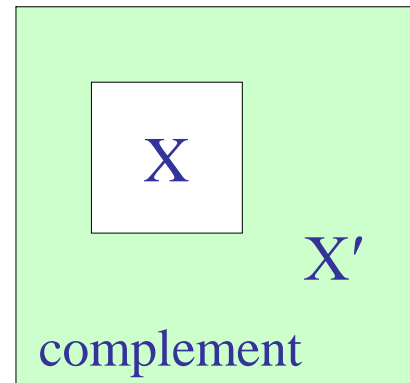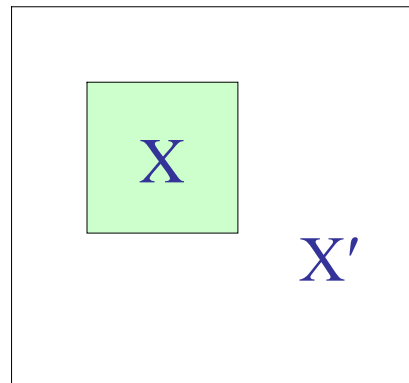
 
They can be visualized with **Venn diagrams**.




# De Morgan's laws for sets

  

$X \cdot Y$

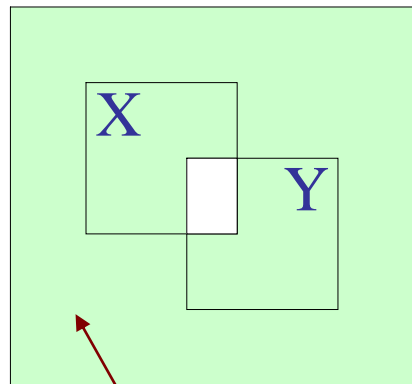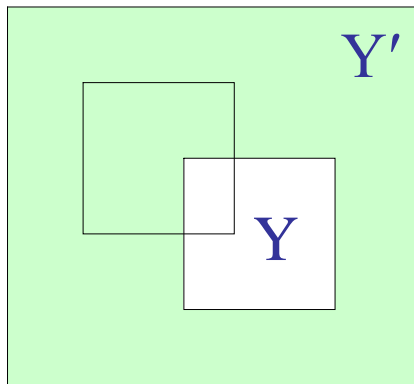

$(X \cdot Y)'$


 


$X' + Y'$



$(X \cdot Y)' = X' + Y'$




# De Morgan's laws for sets

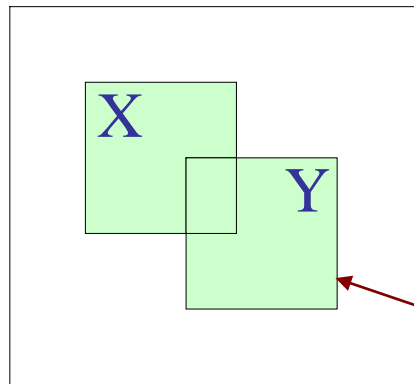 

$X + Y$

  

$(X + Y)'$

 


$X' \cdot Y'$



$(X + Y)' = X' \cdot Y'$
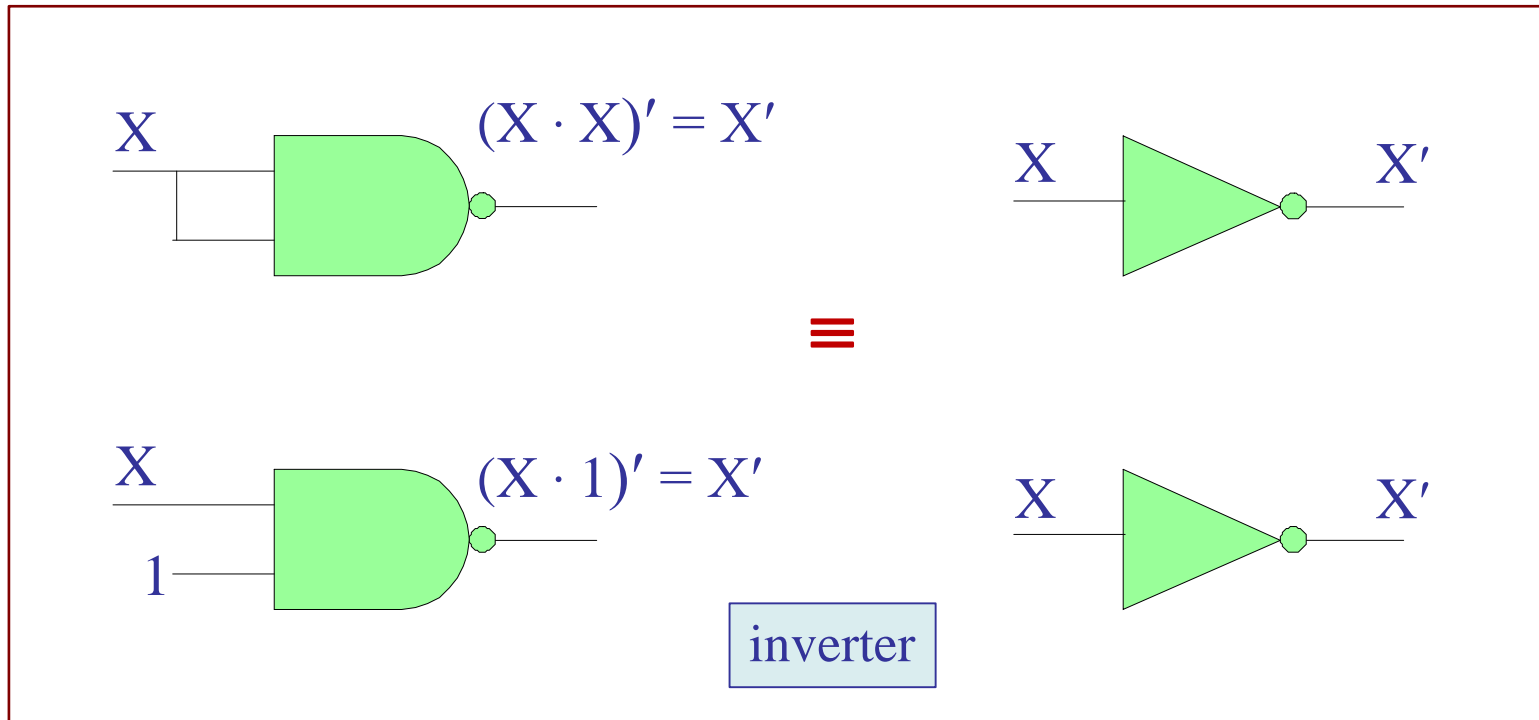
## 8. NAND and NOR universal gates



NAND and NOR gates are **universal gates** in the sense they can be used to build any other type of gate – they are preferred in all IC logic families because they are fast, economical, and easy to fabricate.



# 8. NAND and NOR universal gates

 
 


≡

 
 


inverter

# 8. NAND and NOR universal gates

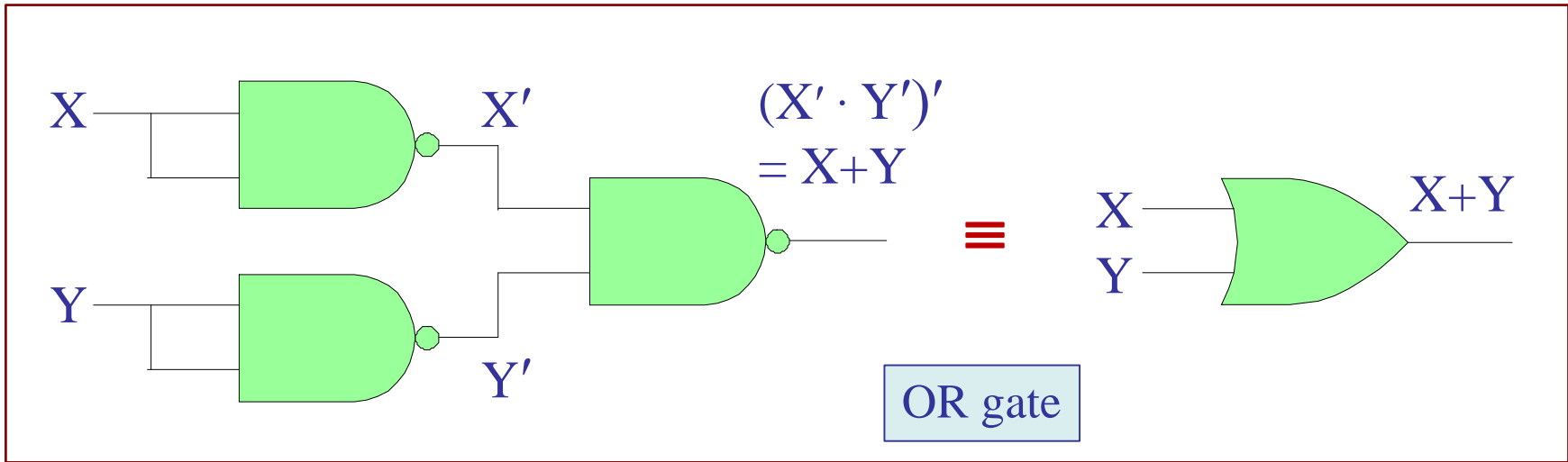 


# 8. NAND and NOR universal gates

  


## 9. NAND–NAND and NOR–NOR implementations
 
## 10. Bubble-to-bubble transformations, bubble pushing operations




AND – OR  
implementation

 




De Morgan's theorem

$$(X \cdot Y)' = X' + Y'$$

 


NAND – NAND  
implementation

   NAND-NAND realizations  
 bubble-to-bubble transformations  
 bubble pushing operations




more examples from Wakerly

 NAND–NAND realizations  
bubble-to-bubble transformations  
bubble pushing operations




sum-of-products (SOP) form


bubbles cancel on same line

 

NAND gate

 


De Morgan equivalents

 




more examples from Wakerly

 NOR-NOR realizations  
bubble-to-bubble transformations  
bubble pushing operations




product-of-sums (POS) form


bubbles cancel on same line

 

NOR gate

 

De Morgan equivalents




 


NOR gates

# more examples from Wakerly

    - (a) original
- (b) non-standard gate
- (c) eliminate non-standard gate
- (d) preferred inverter placement


NAND-NOR realizations  
bubble-to-bubble transformations  
bubble pushing operations



more examples from Wakerly

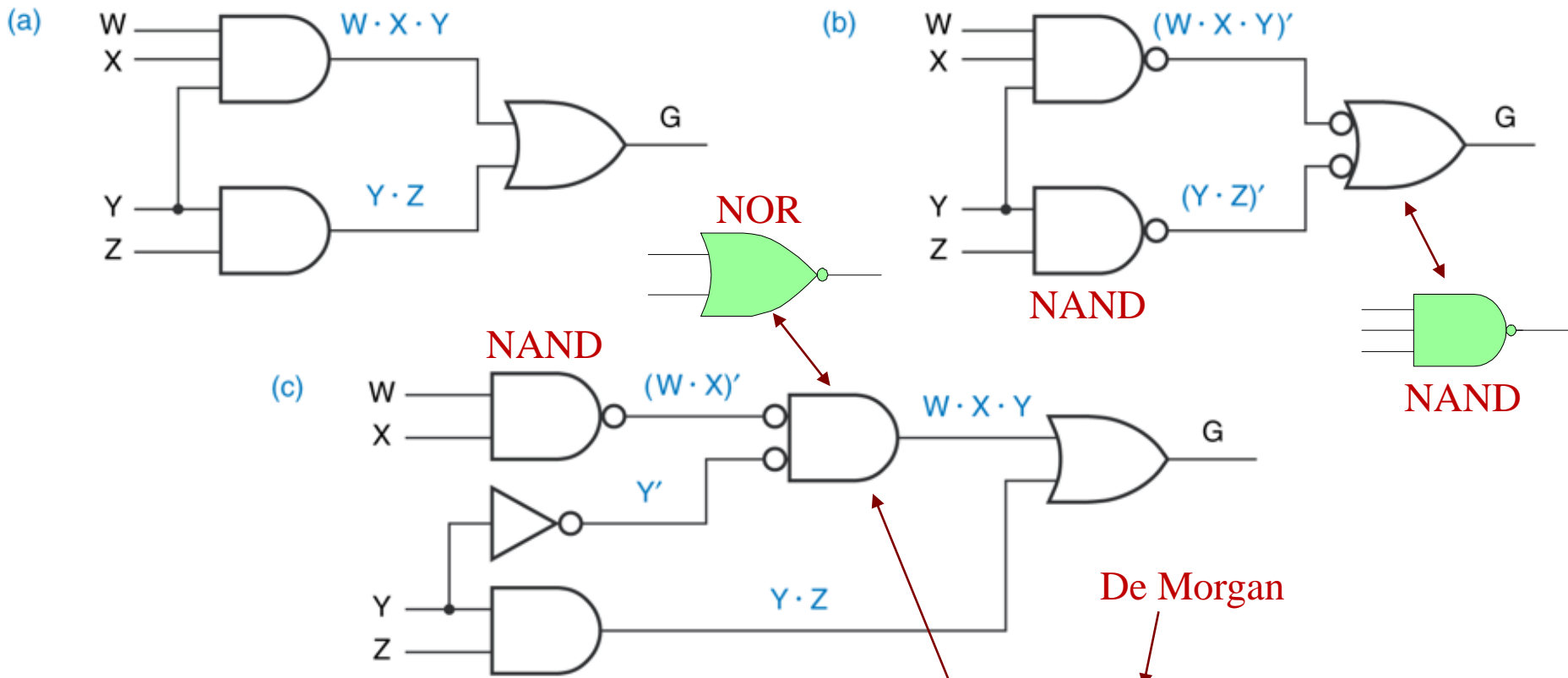- (a) two-level AND-OR
- (b) two-level NAND-NAND
- (c) 2-input gates only

NAND-NAND realizations  
bubble-to-bubble transformations  
bubble pushing operations



$$G = W \cdot X \cdot Y + Y \cdot Z$$

$$W \cdot X \cdot Y = (W \cdot X)'' \cdot (Y)'' = ((WX)' + Y')'$$

## 11. Boolean theorem proofs

Proofs of the various Boolean theorems can be given by simply verifying the **truth tables** of the two sides of the expressions.

For example, to prove the **covering** theorem,  $X + X \cdot Y = X$ , we may evaluate both sides of the expression for all possible values of the Boolean variables X,Y, making a truth table for each side:

X	Y	$X \cdot Y$	$X + X \cdot Y$
0	0	0	0
0	1	0	0
1	0	0	1
1	1	1	1

← equal →

Alternative analytical proof:

$$\begin{aligned} X + X \cdot Y &= X \cdot (1+Y) \\ &= X \cdot 1 \\ &= X \end{aligned}$$

note,  $1+Y = 1$

As another example, in order to prove the **distributive** theorem,

$$X + Y \cdot Z = (X + Y) \cdot (X + Z)$$

we construct the truth tables for each side:

X	Y	Z	Y·Z	X + Y·Z	X + Y	X + Z	(X + Y) · (X + Z)
0	0	0	0	0	0	0	0
0	0	1	0	0	0	1	0
0	1	0	0	0	1	0	0
0	1	1	1	1	1	1	1
1	0	0	0	1	1	1	1
1	0	1	0	1	1	1	1
1	1	0	0	1	1	1	1
1	1	1	1	1	1	1	1



3-bit binary pattern

Analytical proof of the **distributive** theorem,

$$X + Y \cdot Z = (X + Y) \cdot (X + Z)$$

using the covering theorem,  $A + A \cdot B = A$ , and the idempotent theorem,  $A \cdot A = A$ ,

$$\begin{aligned}(X + Y) \cdot (X + Z) &= X \cdot X + X \cdot Y + X \cdot Z + Y \cdot Z \\ &= X + X \cdot Y + X \cdot Z + Y \cdot Z \\ &= \underbrace{X + X \cdot Y}_{\searrow} + X \cdot Z + Y \cdot Z \\ &= X + \underbrace{X \cdot Z}_{\searrow} + Y \cdot Z \\ &= X + Y \cdot Z\end{aligned}$$

MATLAB proof of the **distributive** theorem,







$$X + Y \cdot Z = (X + Y) \cdot (X + Z)$$

**MATLAB code:**

```
[X,Y,Z] = a2d(0:7,3);           % generate inputs
F1 = X | (Y&Z);                 % left-hand side
F2 = (X|Y) & (X|Z);            % right-hand side
[X,Y,Z,F1,F2]                  % print columns
```

X	Y	Z	F1	F2
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	1	1
1	0	0	1	1
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

      Set-theoretic proof of the **distributive** theorem,  $X + Y \cdot Z = (X + Y) \cdot (X + Z)$





Proofs of the **consensus** theorems:

note:  $X + X' = 1$




$$\begin{aligned} X \cdot A + X' \cdot B + A \cdot B &= X \cdot A + X' \cdot B + (X + X') \cdot A \cdot B \\ &= X \cdot A + X \cdot A \cdot B + X' \cdot B + X' \cdot A \cdot B \\ &= X \cdot A \cdot (1+B) + X' \cdot B \cdot (1+A) \\ &= X \cdot A \cdot 1 + X' \cdot B \cdot 1 \\ &= X \cdot A + X' \cdot B \end{aligned}$$



dual ↓

$$\begin{aligned} (X + A) (X' + B) (A+B) &= (X X' + XB + X' A + AB)(A+B) \\ &= (XB + X' A + AB)(A+B) \\ &= XB(A+B) + X' A(A+B) + AB(A+B) \\ \text{note: } AA = A \quad \longrightarrow &= X(BA+BB) + X' (AA+AB) + AAB+BBA \\ &= X(BA+B) + X' (A+AB) + AB+BA \\ \text{note: } A + 1 = 1 \quad \longrightarrow &= XB(A+1) + X' A(1+B) + AB \\ &= XB + X' A + AB \\ \text{note: } XX' = 0 \quad \longrightarrow &= X X' + XB + X' A + AB \\ &= (X+A) \cdot (X' +B) \end{aligned}$$

 
Set-theoretic proof  
of the **consensus** theorem





$$X \cdot A$$

  

$$X' \cdot B$$

 

$$A \cdot B$$

  

$$X \cdot A + X' \cdot B + A \cdot B = X \cdot A + X' \cdot B$$

## 12. Algebraic simplification of combinational logic expressions

Next, we discuss a few examples of using the Boolean properties and theorems to simplify logic expressions.

**Simplification** leads to more efficient implementations requiring fewer logic gates.

Although, the theorems can always be used to simplify an expression, a much better and easier approach is through the use of **Karnaugh maps (K-maps)** – they will be discussed in detail later on.

An additional requirement in designing logic circuits is the minimization of propagation **delays** through the various stages (or, levels) of the realization.

It should be noted, however, that minimizing the number of logic gates does not necessarily guarantee shorter propagation delays.

## Nomenclature

<b>literal:</b>	a single Boolean variable, e.g., X
<b>product term:</b>	a product of variables, e.g., XZ
<b>sum term:</b>	a sum of variables, e.g., Y+Z
<b>minterm:</b>	a product of input variables corresponding to a row in truth table e.g., XY'Z, corresponding to row 101 = 5
<b>canonical SOP:</b>	canonical minterm sum-of-products, e.g., $\Sigma_{X,Y,Z}(0,3,4,6,7)$
<b>minterm list :</b>	list of row numbers that appear in a canonical SOP
<b>maxterm:</b>	a sum of input variables, e.g., X+Y'+Z, corresponding to the <b>complement</b> of a row in the truth table
<b>canonical POS:</b>	canonical maxterm product-of-sums, e.g., $\Pi_{X,Y,Z}(1,2,5)$
<b>maxterm list :</b>	list of row numbers that appear in a canonical POS

to be explained further later on

## Nomenclature

**implicant:** a minterm or sum of minterms appearing in a function  $F$ , if an implicant evaluates to 1, then so does  $F$  as a whole, i.e., if, **implicant=1**, then it implies,  **$F=1$**

**prime implicant:** a simplified implicant that cannot be combined into another implicant that has fewer number of literals.

**covers:** all implicants that account for all possible evaluations of the function into  $F=1$  (i.e., all the 1's in a Karnaugh map).

**essential prime implicant:** a prime implicant that contains an  $F=1$  minterm that is not included in any other prime implicant, all essential prime implicants **must be included** in the cover of the function.

In addition to the essential PIs, it may be necessary to include possible non-essential PIs in order to achieve a complete cover, (if there are several such possibilities, one could choose the one that has the smallest number of literals.

## Nomenclature

### Sum-of-Products (SOP) rule:

F is the **sum** of those minterms that correspond to the values **F=1** in the truth table

Notation:  $F = \Sigma(\text{of the } F=1 \text{ minterms}) = \text{canonical sum-of-products}$   
as indicated by the **row numbers** in the truth table

### Product-of-Sums (POS) rule:

F is the **product** of those maxterms that correspond to the values **F=0** (or,  $F' = 1$ ) in the truth table

Notation:  $F = \Pi(\text{of the } F=0 \text{ maxterms}) = \text{canonical product-of-sums}$   
as indicated by the **row numbers** in the truth table

# Truth-table representations with minterms or maxterms

## 3-variable logic function $F(X,Y,Z)$

row	X	Y	Z	F	minterms	maxterms
0	0	0	0	$F(0,0,0)$	$X' \cdot Y' \cdot Z'$	$X + Y + Z$
1	0	0	1	$F(0,0,1)$	$X' \cdot Y' \cdot Z$	$X + Y + Z'$
2	0	1	0	$F(0,1,0)$	$X' \cdot Y \cdot Z'$	$X + Y' + Z$
3	0	1	1	$F(0,1,1)$	$X' \cdot Y \cdot Z$	$X + Y' + Z'$
4	1	0	0	$F(1,0,0)$	$X \cdot Y' \cdot Z'$	$X' + Y + Z$
5	1	0	1	$F(1,0,1)$	$X \cdot Y' \cdot Z$	$X' + Y + Z'$
6	1	1	0	$F(1,1,0)$	$X \cdot Y \cdot Z'$	$X' + Y' + Z$
7	1	1	1	$F(1,1,1)$	$X \cdot Y \cdot Z$	$X' + Y' + Z'$

  
 complements of each other  
 by De Morgan

## 12. Algebraic simplification of combinational logic expressions

**Example 1:** Prove the dual results,

$$X + X' \cdot Y = X + Y$$

$$X \cdot (X' + Y) = X \cdot Y$$

**Proof:** Using,  $A + A' = 1$ , and the distributive property:

$$A + B \cdot C = (A+B) \cdot (A+C)$$

with,  $A = X$ ,  $B = X'$ ,  $C = Y$ , we have,

$$X + X' \cdot Y = (X+X') \cdot (X+Y) = 1 \cdot (X+Y) = X+Y$$

For the dual, we simply multiply the terms out,

$$X \cdot (X' + Y) = X \cdot X' + X \cdot Y = 0 + X \cdot Y = X \cdot Y$$





**Example 2:** Truth table of multiplexer function from Unit-1

$$\begin{aligned}
 Z &= S' \cdot A \cdot B' + S' \cdot A \cdot B + S \cdot A' \cdot B + S \cdot A \cdot B \\
 &= S' \cdot A \cdot (B' + B) + S \cdot (A' + A) \cdot B \\
 &= S' \cdot A \cdot 1 + S \cdot 1 \cdot B \\
 &= S' \cdot A + S \cdot B
 \end{aligned}$$

minterm SOP  
 $Z = \sum_{S,A,B}(2,3,5,7)$

rows	S	A	B	Z
0	0	0	0	0
1	0	0	1	0
<b><math>S' \cdot A \cdot B'</math></b>	0	1	0	1
<b><math>S' \cdot A \cdot B</math></b>	0	1	1	1
4	1	0	0	0
<b><math>S \cdot A' \cdot B</math></b>	1	0	1	1
6	1	1	0	0
<b><math>S \cdot A \cdot B</math></b>	1	1	1	1

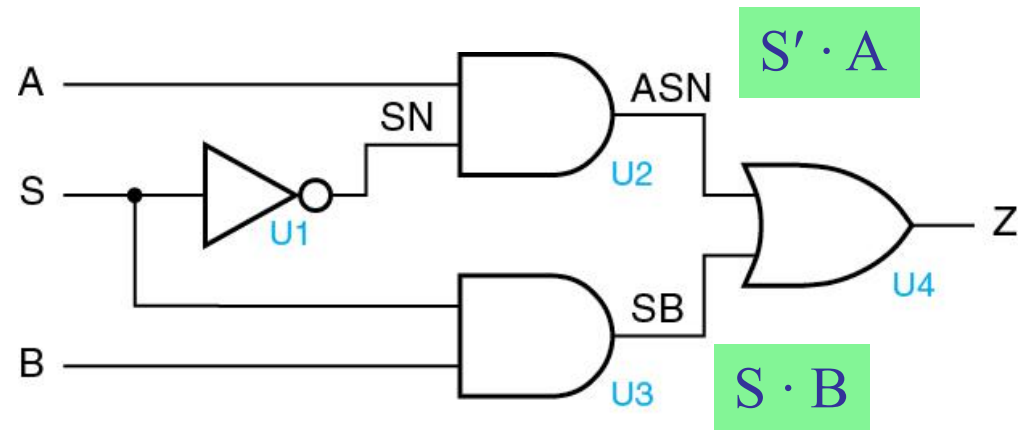 

**Example 2:** Truth table of multiplexer function from Unit-1

$$Z' = S' \cdot A' \cdot B' + S' \cdot A' \cdot B + S \cdot A' \cdot B' + S \cdot A \cdot B'$$

De Morgan

$$Z = (S+A+B) \cdot (S+A+B') \cdot (S'+A+B) \cdot (S'+A'+B)$$

combining

$$= (S+A) \cdot (S'+B) = S' \cdot A + S \cdot B + A \cdot B$$


consensus

$$= S' \cdot A + S \cdot B$$

	S	A	B	Z	Z'	rows
$S' \cdot A' \cdot B'$	0	0	0	0	1	0
$S' \cdot A' \cdot B$	0	0	1	0	1	1
	0	1	0	1	0	2
	0	1	1	1	0	3
$S \cdot A' \cdot B'$	1	0	0	0	1	4
	1	0	1	1	0	5
$S \cdot A \cdot B'$	1	1	0	0	1	6
	1	1	1	1	0	7

maxterm POS  
 $Z = \Pi_{S,A,B}(0,1,4,6)$

minterm SOP  
 $Z = \Sigma_{S,A,B}(2,3,5,7)$

 


**Example 2:** Truth table of multiplexer function from Unit-1

Karnaugh map (K-map) simplification (to be discussed in detail later on)

$$Z = S' \cdot A \cdot B' + S' \cdot A \cdot B + S \cdot A' \cdot B + S \cdot A \cdot B$$

$$= S' \cdot A + S \cdot B = S' \cdot A + S \cdot B + A \cdot B$$

	S	A	B	Z
	0	0	0	0
	0	0	1	0
$S' \cdot A \cdot B'$	0	1	0	1
$S' \cdot A \cdot B$	0	1	1	1
	1	0	0	0
$S \cdot A' \cdot B$	1	0	1	1
	1	1	0	0
$S \cdot A \cdot B$	1	1	1	1

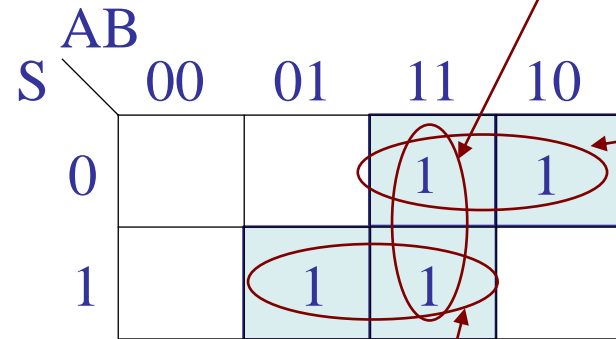

$A \cdot B$  non-essential PI, consensus term

$S' \cdot A$  essential PI

$S \cdot B$  essential PI

blue areas indicate a complete cover

**Example 3:** For the truth table given in **Table 3-5** of the Wakerly text, demonstrate the equivalence of the following expressions for F as a function of the Boolean variables X, Y, Z,

truth table			
X	Y	Z	F
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

$$(1) F = X'Y'Z' + XY'Z' + X'YZ + XYZ + XYZ'$$

$$(2) F = Y'Z' + YZ + XYZ'$$

$$(3) F = Y'Z' + YZ + XZ'$$

$$(4) F = Y'Z' + YZ + XY$$

$$(5) F = Y'Z' + YZ + XZ' + XY$$

$$(6) F = (Y + Z')(X + Y' + Z)$$

$$(7) F = (X + Y + Z')(X + Y' + Z)(X' + Y + Z')$$

minterm SOP  
(sum-of-products)

literals,  
product terms

maxterm POS  
(product-of-sums)

In particular, given (1) use the theorems to demonstrate the equivalence of (2)-(7) to (1).

(1) → (2)

$$\begin{aligned} F &= X'Y'Z' + XY'Z' + X'YZ + XYZ + XYZ' \\ &= (X' + X)Y'Z' + (X' + X)YZ + XYZ' = Y'Z' + YZ + XYZ' \end{aligned}$$

(1) → (4)

$$\begin{aligned} F &= X'Y'Z' + XY'Z' + X'YZ + XYZ + XYZ' \quad \text{duplicated} \\ &= X'Y'Z' + XY'Z' + X'YZ + XYZ + \mathbf{XYZ} + XYZ' \\ &= (X' + X)Y'Z' + (X' + X)YZ + XY(Z + Z') \\ &= Y'Z' + YZ + XY \end{aligned}$$

(1) → (2)

$$\begin{aligned} F &= X'Y'Z' + XY'Z' + X'YZ + XYZ + XYZ' \\ &= (X' + X)Y'Z' + (X' + X)YZ + XYZ' = Y'Z' + YZ + XYZ' \end{aligned}$$

(2) → (3)

distributive

$$X + A \cdot B = (X+A) \cdot (X+B)$$

$$\begin{aligned} F &= Y'Z' + YZ + XYZ' \\ &= (Y' + XY)Z' + YZ = (Y' + X) (Y' + Y) Z' + YZ \\ &= (Y' + X) Z' + YZ = Y'Z' + YZ + XZ' \end{aligned}$$

(2) → (4)

distributive

$$\begin{aligned} F &= Y'Z' + YZ + XYZ' \\ &= Y'Z' + Y(Z + XZ') = Y'Z' + Y(Z + X) (Z + Z') \\ &= Y'Z' + Y(Z + X) = Y'Z' + YZ + XY \end{aligned}$$

(3) → (5)

consensus

$$F = Y'Z' + (YZ + XZ') = Y'Z' + (YZ + XZ' + XY)$$

truth table				
X	Y	Z	F	F'
0	0	0	1	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	0	1
1	1	0	1	0
1	1	1	1	0

justification of Eq.(7)  
from the truth table

$$F = X'Y'Z' + XY'Z' + X'YZ + XYZ + XYZ'$$

minterm SOP for F  
(sum-of-products)

minterm SOP for F'  
(sum-of-products)

maxterm POS for F  
(product-of-sums)

$$F' = X'Y'Z + X'YZ' + XY'Z$$

De Morgan

$$F = (X + Y + Z') (X + Y' + Z) (X' + Y + Z')$$

Eq.(7)

# Karnaugh map examples – 1

(to be fully explained later on)

Previously (in Example 3) we considered the simplification of the truth table function given in **Table 3-5** of the Wakerly text, and demonstrated the equivalence of the following expressions for F as a function of the Boolean variables X, Y, Z,


$$(1) F = X'Y'Z' + XY'Z' + X'YZ + XYZ + XYZ'$$

$$(2) F = Y'Z' + YZ + XZ' \longrightarrow \text{p.64, gate-level realizations}$$

$$(3) F = Y'Z' + YZ + XY$$

truth table

X	Y	Z	F
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

 

blue areas indicate a complete cover

Y'Z' essential PI

XZ'

essential PI YZ

XY

essential PIs, must include either for a complete cover one is essential, the other not



## 12. Algebraic simplification of combinational logic expressions

**Example 4:** For the truth table given below [ref. A. F. Kana, on Canvas], show the equivalence of the following expressions for F as a function of the Boolean variables X, Y, Z,

truth table			
X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$(1) F = X'YZ + XY'Z + XYZ' + XYZ$$

$$(2) F = X'YZ + XY'Z + XY$$

$$(3) F = X'YZ + XZ + XYZ'$$

$$(4) F = YZ + XY'Z + XYZ'$$

$$(5) F = XY + YZ + XZ$$

In particular, given Eq.(1) use the theorems to demonstrate the equivalence of Eqs.(2)-(5) to Eq.(1).

$$\begin{aligned}
 (1) \rightarrow (2) \quad F &= X'YZ + XY'Z + XYZ' + XYZ \\
 &= X'YZ + XY'Z + XY(Z' + Z) = X'YZ + XY'Z + XY
 \end{aligned}$$

$$\begin{aligned}
 (1) \rightarrow (3) \quad F &= X'YZ + XY'Z + XYZ' + XYZ \\
 &= X'YZ + X(Y' + Y)Z + XYZ' = X'YZ + XZ + XYZ'
 \end{aligned}$$

$$\begin{aligned}
 (1) \rightarrow (4) \quad F &= X'YZ + XY'Z + XYZ' + XYZ \\
 &= (X' + X)YZ + XY'Z + XYZ' = YZ + XY'Z + XYZ'
 \end{aligned}$$

$$\begin{aligned}
 (2) \rightarrow (5) \quad F &= X'YZ + XY'Z + XY = X'YZ + X(Y + Y'Z) \\
 &= X'YZ + X(Y + Y')(Y + Z) = X'YZ + X(Y + Z) \\
 &= X'YZ + XY + XZ = Y(X + X'Z) + XZ \\
 &= Y(X + X')(X + Z) + XZ = Y(X + Z) + XZ \\
 &= XY + YZ + XZ
 \end{aligned}$$

(1)  $\rightarrow$  (5) , alternative method,

$$F = X'YZ + XY'Z + XYZ' + XYZ$$

$$= X'YZ + \color{red}{XYZ} + XY'Z + \color{red}{XYZ} + XYZ' + \color{red}{XYZ}$$

$$= (X' + X)YZ + X(Y' + Y)Z + XY(Z' + Z)$$

$$= YZ + XZ + XY$$


duplicate XYZ and  
use the property  
 $A + A + A = A$

**Example 4 – K-map method (to be fully explained later on):** For the truth table given below [ref. A. F. Kana], show the equivalence of the following expressions for F as a function of the Boolean variables X, Y, Z,

truth table			
X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

(1)  $F = X'YZ + XY'Z + XYZ' + XYZ$

(5)  $F = XY + YZ + XZ$

 

blue areas indicate a complete cover

YZ

XY

all three are essential PIs

## 12. Algebraic simplification of combinational logic expressions

**Example 5:** Provide two proofs of the equivalence of the following two expressions:

$$F = X'Y + XY' + XY$$

$$F = X + Y$$

**Method 1:**  $F = X'Y + XY' + XY = X'Y + X(Y' + Y) =$   
 $= X'Y + X = X + Y$  (from Example 1)

**Method 2:**  $F = X'Y + XY' + XY$   
 $= X'Y + XY' + XY + XY =$   
 $= (X' + X)Y + X(Y' + Y)$   
 $= X + Y$

replicate XY  
using the property  
 $A + A = A$

**Example 6:** Show the equivalence of the following two 4-variable expressions [ref. A. F. Kana],

$$F = A'BC'D + A'BCD + ABC'D' + ABC'D + ABCD + ABCD' + \dots \\ + AB'CD + AB'CD'$$

$$F = BD + AB + AC$$

Proof:

$$F = A'BC'D + A'BCD + ABC'D' + ABC'D + ABCD + ABCD' + \dots \\ + AB'CD + AB'CD'$$

$$= A'B(C' + C)D + ABC'D' + AB(C' + C)D + ABCD' + \dots \\ + AB'CD + AB'CD'$$

$$= A'BD + ABC'D' + ABD + ABCD' + AB'CD + AB'CD'$$

$$= (A' + A)BD + AB(C' + C)D' + AB'C(D + D')$$

$$= BD + ABD' + AB'C = B(D + AD') + AB'C$$

$$= B(D + A)(D + D') + AB'C = B(D+A) + AB'C = BD + AB + AB'C$$

$$= BD + A(B + B'C) = BD + A(B + B')(B + C) = BD + A(B + C)$$

$$= BD + AB + AC$$

see next page for simpler K-map method


## Karnaugh map examples – 5

(to be fully explained later on)

Previously (in Example 6), we showed the equivalence of the following two 4-variable expressions [ref. A. F. Kana],

$$F = A'BC'D + A'BCD + ABC'D' + ABC'D + ABCD + ABCD' + AB'CD + AB'CD'$$

$$F = BD + AB + AC$$

 

all three are essential PIs

blue areas indicate a complete cover

implicant example

$$\begin{aligned} \text{if } AB = 1, \text{ then, } A=1, B=1, A'=0, B'=0 \\ F &= C'D' + C'D + CD + CD' \\ &= (C+C')(D+D') = 1 \cdot 1 = 1 \end{aligned}$$

### 13. Combinational circuit truth-table synthesis example

**Example 3, continued:** Previously (p.52), we demonstrated the equivalence of the following expressions for F as a function of the Boolean variables X, Y, Z,

$$F = X'Y'Z' + XY'Z' + X'YZ + XYZ + XYZ'$$

$$F = Y'Z' + YZ + XZ'$$

As a first **synthesis** example, we wish to **realize** the second relationship by means of logic gates, and on the **Emona** board, and **simulate** it in MATLAB and Simulink, generate the given **truth table** and a **timing diagram**, and **observe** the input and output signals on a scope, and **plot** them in MATLAB.


The following files are on Canvas Resources, and may be used as templates for future examples:

- table35m.m**, MATLAB m-file for the truth table and plotting
- table35s.slx**, Simulink file,
- table35v.v**, Verilog code generated by Simulink


truth table			
X	Y	Z	F
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1



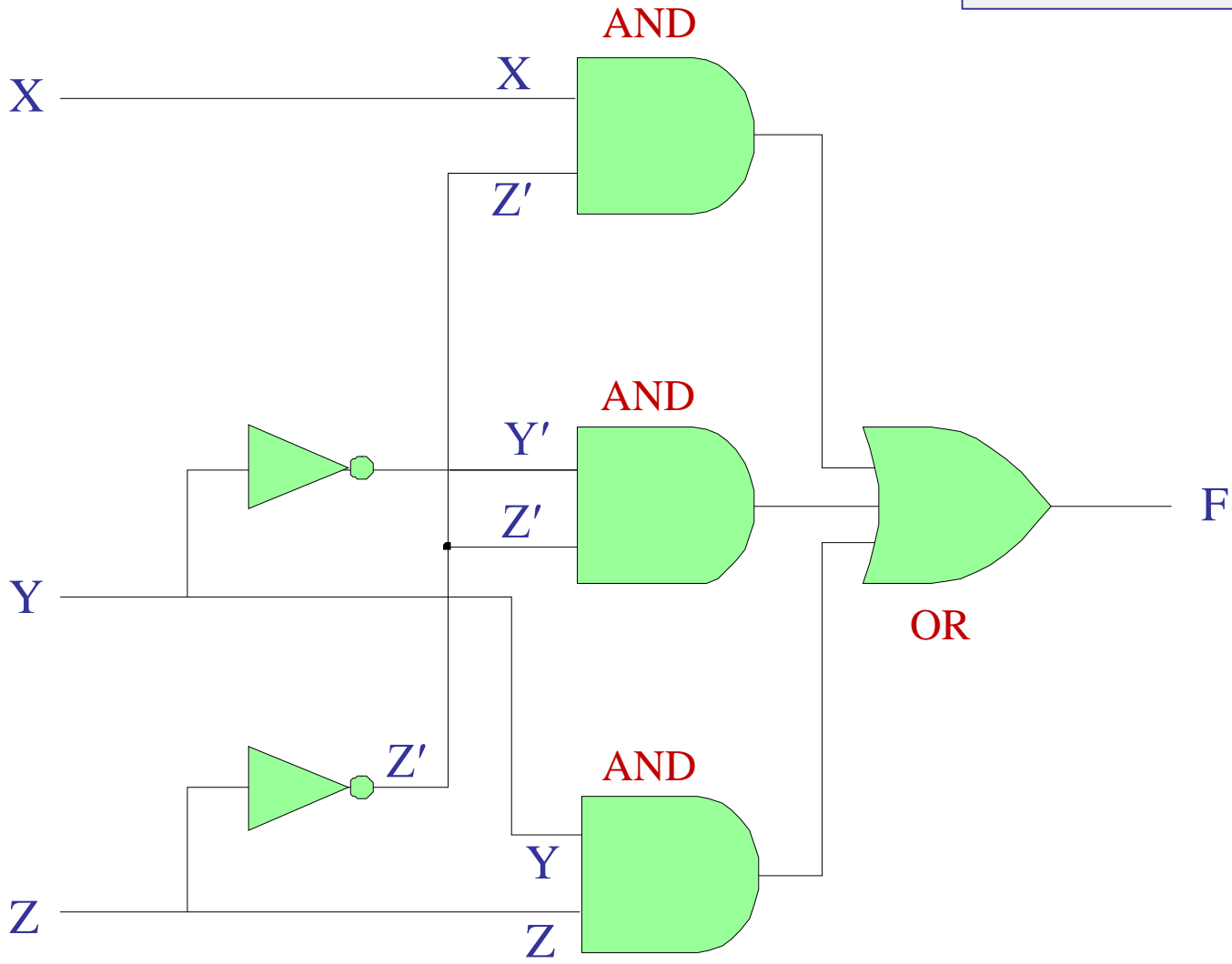$F = Y'Z' + YZ + XZ'$   
AND – OR realization




# Emona board realization

 


$$F = Y'Z' + YZ + XZ'$$

$$F = ( (Y'Z')' (YZ)' (XZ')' )'$$

NAND – NAND realization

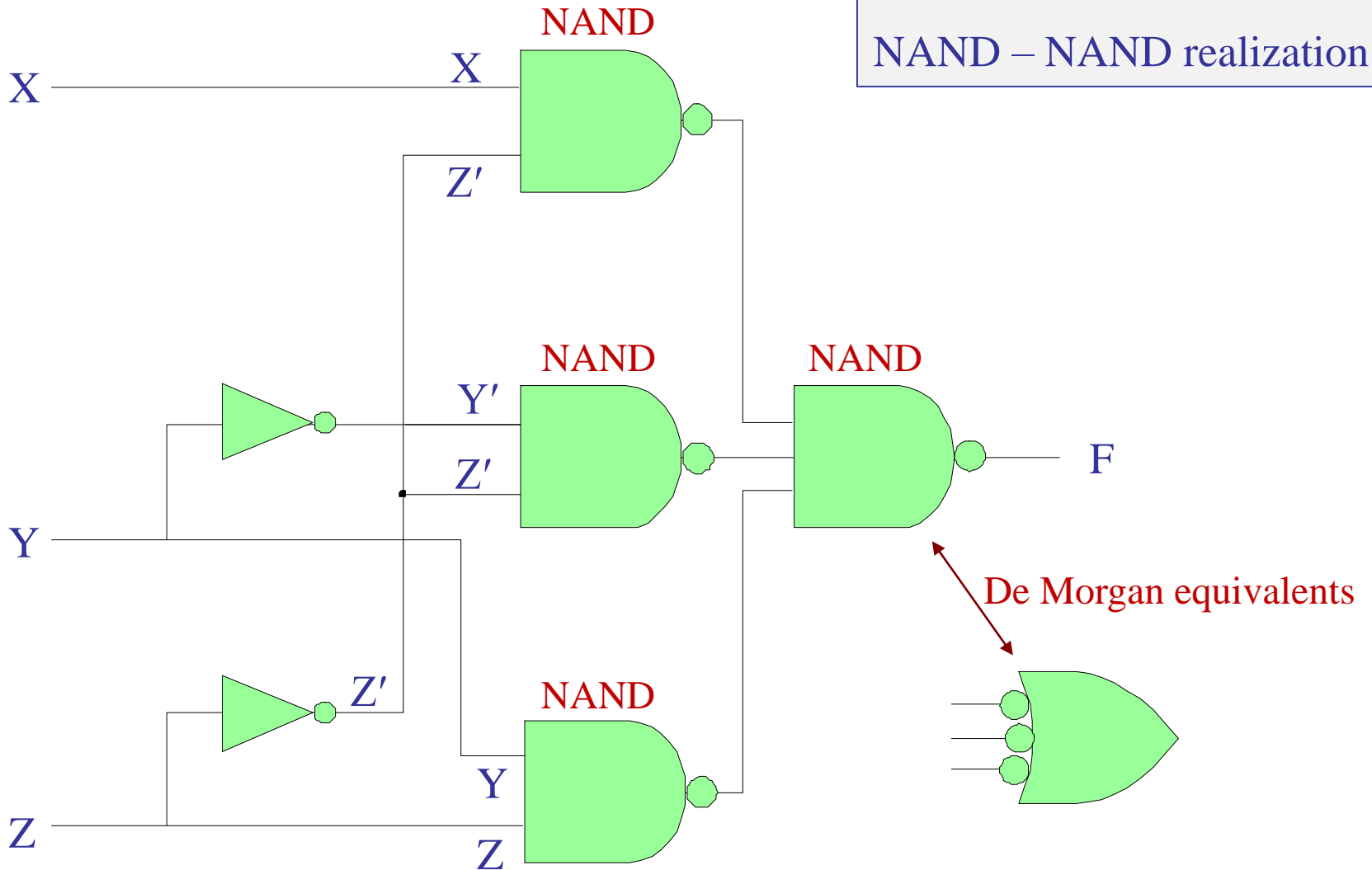

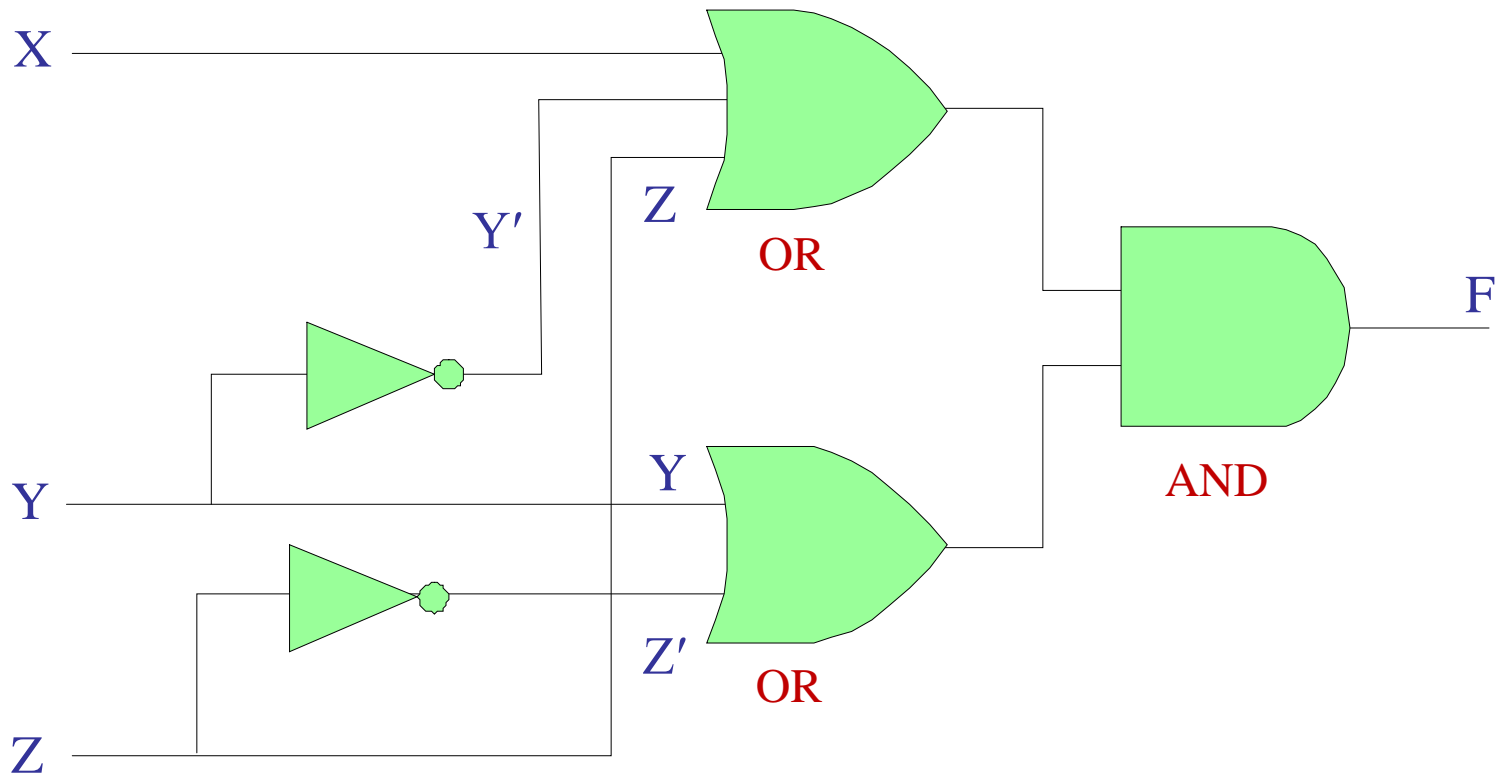$F = (Y + Z')(X + Y' + Z)$   
simplified POS realization  
OR – AND realization  
see next page for explanation



### truth table

X	Y	Z	F	F'
0	0	0	1	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	0	1
1	1	0	1	0
1	1	1	1	0

minterm SOP form for F,  
from the truth table

$$F = X'Y'Z' + XY'Z' + X'YZ + XYZ + XYZ'$$

minterm SOP form for F',  
from the truth table

$$F' = X'Y'Z + X'YZ' + XY'Z = (X' + X)Y'Z + X'YZ' = Y'Z + X'YZ'$$

$$F = (Y + Z')(X + Y' + Z)$$


↓ De Morgan

simplified POS realization
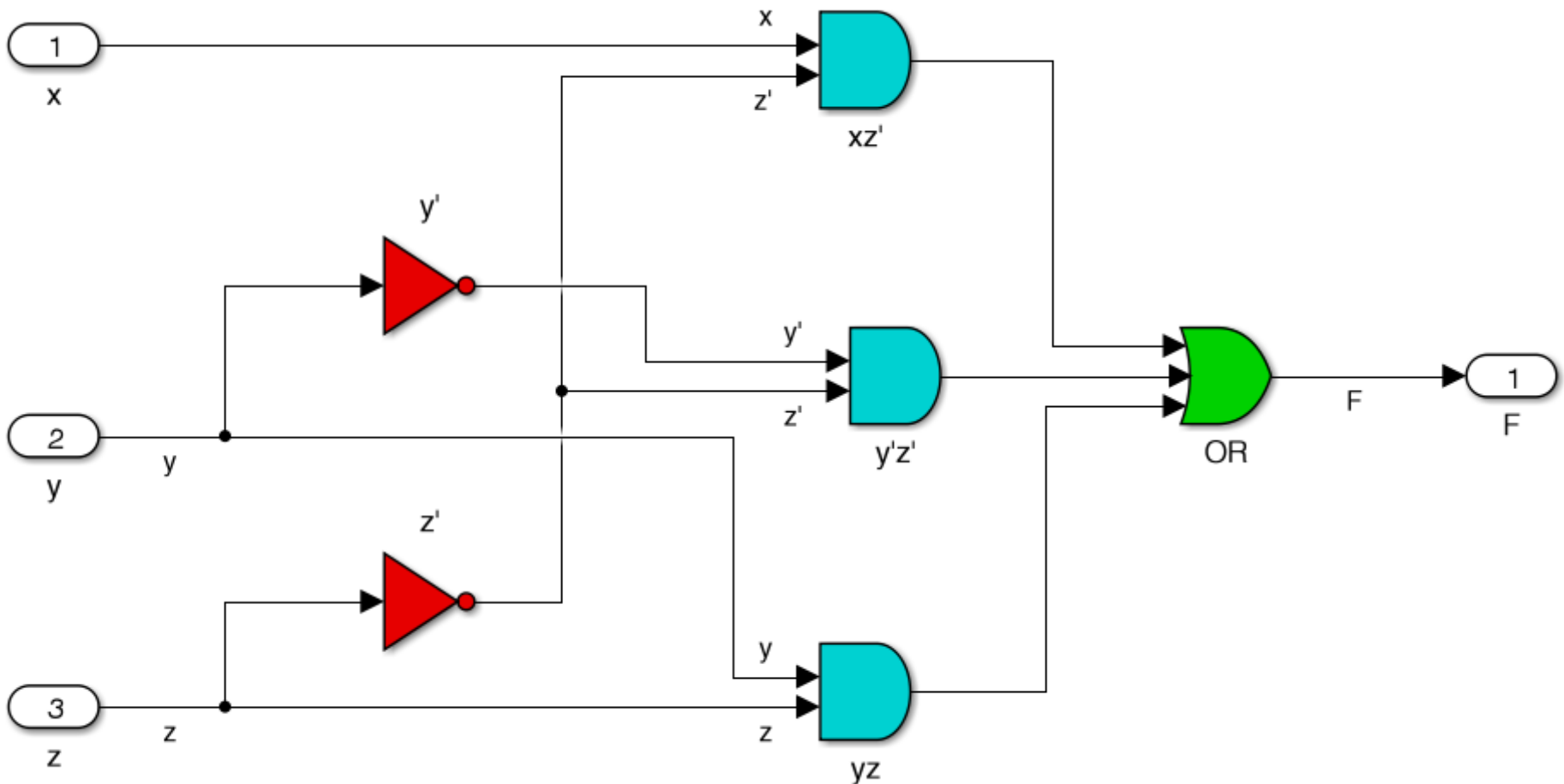
## 14. MATLAB/Simulink implementations, and exporting to Verilog

$$F = Y'Z' + YZ + XZ'$$

AND-OR realization, F-function re-drawn with Simulink




$$F = Y'Z' + YZ + XZ'$$

F-function embedded in executable Simulink realization

generate  
X,Y,Z signals for  
timing diagram

plot  
X,Y,Z,F  
signals

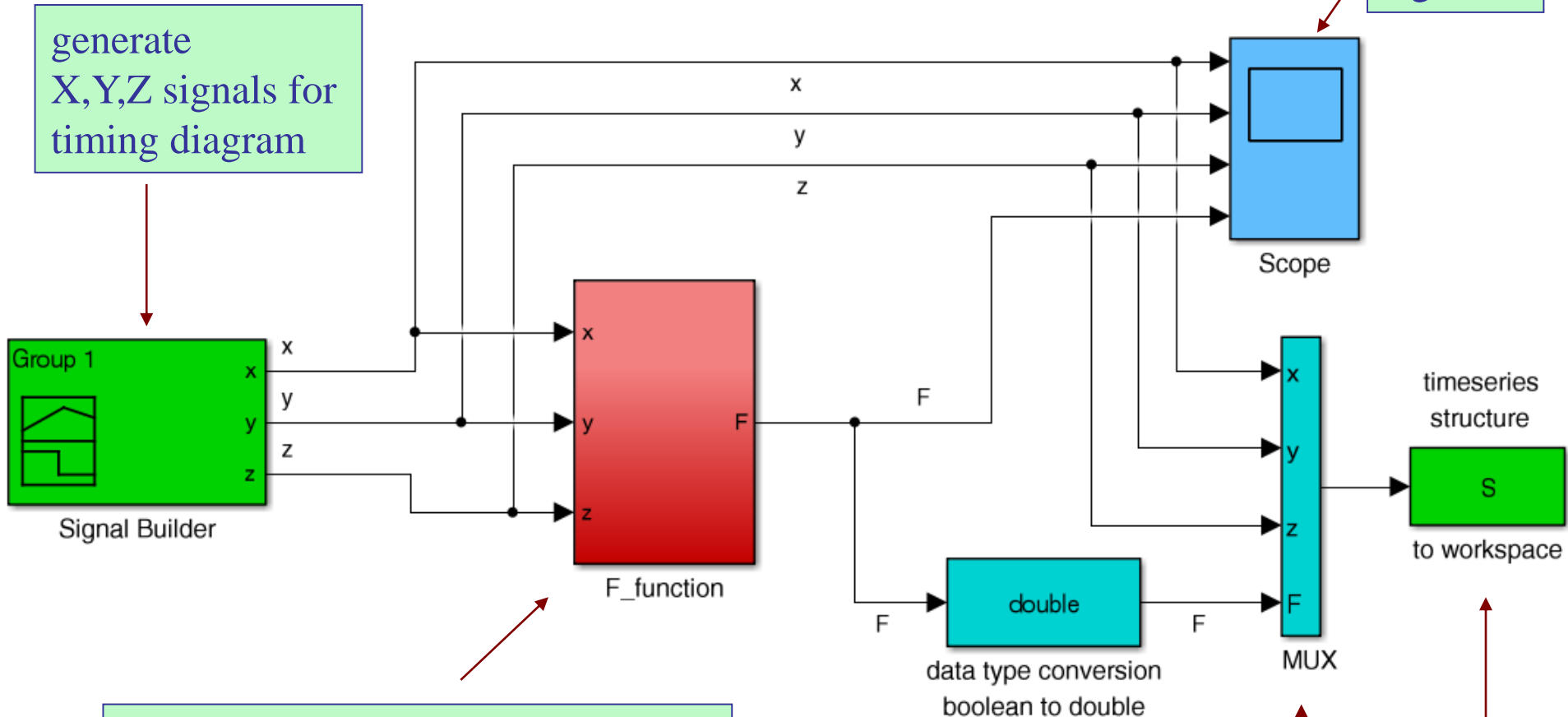


F-function resides within this block  
and can be exported to Verilog

needed for exporting X,Y,Z,F  
data to MATLAB's workspace

## Verilog code generated by Simulink – file table35v.v

```
module table35v (x, y, z, F);  
  
    input    x, y, z, F;  
  
    wire z_2; wire z_3; wire x_1;  
    wire y_2; wire y_3; wire y_4; wire y_5;  
    wire xz_out1;  
  
    assign z_2 = ~ z;  
    assign z_3 = z_2;  
    assign x_1 = x & z_3;  
    assign y_2 = ~ y;  
    assign y_3 = y_2;  
    assign y_4 = y_3 & z_3;  
    assign y_5 = y & z;  
    assign xz_out1 = y_5 | (x_1 | y_4);  
    assign F = xz_out1;  
  
endmodule
```

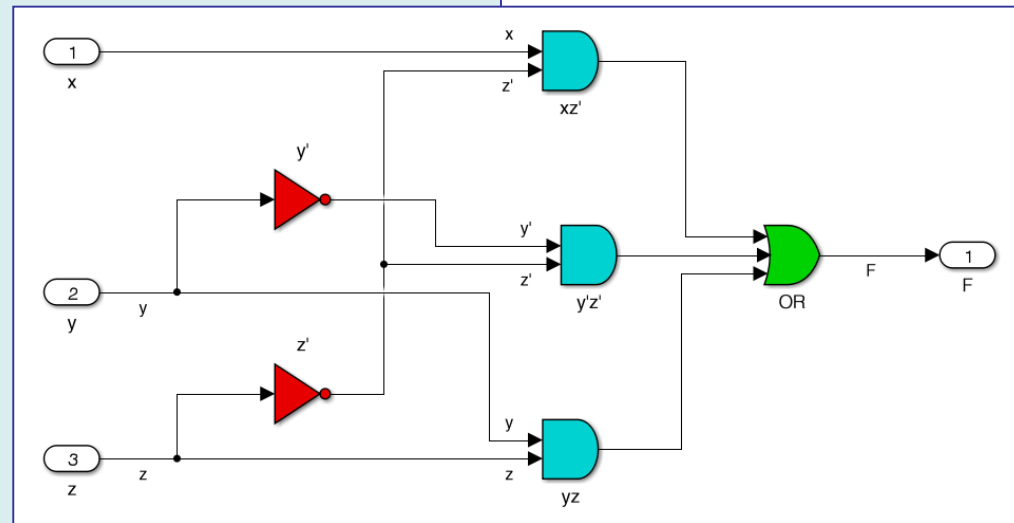




$F = Y'Z' + YZ + XZ'$   
verify truth table

truth table			
X	Y	Z	F
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

viewing timing diagram on scope

 

```
%% table35m.m - generating the truth table
```

```
[X,Y,Z] = a2d(0:7,3);    % 3-bit binary pattern
```

```
F = (~Y & ~Z) | (Y & Z) | (X & ~Z);    % construct output F
```

```
[X,Y,Z,F]    % print truth table
```

```
%   X   Y   Z   F
%   ---
%   0   0   0   1
%   0   0   1   0
%   0   1   0   0
%   0   1   1   1
%   1   0   0   1
%   1   0   1   0
%   1   1   0   1
%   1   1   1   1
```

MATLAB version of  
 $F = Y'Z' + YZ + XZ'$

the operations **&** and **|** are vectorized

```
% plot timing diagram


t = (0:8);      % last bit has duration from t=7 to t=8

x = [X; X(end)];      % extend duration of last bit
y = [Y; Y(end)];
z = [Z; Z(end)];
f = [F; F(end)];

set(0, 'DefaultAxesFontSize', 10);

figure;      % xaxis, yaxis are on Canvas M-files
subplot(4,1,1);
    stairs(t,x, 'b-'); yaxis(0,2,0:1); xaxis(0,8,0:8);
subplot(4,1,2);
    stairs(t,y, 'b-'); yaxis(0,2,0:1); xaxis(0,8,0:8);
subplot(4,1,3);
    stairs(t,z, 'b-'); yaxis(0,2,0:1); xaxis(0,8,0:8);
subplot(4,1,4);
    stairs(t,f, 'r-'); yaxis(0,2,0:1); xaxis(0,8,0:8);
xlabel('\itt');
```

timing diagram

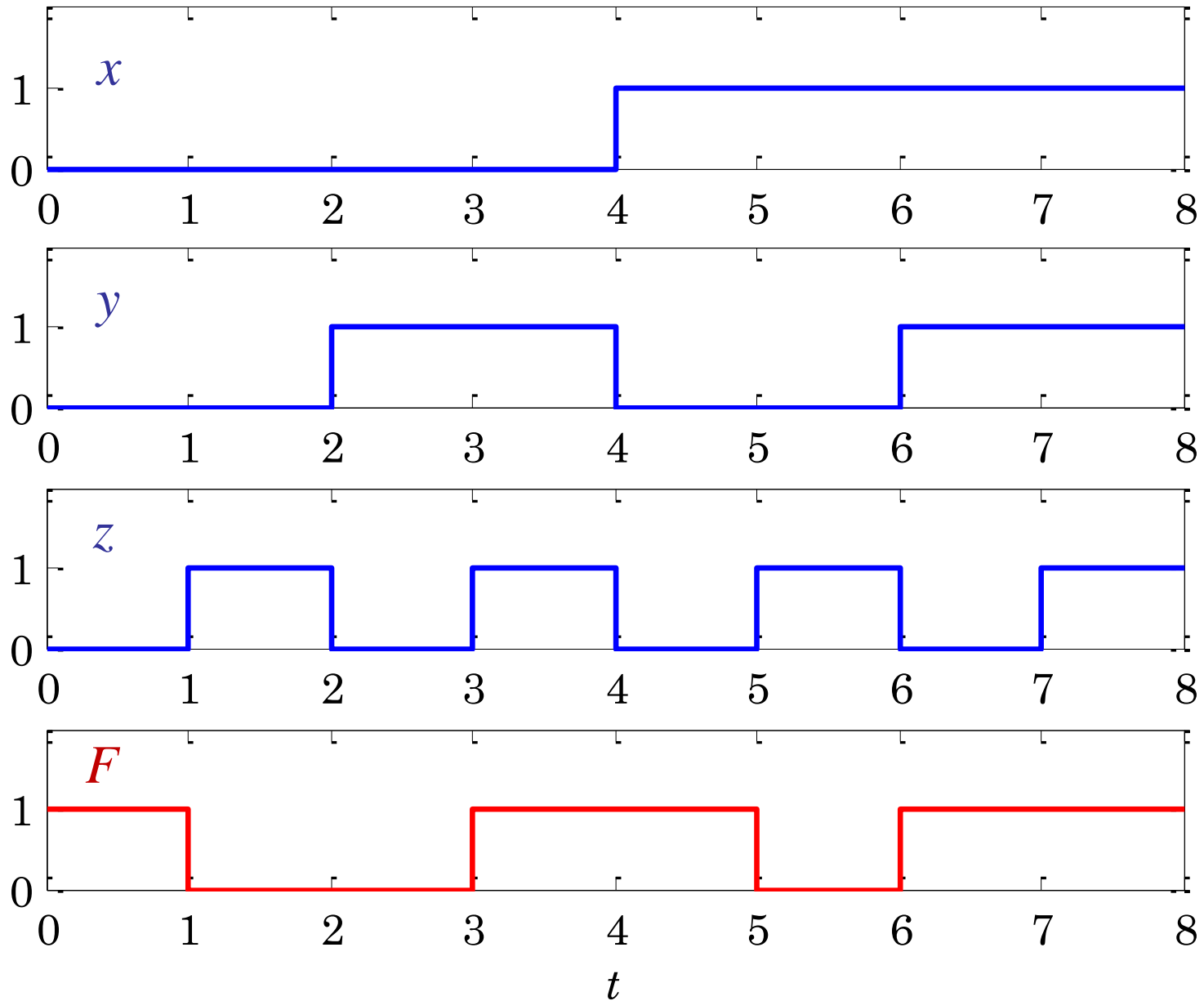


```
% plot timing diagram from saved simulation data  
% extracted from the timeseries structure S
```

```
t = S.time;  
x = S.data(:,1);  
y = S.data(:,2);  
z = S.data(:,3);  
F = S.data(:,4);
```

generating a better plot of the  
timing diagram, than from the  
scope plot

```
figure; % xaxis,yaxis are on Canvas M-files  
subplot(4,1,1);  
stairs(t,x,'b-'); yaxis(0,2,0:1); xaxis(0,8,0:8);  
subplot(4,1,2);  
stairs(t,y,'b-'); yaxis(0,2,0:1); xaxis(0,8,0:8);  
subplot(4,1,3);  
stairs(t,z,'b-'); yaxis(0,2,0:1); xaxis(0,8,0:8);  
subplot(4,1,4);  
stairs(t,F,'r-'); yaxis(0,2,0:1); xaxis(0,8,0:8);  
xlabel('\itt')
```

 
timing diagram from Simulink data exported to workspace



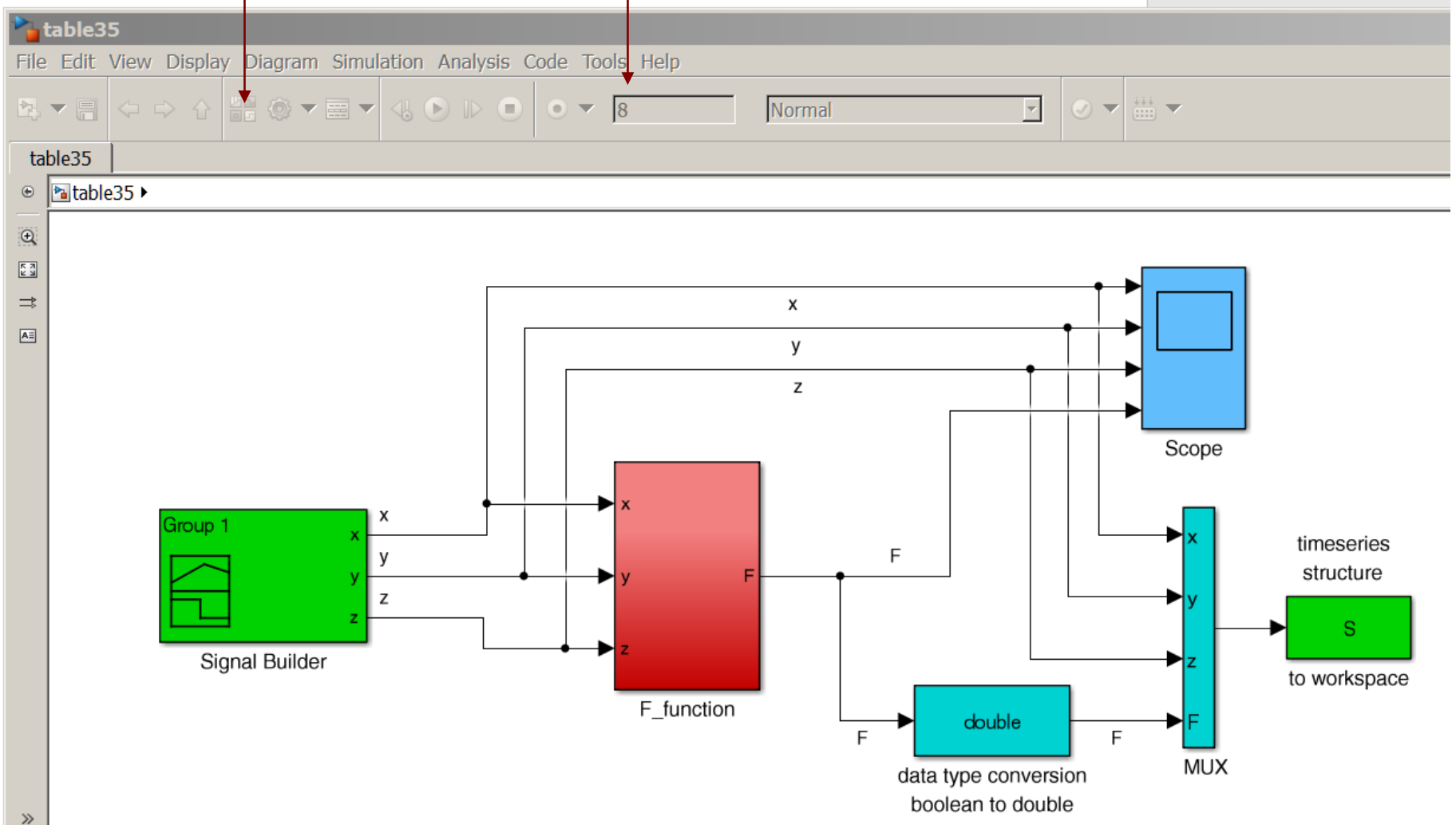
# Additional notes on Simulink

click here to open  
Simulink Library

set simulation duration to  
8 time units



 
click here to open scope parameters and select 4 axes (for X,Y,X,F) and time range of 8 units






drag the signal edges to change the shape of the signals

 double-click on the Signal Builder block to view the signals X,Y,Z over the time range of 8 units




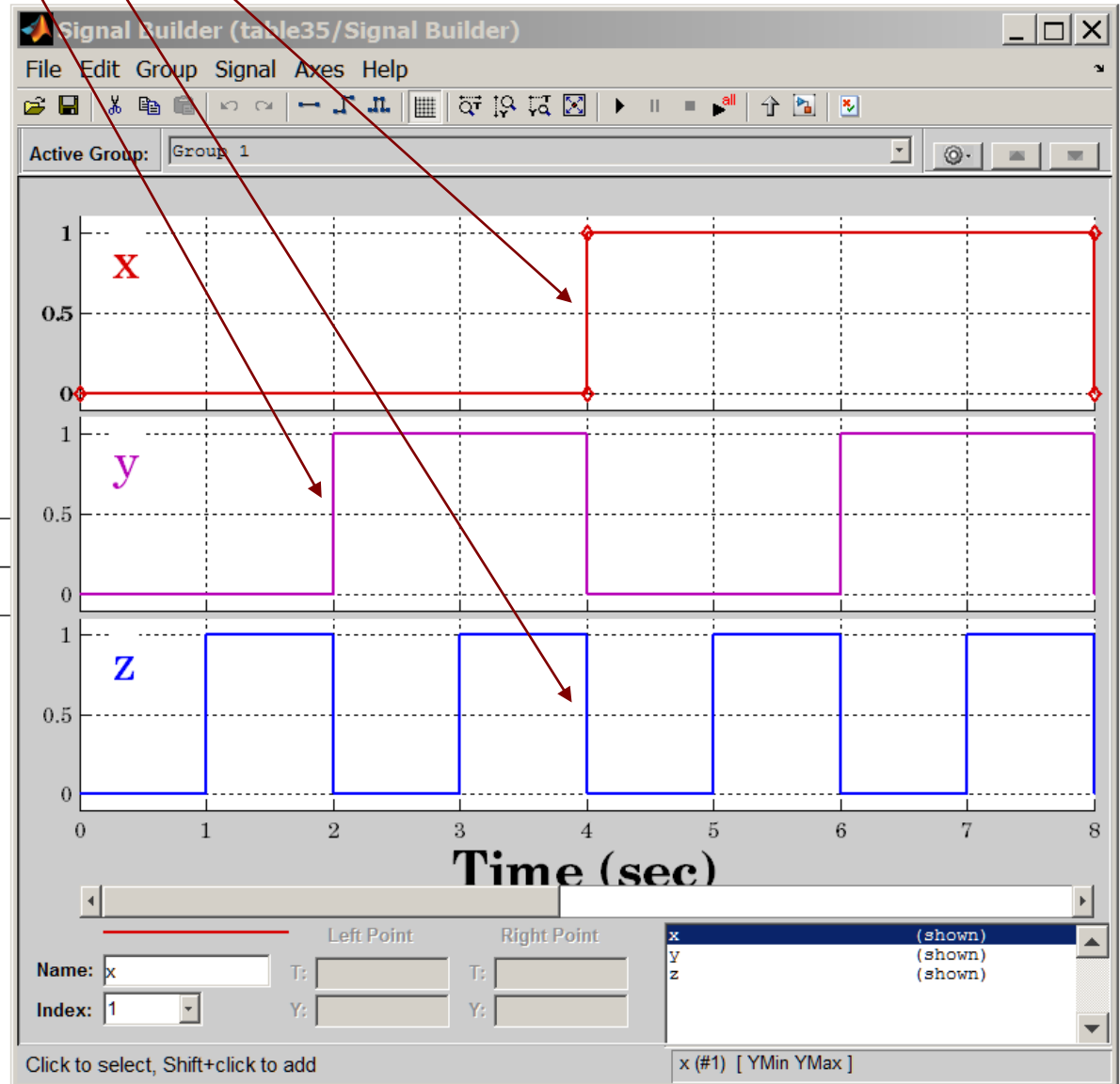can also be preloaded by copy/pasting from the file [signals234.slx](#) on Canvas



before exporting into Verilog, save the subfunction into a separate SLX Simulink file, then set the data types of the input/output ports to Boolean

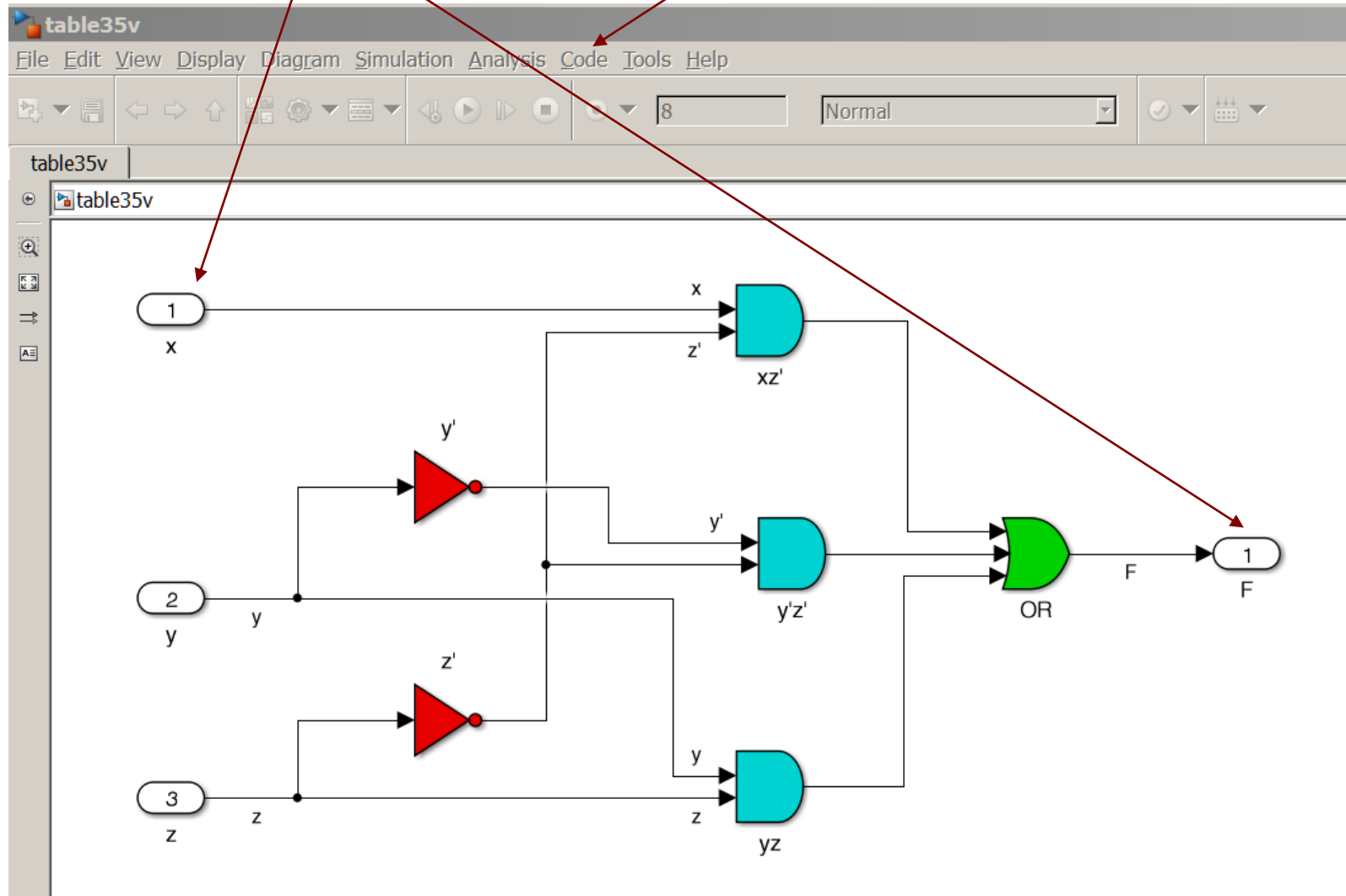select Code, then HDL code, Options, and Verilog



## 15. Standard representations of combinational circuits

truth table representations

2-variable $F(X,Y)$			
row	X	Y	F
0	0	0	$F(0,0)$
1	0	1	$F(0,1)$
2	1	0	$F(1,0)$
3	1	1	$F(1,1)$

3-variable $F(X,Y,Z)$				
row	X	Y	Z	F
0	0	0	0	$F(0,0,0)$
1	0	0	1	$F(0,0,1)$
2	0	1	0	$F(0,1,0)$
3	0	1	1	$F(0,1,1)$
4	1	0	0	$F(1,0,0)$
5	1	0	1	$F(1,0,1)$
6	1	1	0	$F(1,1,0)$
7	1	1	1	$F(1,1,1)$

↓ binary  
order

4-variable function  $F(A,B,C,D)$ 

row	A	B	C	D	F
0	0	0	0	0	$F(0,0,0,0)$
1	0	0	0	1	$F(0,0,0,1)$
2	0	0	1	0	$F(0,0,1,0)$
3	0	0	1	1	$F(0,0,1,1)$
4	0	1	0	0	$F(0,1,0,0)$
5	0	1	0	1	$F(0,1,0,1)$
6	0	1	1	0	$F(0,1,1,0)$
7	0	1	1	1	$F(0,1,1,1)$
8	1	0	0	0	$F(1,0,0,0)$
9	1	0	0	1	$F(1,0,0,1)$
10	1	0	1	0	$F(1,0,1,0)$
11	1	0	1	1	$F(1,0,1,1)$
12	1	1	0	0	$F(1,1,0,0)$
13	1	1	0	1	$F(1,1,0,1)$
14	1	1	1	0	$F(1,1,1,0)$
15	1	1	1	1	$F(1,1,1,1)$

## Truth-table representations with minterms or maxterms

3-variable  $F(X,Y,Z)$

row	X	Y	Z	F	minterms	maxterms
0	0	0	0	$F(0,0,0)$	$X' \cdot Y' \cdot Z'$	$X + Y + Z$
1	0	0	1	$F(0,0,1)$	$X' \cdot Y' \cdot Z$	$X + Y + Z'$
2	0	1	0	$F(0,1,0)$	$X' \cdot Y \cdot Z'$	$X + Y' + Z$
3	0	1	1	$F(0,1,1)$	$X' \cdot Y \cdot Z$	$X + Y' + Z'$
4	1	0	0	$F(1,0,0)$	$X \cdot Y' \cdot Z'$	$X' + Y + Z$
5	1	0	1	$F(1,0,1)$	$X \cdot Y' \cdot Z$	$X' + Y + Z'$
6	1	1	0	$F(1,1,0)$	$X \cdot Y \cdot Z'$	$X' + Y' + Z$
7	1	1	1	$F(1,1,1)$	$X \cdot Y \cdot Z$	$X' + Y' + Z'$

complements of each other  
by De Morgan

## Truth-table representations with minterms or maxterms

2-variable F(X,Y)					
row	X	Y	F	minterms	maxterms
0	0	0	F(0,0)	$X' \cdot Y'$	$X + Y$
1	0	1	F(0,1)	$X' \cdot Y$	$X + Y'$
2	1	0	F(1,0)	$X \cdot Y'$	$X' + Y$
3	1	1	F(1,1)	$X \cdot Y$	$X' + Y'$



complements of each other  
by De Morgan

**Example 3, continued:** Previously, we demonstrated the equivalence of the following expressions for F as a function of the Boolean variables X, Y, Z,

$$F = X'Y'Z' + XY'Z' + X'YZ + XYZ + XYZ' = \text{(sum of minterms, SOP)}$$

$$F = (X + Y + Z')(X + Y' + Z)(X' + Y + Z') = \text{(product of maxterms, POS)}$$

They were based on the truth table shown on the right (Table 3-5 of the Wakerly text)

To understand these expressions, we expand the truth table to also include the **complement** of F, that is, F', obtained by interchanging 0s and 1s in the F column.

truth table			
X	Y	Z	F
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

$$F = X'Y'Z' + X'YZ + XY'Z' + XYZ' + XYZ \quad (\text{minterm SOP, sum-of-products})$$

$$F' = X'Y'Z + X'YZ' + XY'Z \quad (\text{minterms of } F' \text{ from truth table})$$

$$F = F'' = (X'Y'Z + X'YZ' + XY'Z)' = (X'Y'Z)' (X'YZ')' (XY'Z)' \quad \leftarrow \text{De Morgan}$$

$$F = (X + Y + Z') (X + Y' + Z) (X' + Y + Z') \quad (\text{maxterm POS, product-of-sums})$$

truth table							
X	Y	Z	F	F'	F minterms	F' minterms	F maxterms
0	0	0	1	0	$X'Y'Z'$		
0	0	1	0	1		$X'Y'Z$	$X+Y+Z'$
0	1	0	0	1		$X'YZ'$	$X+Y'+Z$
0	1	1	1	0	$X'YZ$		
1	0	0	1	0	$XY'Z'$		
1	0	1	0	1		$XY'Z$	$X'+Y+Z'$
1	1	0	1	0	$XYZ'$		
1	1	1	1	0	$XYZ$		

De Morgan  


$$(\text{maxterms of } F = (\text{minterms of } F')')$$



## 16. Canonical minterm/SOP and maxterm/POS representations

### Sum-of-Products (SOP) rule:

F is the **sum** of those minterms that correspond to the values **F=1** in the truth table

Notation:  $F = \Sigma(\text{of the } F=1 \text{ minterms}) = \text{canonical sum-of-products}$

as indicated by the **row numbers** in the truth table

### Product-of-Sums (POS) rule:

F is the **product** of those maxterms that correspond to the values **F=0** (or,  $F' = 1$ ) in the truth table

Notation:  $F = \Pi(\text{of the } F=0 \text{ maxterms}) = \text{canonical product-of-sums}$

as indicated by the **row numbers** in the truth table

Example:

$$F = X'Y'Z' + X'YZ + XY'Z' + XYZ' + XYZ = \Sigma_{X,Y,Z}(0,3,4,6,7)$$

$$F = (X + Y + Z') (X + Y' + Z) (X' + Y + Z') = \Pi_{X,Y,Z}(1,2,5)$$

equivalent

truth table					
row	X	Y	Z	F	F'
0	0	0	0	1	0
1	0	0	1	0	1
2	0	1	0	0	1
3	0	1	1	1	0
4	1	0	0	1	0
5	1	0	1	0	1
6	1	1	0	1	0
7	1	1	1	1	0

how does it work? →

X	Y	Z	F	minterms	X' Y' Z'	X' Y Z	X Y' Z'	X Y Z'	X Y Z
0	0	0	1	X' Y' Z'	1	0	0	0	0
0	0	1	0		0	0	0	0	0
0	1	0	0		0	0	0	0	0
0	1	1	1	X' Y Z	0	1	0	0	0
1	0	0	1	X Y' Z'	0	0	1	0	0
1	0	1	0		0	0	0	0	0
1	1	0	1	X Y Z'	0	0	0	1	0
1	1	1	1	X Y Z	0	0	0	0	1



F = OR'ing these five columns together

$$F = X'Y'Z' + X'YZ + XY'Z' + XYZ' + XYZ$$

```
[x,y,z] = a2d(0:7,3);
[x, y, z, ~x&~y&~z, ~x&y&z, x&~y&~z, x&y&~z, x&y&z]
```

X	Y	Z	F	maxterms	$X+Y+Z'$	$X+Y'+Z$	$X'+Y+Z'$
0	0	0	1		1	1	1
0	0	1	0	$X+Y+Z'$	0	1	1
0	1	0	0	$X+Y'+Z$	1	0	1
0	1	1	1		1	1	1
1	0	0	1		1	1	1
1	0	1	0	$X'+Y+Z'$	1	1	0
1	1	0	1		1	1	1
1	1	1	1		1	1	1

F = AND'ing these three columns together

$$F = (X + Y + Z') (X + Y' + Z) (X' + Y + Z')$$

```
[x,y,z] = a2d(0:7,3);
```

```
[x, y, z, x|y|~z, x|~y|z, ~x|y|~z]
```

## Nomenclature

<b>literal:</b>	a single Boolean variable, e.g., X
<b>product term:</b>	a product of variables, e.g., XZ
<b>sum term:</b>	a sum of variables, e.g., Y+Z
<b>minterm:</b>	a product of input variables corresponding to a row in truth table e.g., XY'Z, corresponding to row 101 = 5
<b>canonical SOP:</b>	canonical minterm sum-of-products, e.g., $\Sigma_{X,Y,Z}(0,3,4,6,7)$
<b>minterm list :</b>	list of row numbers that appear in a canonical SOP
<b>maxterm:</b>	a sum of input variables, e.g., X+Y'+Z, corresponding to the <b>complement</b> of a row in the truth table
<b>canonical POS:</b>	canonical maxterm product-of-sums, e.g., $\Pi_{X,Y,Z}(1,2,5)$
<b>maxterm list :</b>	list of row numbers that appear in a canonical POS

## Nomenclature

**implicant:** a minterm or sum of minterms appearing in a function  $F$ , if an implicant evaluates to 1, then so does  $F$  as a whole, i.e., if, **implicant=1**, then it implies,  **$F=1$**

**prime implicant:** a simplified implicant that cannot be combined into another implicant that has fewer number of literals.

**covers:** all implicants that account for all possible evaluations of the function into  $F=1$  (i.e., all the 1's in a Karnaugh map).


**essential prime implicant:** a prime implicant that contains an  $F=1$  minterm that is not included in any other prime implicant, all essential prime implicants **must be included** in the cover of the function.

In addition to the essential PIs, it may be necessary to include possible non-essential PIs in order to achieve a **complete cover**, (if there are several such possibilities, one could choose the one that has the smallest number of literals.
 
## 17. Combinational circuit analysis – Example 1

Previously (in Example 3) we looked at a combinational circuit **synthesis** problem, in which the circuit was defined by a truth table, and we synthesized it in several equivalent ways using logic gates.

Here, we look at an **analysis** example of a circuit constructed in terms of logic gates, as shown below, the objective being to determine its **input/output function**,  $F=f(X,Y,Z)$ , and its **truth table**, construct its **timing diagram**, and additionally, realize it in alternative ways.




Wakerly, Fig.3-8


$$F = (X+Y')Z + X'YZ' = XZ + Y'Z + X'YZ'$$

**procedure:** assign labels to the circuit lines and implement the indicated logic gate operations from the inputs to the output.

 $F = (X+Y')Z + X'YZ'$   
 $F = XZ + Y'Z + X'YZ'$   
 alternative realization based  
 on the second expression




 $F = XZ + Y'Z + X'YZ'$   
 NAND-NAND realization  
 after bubble pushing





$$F = XZ + Y'Z + X'YZ'$$
 truth table

 

truth table				
row	X	Y	Z	F
0	0	0	0	0
1	0	0	1	1
2	0	1	0	1
3	0	1	1	0
4	1	0	0	0
5	1	0	1	1
6	1	1	0	0
7	1	1	1	1

Wakerly, Table 3-7

## MATLAB implementation

```
[X,Y,Z] = a2d(0:7,3); % 3-bit binary pattern
```

```
F = (X & Z) | (~Y & Z) | (~X & Y & ~Z); % output F
```

```
[X,Y,Z,F] % collect X,Y,Z,F for printing  
           % print truth table
```

```
% X Y Z F  
% -----  
% 0 0 0 0  
% 0 0 1 1  
% 0 1 0 1  
% 0 1 1 0  
% 1 0 0 0  
% 1 0 1 1  
% 1 1 0 0  
% 1 1 1 1
```

MATLAB code for  
 $F = XZ + Y'Z + X'YZ'$

the operations **&** and **|** are vectorized


## Verilog implementation

```
module Acirc1f(  
  input X,Y,Z,  
  wire XN, YN, ZN, XYN, XYNZ, XNYZN,  
  output wire F  
);
```


Verilog code for  
 $F = (X + Y')Z + X'YZ'$

```
  assign XN = ~X; assign YN = ~Y; assign ZN = ~Z;  
  assign XYN = X | YN; assign XYNZ = XYN & Z;  
  assign XNYZN = XN & Y & ZN; assign F = XYNZ | XNYZN;
```

```
endmodule
```

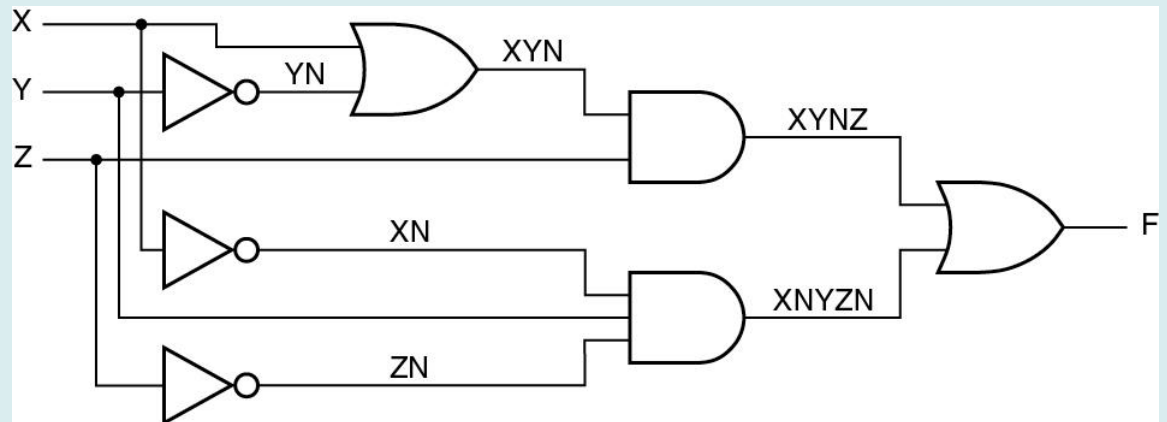
 
$$F = XZ + Y'Z + X'YZ' - \text{timing diagram}$$



truth table				
row	X	Y	Z	F
0	0	0	0	0
1	0	0	1	1
2	0	1	0	1
3	0	1	1	0
4	1	0	0	0
5	1	0	1	1
6	1	1	0	0
7	1	1	1	1

$F = XZ + Y'Z + X'YZ'$  - MATLAB code for timing diagram

```
t = 0:8;

% see p.98 for definitions of X,Y,Z,F

X = [X; X(end)];      % replicate last entries
Y = [Y; Y(end)];
Z = [Z; Z(end)];
F = [F; F(end)];      % t,X,Y,Z now have length 9

figure;
subplot(4,1,1);
    stairs(t,X,'b-'); yaxis(0,2,0:1); xaxis(0,8,0:8);
subplot(4,1,2);
    stairs(t,Y,'b-'); yaxis(0,2,0:1); xaxis(0,8,0:8);
subplot(4,1,3);
    stairs(t,Z,'b-'); yaxis(0,2,0:1); xaxis(0,8,0:8);
subplot(4,1,4);
    stairs(t,F,'r-'); yaxis(0,2,0:1); xaxis(0,8,0:8);
xlabel('\itt')
```

$$F = (X+Y')Z + X'YZ'$$

alternative representation based on product-of-sums

$$F = (X+Y'+Z') (X'+Z) (Y+Z) = (X+Y+Z) (X+Y'+Z') (X'+Y+Z) (X'+Y'+Z)$$

it is actually a simplified version of the canonical maxterm expansion, but a direct proof is as follows:

Using the ordinary distributive law,  $(X+A)(X+B) = (X+AB)$ , we obtain the more general version of the distributive law,

$$(AB + CDE) = (A + C) (A + D) (A + E) (B + C) (B + D) (B + E)$$

and apply it with,  $A=X+Y'$ ,  $B=Z$ ,  $C=X'$ ,  $D=Y$ ,  $E=Z'$ , and note that,  $X+1 = 1$ ,  $X+X'=1$ ,

$$\begin{aligned} F &= (X + Y')Z + X'YZ' \\ &= (X + Y' + X') (X + Y' + Y) (X + Y' + Z') (Z + X') (Z + Y) (Z + Z') \\ &= (1 + Y') (X + 1) (X + Y' + Z') (Z + X') (Z + Y) 1 = \\ &= (X + Y' + Z') (X' + Z) (Y + Z) \end{aligned}$$

Proof of the generalized distributive law:

$$(AB + CDE) = (A + C) (A + D) (A + E) (B + C) (B + D) (B + E)$$

apply the ordinary distributive law,  $(X+A)(X+B) = (X+AB)$ , in stages:

$$\begin{aligned} AB + CDE &= (A + CDE) (B + CDE) \\ &= (A + C) (A + DE) (B + C) (B + DE) \\ &= (A + C) (A + D) (A + E) (B + C) (B + D)(B + E) \end{aligned}$$

Next, we look at the minterm / maxterm canonical expansions of this example, and their simplifications

## minterm / maxterm representations

truth table					
X	Y	Z	F	F'	
					minterms
					maxterms
0	0	0	0	1	
0	0	1	1	0	X' Y' Z
0	1	0	1	0	X' Y Z'
0	1	1	0	1	
1	0	0	0	1	
1	0	1	1	0	X Y' Z
1	1	0	0	1	
1	1	1	1	0	X Y Z

$$F = X'Y'Z + X'YZ' + XY'Z + XYZ = \text{minterm SOP}$$

$$F = (X + Y + Z) (X + Y' + Z') (X' + Y + Z) (X' + Y' + Z) = \text{maxterm POS}$$



## minterm / maxterm simplifications

minterms:


$$\begin{aligned} F &= X'Y'Z + X'YZ' + XY'Z + XYZ = X'Y'Z + X'YZ' + XY'Z + \mathbf{XY'Z} + XYZ \\ &= (X' + X)Y'Z + X'YZ' + X(Y + Y')Z = \\ &= Y'Z + X'YZ' + XZ \end{aligned}$$

replicated


maxterms:

$$\begin{aligned} F &= (X + Y + Z) (X + Y' + Z') (X' + Y + Z) (X' + Y' + Z) = \\ &= (X + Y + Z) (X + Y' + Z') (X' + Y + Z) (\mathbf{X' + Y + Z}) (X' + Y' + Z) \\ &= (\mathbf{X + Y + Z}) (\mathbf{X' + Y + Z}) (X' + Y + Z) (X' + Y' + Z) (X + Y' + Z') \\ &= (\mathbf{Y + Z}) (X' + Z) (X + Y' + Z') \end{aligned}$$

property:  $(Y + A)(Y' + A) = A$

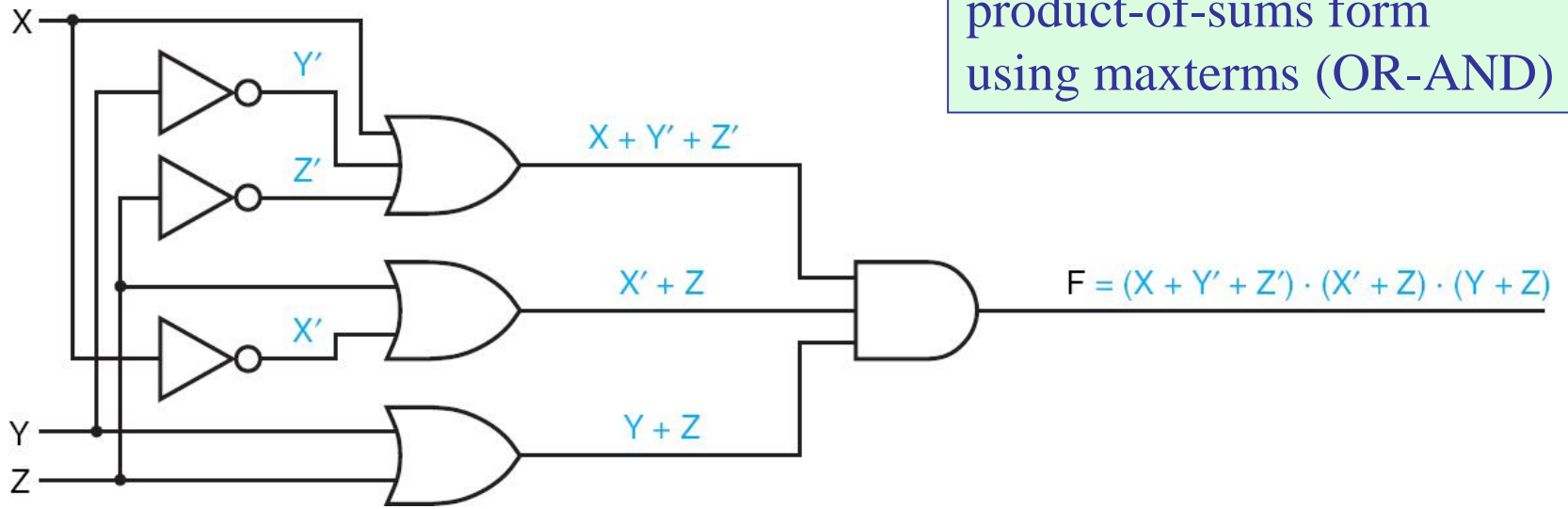

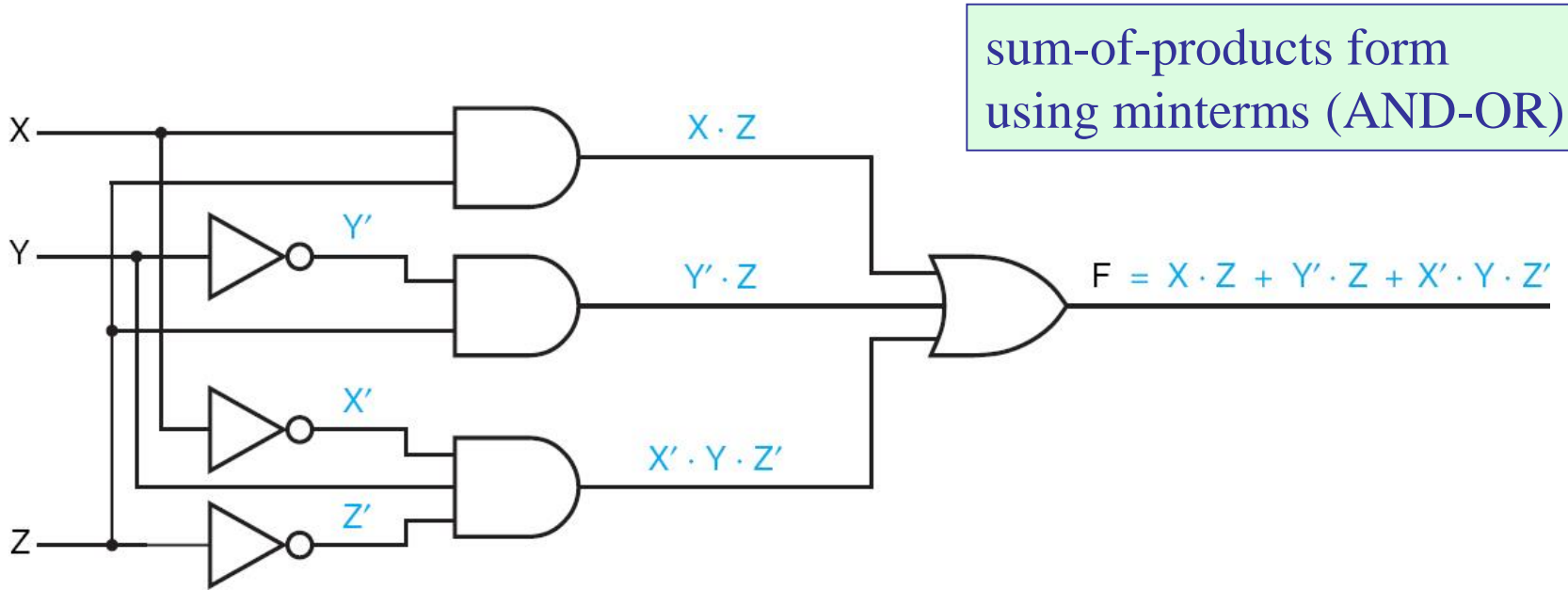
product-of-sums form  
using maxterms (OR-AND)



sum-of-products form  
using minterms (AND-OR)

## 17. Combinational circuit analysis – Example 2

Wakerly, Fig.3-11

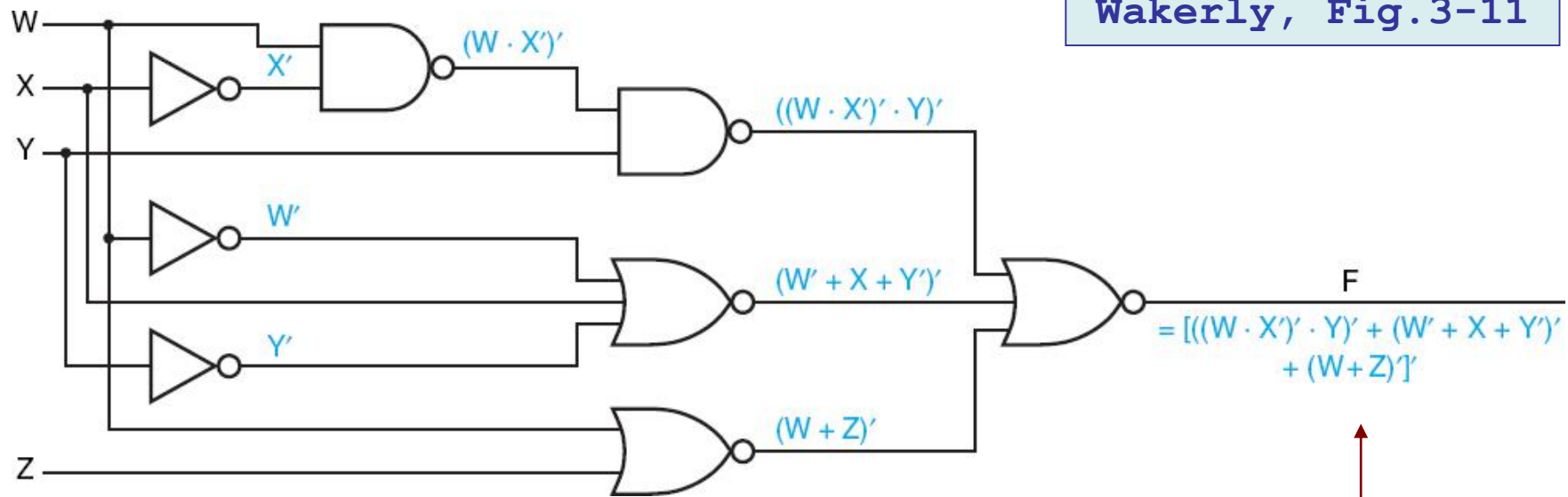


De Morgan



$$\begin{aligned}
 F &= [((W \cdot X') \cdot 'Y)' + (W' + X + Y)' + (W + Z)]' \\
 &= ((W' + X)' + Y)' \cdot (W \cdot X' \cdot Y) \cdot '(W' \cdot Z)' \\
 &= ((W \cdot X')' \cdot Y \cdot (W' + X + Y)' \cdot (W + Z) \\
 &= (W' + X) \cdot Y \cdot (W' + X + Y)' \cdot (W + Z)
 \end{aligned}$$

$$F = (W' + X) \cdot Y \cdot (W' + X + Y)' \cdot (W + Z)$$
 
$$F = (W'+X) \cdot Y \cdot (W'+X+Y') \cdot (W+Z)$$



De Morgan

 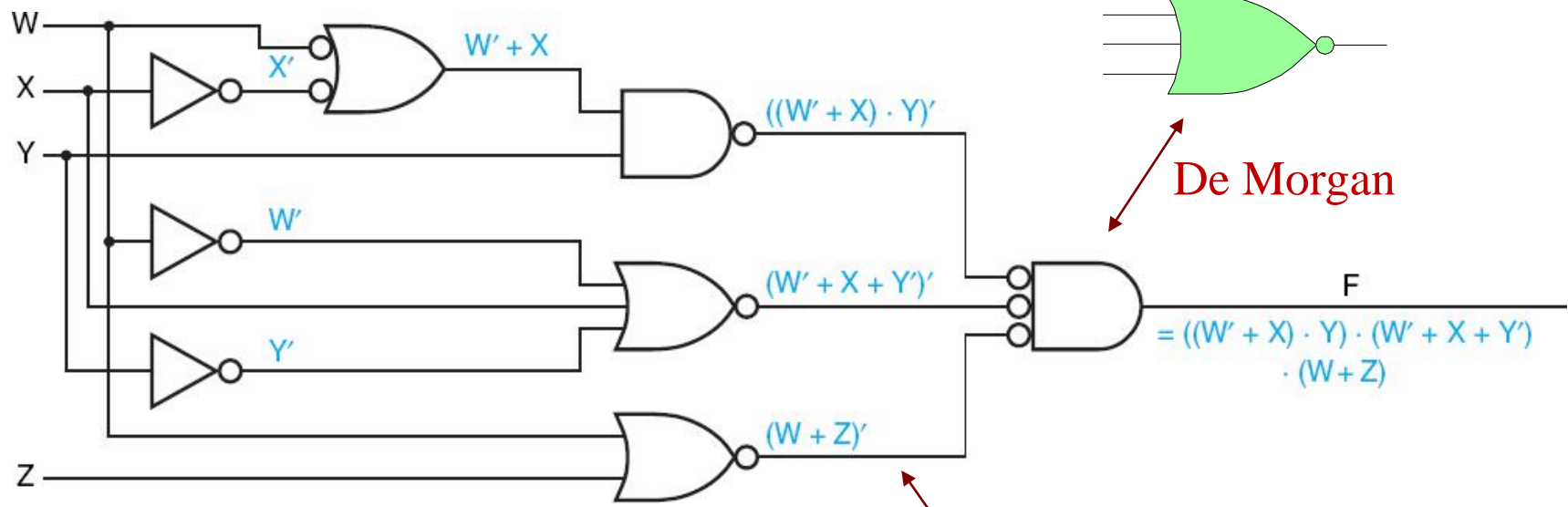


De Morgan

bubbles cancel on same line

Wakerly, Fig.3-12
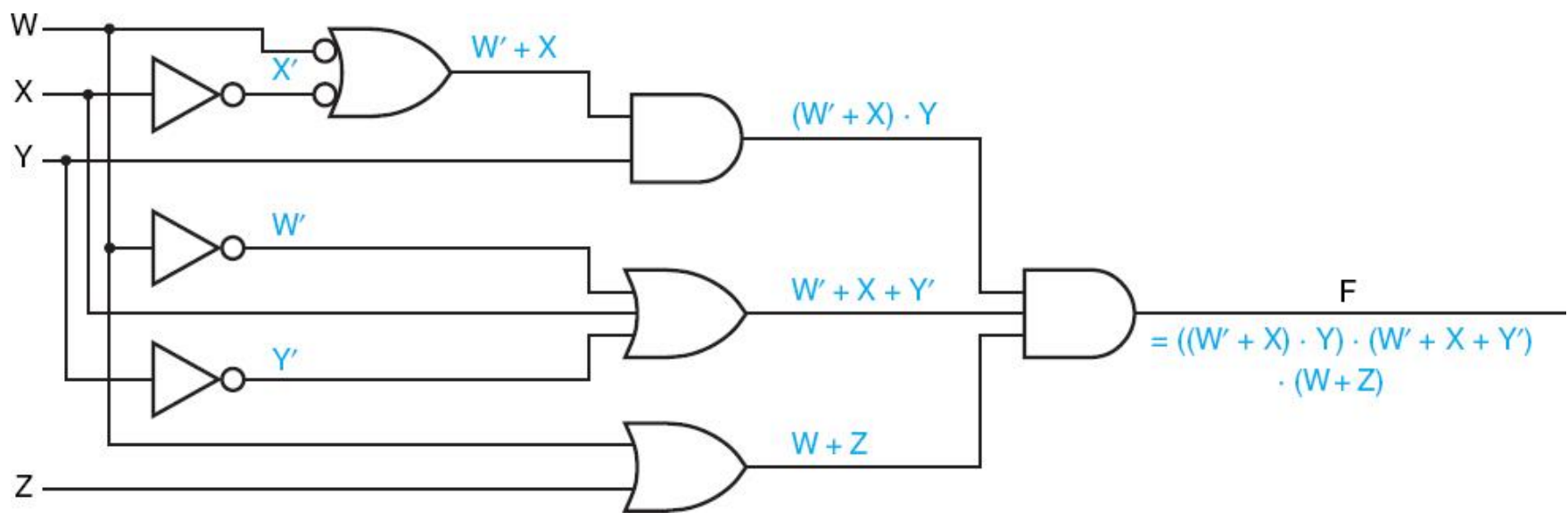
$$F = (W' + X) \cdot Y \cdot (W' + X + Y') \cdot (W + Z)$$




Wakerly, Fig.3-13

## 18. Combinational circuit synthesis

We recall that the analysis and synthesis problems are:

**Analysis Problem:** Given a combinational circuit made up of logic gates, determine the output  $F$  as a function of the input variables,  $X, Y, Z, \dots$

 **Synthesis/Design Problem:** Given a combinational circuit defined by its I/O mapping,  $F = f(X, Y, Z, \dots)$ , typically stated as a truth table, synthesize the circuit with logic gates, preferably using the minimum number of gates, as well as trying to minimize propagation delays.



Below, we present a few synthesis examples based on the circuit's I/O mapping,  $F = f(X, Y, Z, \dots)$ , determined from a given (i) truth table, or, (ii) functional description of the circuit. Karnaugh maps provide a systematic synthesis method and will be discussed later on.

## 18. Combinational circuit synthesis

### Example 1 – prime number detector

Wakerly, Sect.3.3.1

canonical minterm SOP form



$$F = \sum_{A,B,C,D}(1,2,3,5,7,11,13)$$

$$F = \prod_{A,B,C,D}(0,4,6,8,9,10,12,14,15)$$



canonical maxterm POS form

row	A	B	C	D	F	minterms
0	0	0	0	0	0	
1	0	0	0	1	1	$A'B'C'D$
2	0	0	1	0	1	$A'B'CD'$
3	0	0	1	1	1	$A'B'CD$
4	0	1	0	0	0	
5	0	1	0	1	1	$A'BC'D$
6	0	1	1	0	0	
7	0	1	1	1	1	$A'BCD$
8	1	0	0	0	0	
9	1	0	0	1	0	
10	1	0	1	0	0	
11	1	0	1	1	1	$AB'CD$
12	1	1	0	0	0	
13	1	1	0	1	1	$ABC'D$
14	1	1	1	0	0	
15	1	1	1	1	0	

## Example 1 – prime number detector

$$\begin{aligned}
 F &= \sum_{A,B,C,D}(1,2,3,5,7,11,13) = \\
 &= A'B'C'D + A'B'CD' \\
 &\quad + A'B'CD + A'BC'D \\
 &\quad + A'BCD + AB'CD \\
 &\quad + ABC'D
 \end{aligned}$$

row	A	B	C	D	F	minterms
0	0	0	0	0	0	
1	0	0	0	1	1	A'B'C'D
2	0	0	1	0	1	A'B'CD'
3	0	0	1	1	1	A'B'CD
4	0	1	0	0	0	
5	0	1	0	1	1	A'BC'D
6	0	1	1	0	0	
7	0	1	1	1	1	A'BCD
8	1	0	0	0	0	
9	1	0	0	1	0	
10	1	0	1	0	0	
11	1	0	1	1	1	AB'CD
12	1	1	0	0	0	
13	1	1	0	1	1	ABC'D
14	1	1	1	0	0	
15	1	1	1	1	0	



## Example 1 – prime number detector

$$= (A'B'C'D)'$$

$$F = \Pi_{A,B,C,D}(0,4,6,8,9,10,12,14,15)$$

$$= (A+B+C+D) \cdot (A+B'+C+D)$$

$$\cdot (A+B'+C'+D) \cdot (A'+B+C+D)$$


$$\cdot (A'+B+C+D') \cdot (A'+B+C'+D)$$

$$\cdot (A'+B'+C+D) \cdot (A'+B'+C'+D)$$

$$\cdot (A'+B'+C'+D')$$

row	A	B	C	D	F	maxterms
0	0	0	0	0	0	$A+B+C+D$
1	0	0	0	1	1	
2	0	0	1	0	1	
3	0	0	1	1	1	
4	0	1	0	0	0	$A+B'+C+D$
5	0	1	0	1	1	
6	0	1	1	0	0	$A+B'+C'+D$
7	0	1	1	1	1	
8	1	0	0	0	0	$A'+B+C+D$
9	1	0	0	1	0	$A'+B+C+D'$
10	1	0	1	0	0	$A'+B+C'+D$
11	1	0	1	1	1	
12	1	1	0	0	0	$A'+B'+C+D$
13	1	1	0	1	1	
14	1	1	1	0	0	$A'+B'+C'+D$
15	1	1	1	1	0	$A'+B'+C'+D'$

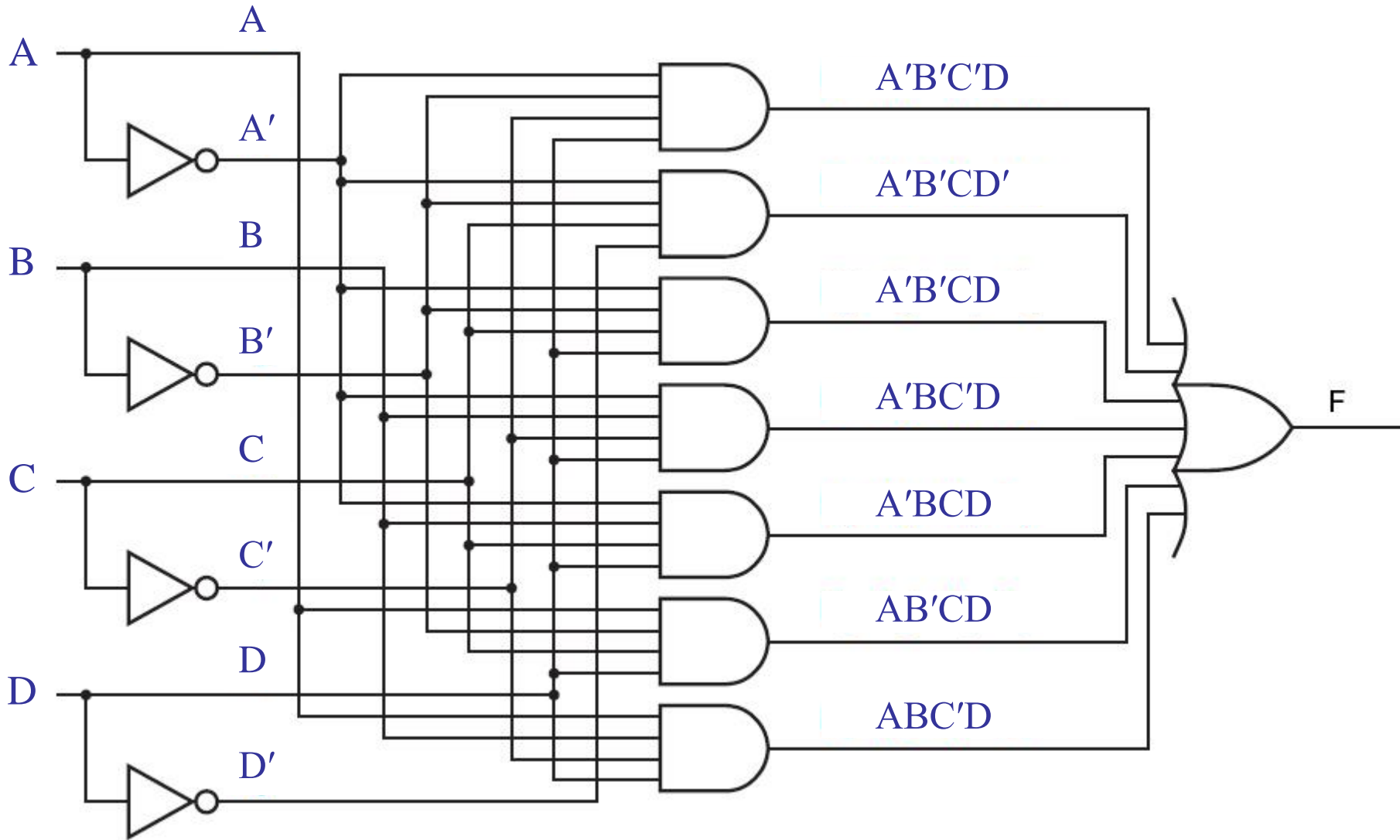
$$F = A'B'C'D + A'B'CD' + A'B'CD + A'BC'D + A'BCD + AB'CD + ABC'D$$



partial simplification:

$$F = A'B'C'D + A'B'CD' + A'B'CD + A'BC'D + A'BCD + AB'CD + ABC'D$$
$$= A'C'D + A'B'CD' + A'CD + AB'CD + ABC'D$$


$$F = A'D + A'B'CD' + AB'CD + ABC'D$$

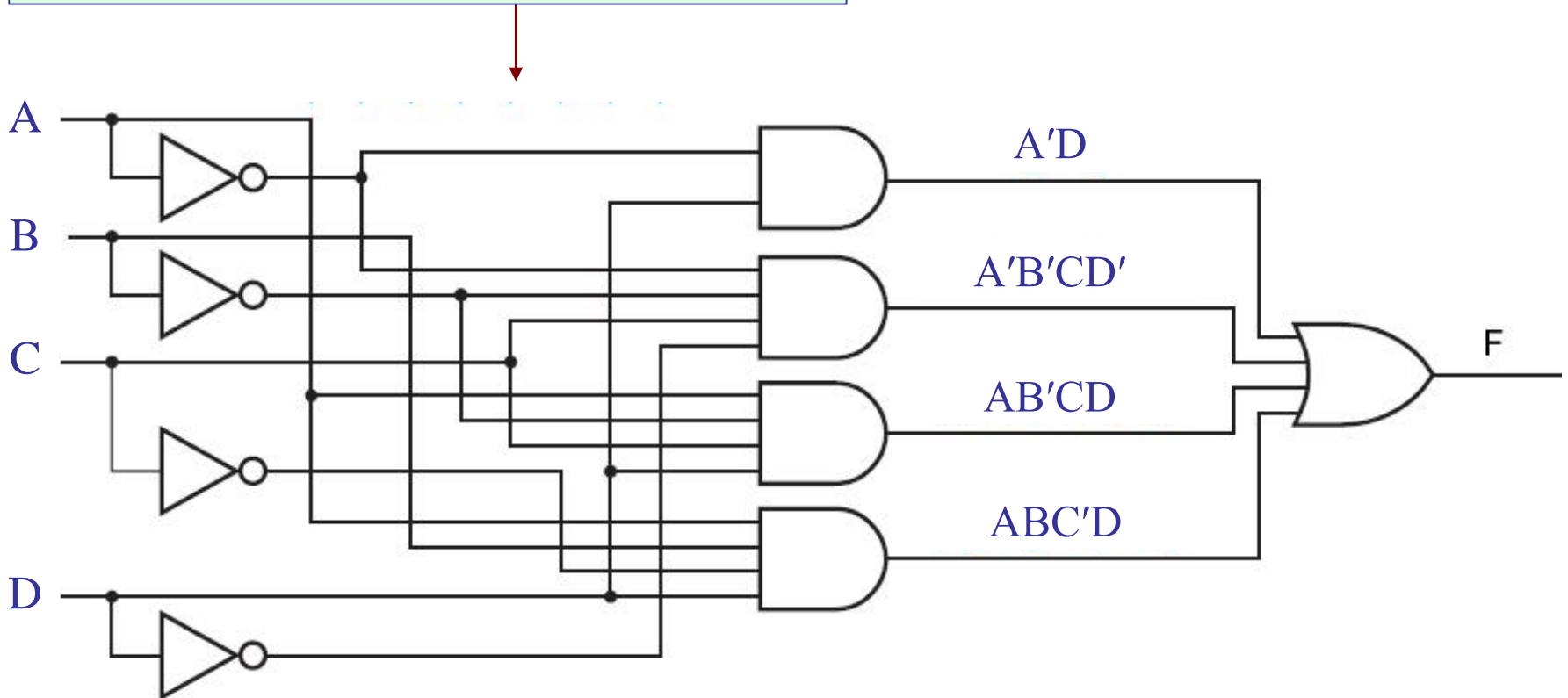

$$F = A'B'C'D + A'B'CD' + A'B'CD + A'BC'D + A'BCD + AB'CD + ABC'D$$

further simplification:


combine into

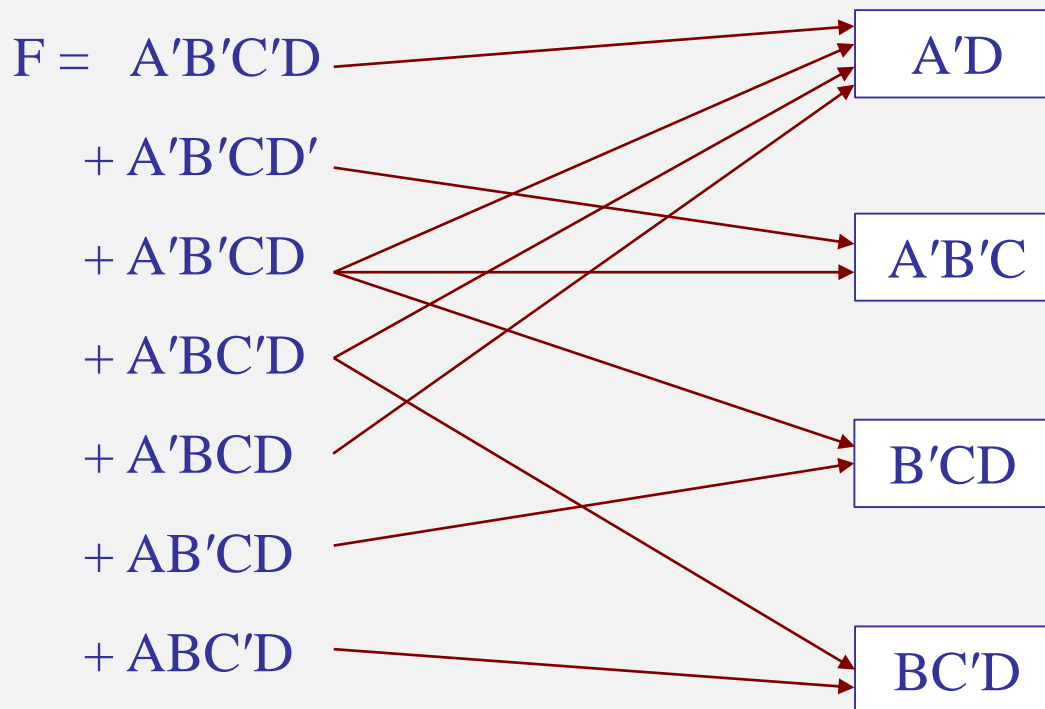

$$F = A'D + A'B'C + B'CD + BC'D$$

this is also the form  
obtained with K-maps

## Example 1 – prime number detector

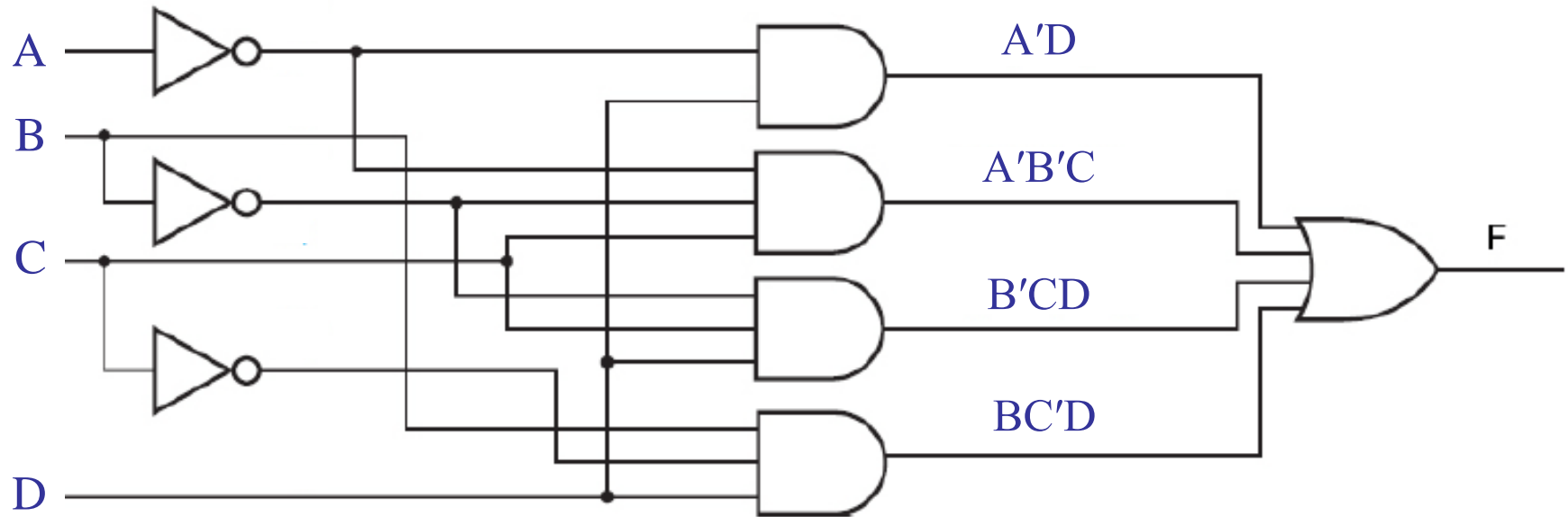

$$F = A'D + A'B'C + B'CD + BC'D$$

Matlab code:


```
[A,B,C,D] = a2d(0:15, 4);
```

```
F = (~A & D) | (~A & ~B & C) | (~B & C & D) | (B & ~C & D);
```

# Karnaugh map for prime number detector

$$F = A'B'C'D + A'B'CD' + A'B'CD + A'BC'D + A'BCD + AB'CD + ABC'D$$

$$F = A'D + A'B'C + B'CD + BC'D$$

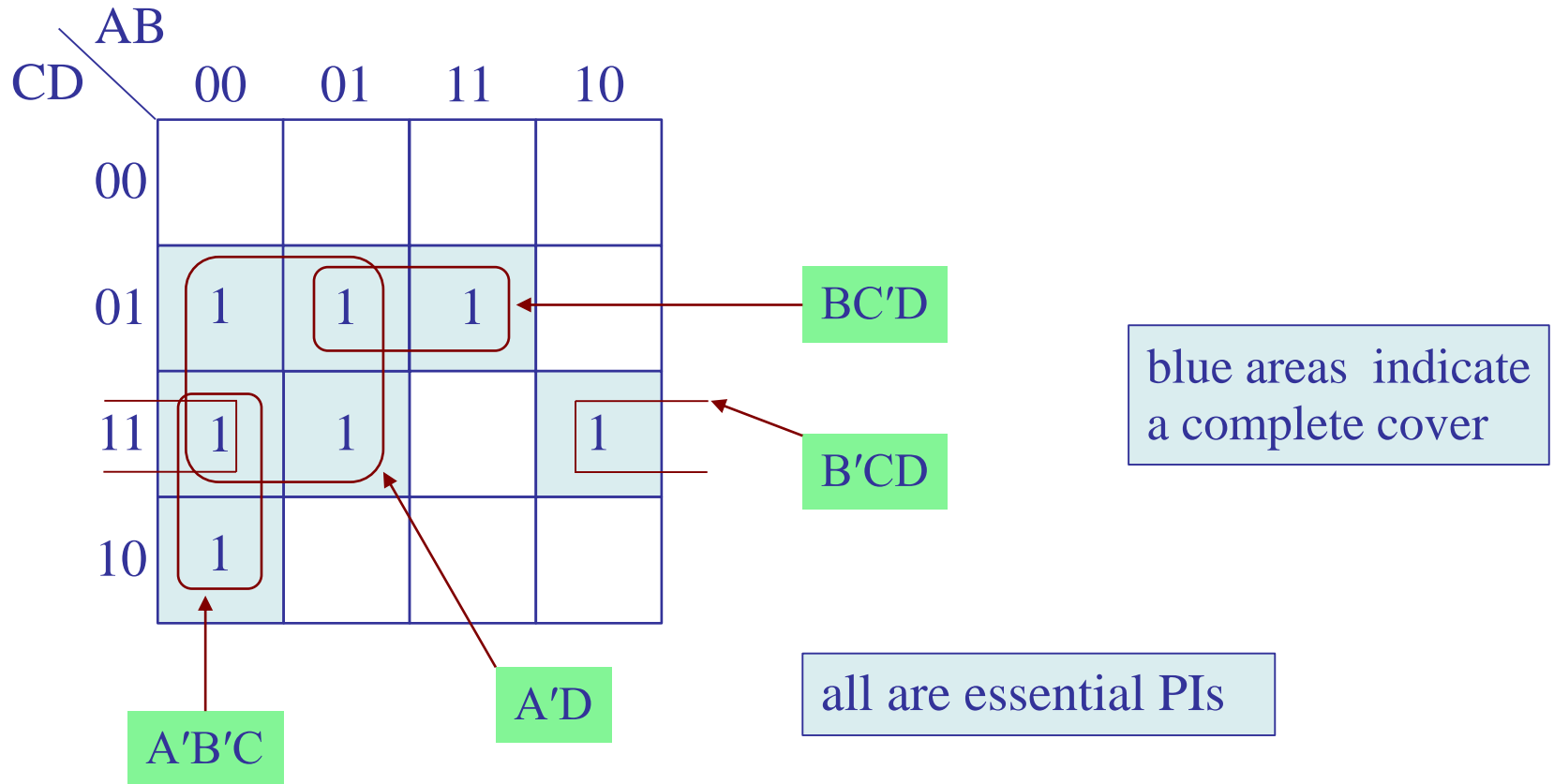

## 18. Combinational circuit synthesis

### Example 2 – alarm circuit

Wakerly, Sect.3.3.1

Design a home alarm circuit whose functional description is as follows:

The ALARM output is 1 if the PANIC-button input is 1, or if the ENABLE input is 1, the EXITING input is 0, and the house is not secure – the house is secure if the WINDOW, DOOR, and GARAGE inputs are all 1.

Translating this description into a Boolean algebraic expression, we have:

$$\text{SECURE} = \text{WINDOW} \cdot \text{DOOR} \cdot \text{GARAGE}$$

$$\text{ALARM} = \text{PANIC} + \text{ENABLE} \cdot \text{EXITING}' \cdot \text{SECURE}'$$

$$= \text{PANIC} + \text{ENABLE} \cdot \text{EXITING}' \cdot (\text{WINDOW} \cdot \text{DOOR} \cdot \text{GARAGE})'$$

$$= \text{PANIC} + \text{ENABLE} \cdot \text{EXITING}' \cdot (\text{WINDOW}' + \text{DOOR}' + \text{GARAGE}')$$


$$= \text{PANIC} + \text{ENABLE} \cdot \text{EXITING}' \cdot \text{WINDOW}'$$

$$+ \text{ENABLE} \cdot \text{EXITING}' \cdot \text{DOOR}'$$

$$+ \text{ENABLE} \cdot \text{EXITING}' \cdot \text{GARAGE}' = \text{sum-of-products form}$$

## 18. Combinational circuit synthesis

### Example 2 – alarm circuit

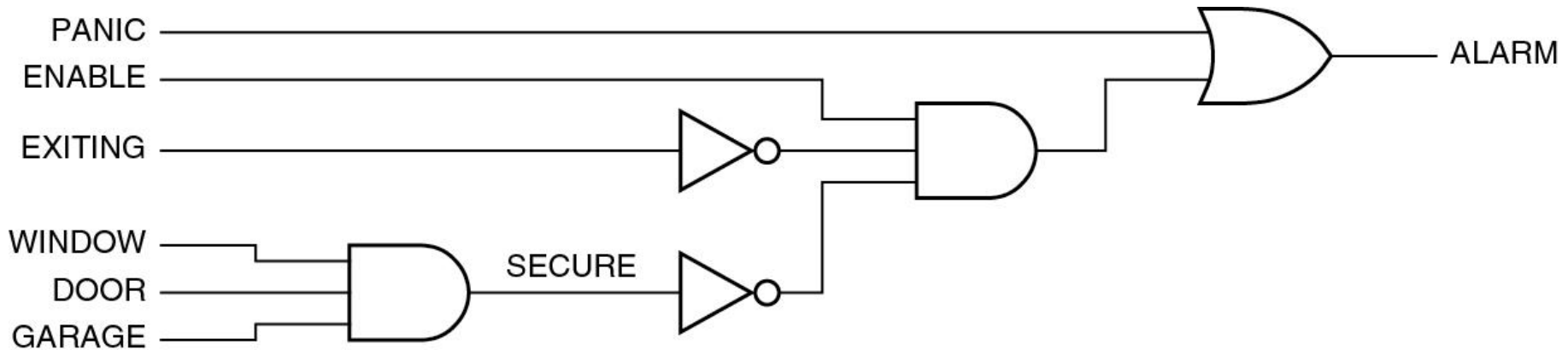


$$\text{SECURE} = \text{WINDOW} \cdot \text{DOOR} \cdot \text{GARAGE}$$

$$\text{ALARM} = \text{PANIC} + \text{ENABLE} \cdot \text{EXITING}' \cdot \text{SECURE}'$$

This design has a serious limitation: If the alarm is set off because the house is not secure, then the alarm will turn off when the house becomes secure again, even though the alarm is still enabled (e.g., someone may break into the house through an alarmed door, and cause the alarm to turn off by simply closing the door.) See [unit-8, Example-1](#) for a similar example and how to fix it by introducing memory into the system (with D flip-flops).



## Example 2 – alarm circuit

 


### alternative realization

$$\begin{aligned} \text{ALARM} = & \text{PANIC} + \text{ENABLE} \cdot \text{EXITING}' \cdot \text{WINDOW}' \\ & + \text{ENABLE} \cdot \text{EXITING}' \cdot \text{DOOR}' \\ & + \text{ENABLE} \cdot \text{EXITING}' \cdot \text{GARAGE}' = \text{sum-of-products form} \end{aligned}$$

## 18. Combinational circuit synthesis

### Example 3 – car dome light

 

Determine the Boolean function for a car dome light based on the following description [cf. Wakerly]:

The light has a 3-position switch such that the light turns on if the switch is in the ON position or if the middle switch MID is on and the door signal DOOR is also on when any door is open, otherwise the light is off when the switch is in the OFF position.

Translating this description into a Boolean algebraic expression, we have:

$$\text{LIGHT} = \text{ON} + \text{MID} \cdot \text{DOOR}$$

The circuit diagram with three inputs, ON, MID, DOOR, and one output LIGHT, is easily drawn using one AND gate and one OR gate.

see p.163 for an alternative realization, and K-map derivations with don't care entries

## 18. Combinational circuit synthesis

### Example 4 – equality test


Given two 2-bit numbers,  $\mathbf{a}$ ,  $\mathbf{b}$ , determine the Boolean function  $F$  that is equal to 1 when the two numbers are equal,  $\mathbf{a} = \mathbf{b}$ , and is equal to 0 otherwise.

Let the two bits of each number be,  $\mathbf{a} = (a_1 a_0)$ , and,  $\mathbf{b} = (b_1 b_0)$

$$F = (a_1 b_1 + a_1' b_1') \cdot (a_0 b_0 + a_0' b_0') = \text{XNOR}(a_1, b_1) \cdot \text{XNOR}(a_0, b_0)$$

The circuit diagram with four inputs,  $a_1$ ,  $a_0$ ,  $b_1$ ,  $b_0$ , and one output  $F$ , is easily drawn using one AND gate and two XNOR gates

 note,  $\text{xnor}(A,B) = 1$  only if  $A=B$  (either both 0 or both 1)  $\longrightarrow$



A	B	$AB + A'B'$
0	0	1
0	1	0
1	0	0
1	1	1

## 19. Combinational circuit minimization – Karnaugh maps

Karnaugh maps (K-maps) are **two-dimensional** representations of **truth tables** that provide an intuitive way to simplify a logic circuit and realize it with fewer logic gate operations.

See also,

[Karnaugh maps - Wikipedia](#)

Karnaugh maps are convenient for 1-5 input variables. For more variables see the following more advanced methods,

[logic minimization methods - Wikipedia](#)

[Quine-McCluskey algorithm - Wikipedia](#)

[Petrick's method - Wikipedia](#)

Consider a 3-variable function,  $F = f(A,B,C)$ . In an ordinary truth table, the possible values of the Boolean variables A,B,C, and the corresponding values of F, are listed in linear arithmetic progression such that the row numbers are represented by their **3-bit binary-pattern**, ABC, with each row corresponding to a particular minterm.

In each row, the function F is either 0 or 1, and the corresponding minterms for which  $F=1$  are added to represent the function as a sum-of-products.

In the **Karnaugh map**, on the other hand, the AB values are listed horizontally and the C values, vertically. However, the AB values are not listed in ordinary binary-order, but rather in **Gray-code order** such that only one bit changes in moving across from column to column. We recall from unit-2 that the ordinary 2-bit binary-order for AB is:

$$AB = 00, 01, 10, 11$$

whereas the Gray-code order is:

$$AB = 00, 01, 11, 10$$

**Gray-code order**  
→

C \ AB	00	01	11	10
0				
1				

ordinary truth table

row	A B C	minterms
0	0 0 0	$A'B'C'$
1	0 0 1	$A'B'C$
2	0 1 0	$A'BC'$
3	0 1 1	$A'BC$
4	1 0 0	$AB'C'$
5	1 0 1	$AB'C$
6	1 1 0	$ABC'$
7	1 1 1	$ABC$

Karnaugh map

Gray-code order

		AB			
		00	01	11	10
C	0	$A'B'C'$	$A'BC'$	$ABC'$	$AB'C'$
	1	$A'B'C$	$A'BC$	$ABC$	$AB'C$

For a particular function,  $F = f(A,B,C)$ , some of the indicated minterms will be replaced by 0's and some by 1's.

Two **adjacent** minterms, either **horizontally or vertically**, combine to a simpler expression by eliminating **that variable that has changed** across the pair of minterms.

This is a consequence of the identity,  $X + X' = 1$ .

The number of adjacent minterms must always be a **power of 2**, that is, the number of grouped minterms must be 1, 2, 4, for a 3-variable function, or, 1,2,4,8, for a 4-variable function.

Moreover, grouped adjacent minterms can overlap either horizontally or vertically.

To understand the simplification mechanism, consider a few examples of groupings.

two adjacent terms, horizontally or vertically

		AB			
		00	01	11	10
C	0	A'B'C'	A'BC'	ABC'	AB'C'
	1	A'B'C	A'BC	ABC	AB'C

$$A'BC' + ABC' = (A' + A)BC' = BC'$$

here, A is changing and was eliminated

		AB			
		00	01	11	10
C	0	A'B'C'	A'BC'	ABC'	AB'C'
	1	A'B'C	A'BC	ABC	AB'C

$$A'BC' + A'BC = A'B(C' + C) = A'B$$

here, C is changing and was eliminated



two horizontally overlapping groups of 2

		AB			
C		00	01	11	10
0	A'B'C'	A'BC'	ABC'	AB'C'	
1	A'B'C	A'BC	ABC	AB'C	

$$A'BC' + ABC' = (A' + A)BC' = BC'$$

$$ABC' + AB'C' = A(B + B')C' = AC'$$

$$\text{total} = BC' + AC'$$

Variable A varies across the first group, and B across the second. The ABC' term was **replicated** based on the property,  
 $X + X = X$

two vertically overlapping groups of 2

		AB			
C		00	01	11	10
0	A'B'C'	A'BC'	ABC'	AB'C'	
1	A'B'C	A'BC	ABC	AB'C	

replicated term

$$A'BC' + ABC' + A'BC' + A'BC =$$

$$= (A' + A)BC' + A'B(C' + C) =$$

$$= BC' + A'B$$

group of 4 horizontal/vertical terms

		AB			
		00	01	11	10
C	0	A'B'C'	A'BC'	ABC'	AB'C'
	1	A'B'C	A'BC	ABC	AB'C

$$\begin{aligned}
 &A'BC' + ABC' + A'BC + ABC \\
 &= (A' + A)BC' + (A' + A)BC \\
 &= BC' + BC = \\
 &= B(C' + C) = B
 \end{aligned}$$

The variable A varies horizontally, and C, vertically. Both A,C were eliminated.

group of 4 horizontally adjacent terms

		AB			
		00	01	11	10
C	0	A'B'C'	A'BC'	ABC'	AB'C'
	1	A'B'C	A'BC	ABC	AB'C

$$\begin{aligned}
 &A'B'C' + A'BC' + ABC' + AB'C' \\
 &= A'(B' + B)C' + A(B + B')C' \\
 &= A'C' + AC' = (A' + A)C' \\
 &= C'
 \end{aligned}$$

Variables A,B vary horizontally across adjacent cells, and were eliminated.

left and right edges **wrap** around

	AB			
C	00	01	11	10
0	$A'B'C'$	$A'BC'$	$ABC'$	$AB'C'$
1	$A'B'C$	$A'BC$	$ABC$	$AB'C$

$$\begin{aligned}
 &A'B'C' + AB'C' + A'B'C + AB'C \\
 &= (A' + A)B'C' + (A' + A)B'C \\
 &= B'C' + B'C = \\
 &= B'(C' + C) = B'
 \end{aligned}$$

Variable A varies horizontally, and C, vertically across the **wrapped square**, thus, both A,C were eliminated.

left and right edges **wrap** around


	AB			
C	00	01	11	10
0	$A'B'C'$	$A'BC'$	$ABC'$	$AB'C'$
1	$A'B'C$	$A'BC$	$ABC$	$AB'C$

$$\begin{aligned}
 &A'B'C' + AB'C' \\
 &= (A' + A) B'C' = B'C'
 \end{aligned}$$

Variable A varies horizontally across the **wrapped cells**, and was eliminated.

row	A B C D	minterms
0	0 0 0 0	$A'B'C'D'$
1	0 0 0 1	$A'B'C'D$
2	0 0 1 0	$A'B'CD'$
3	0 0 1 1	$A'B'CD$
4	0 1 0 0	$A'BC'D'$
5	0 1 0 1	$A'BC'D$
6	0 1 1 0	$A'BCD'$
7	0 1 1 1	$A'BCD$
8	1 0 0 0	$AB'C'D'$
9	1 0 0 1	$AB'C'D$
10	1 0 1 0	$AB'CD'$
11	1 0 1 1	$AB'CD$
12	1 1 0 0	$ABC'D'$
13	1 1 0 1	$ABC'D$
14	1 1 1 0	$ABCD'$
15	1 1 1 1	$ABCD$

4-variable Karnaugh map

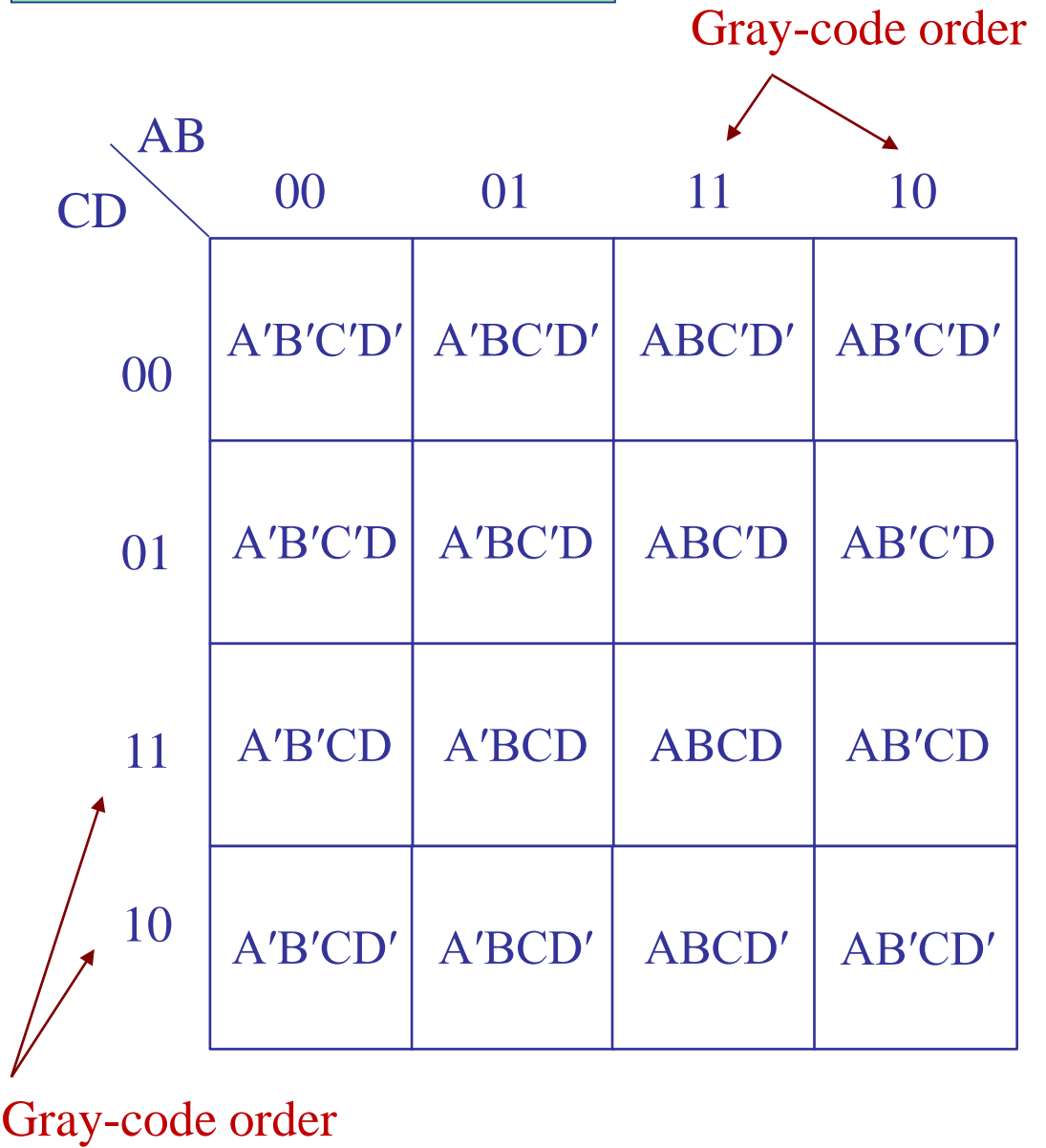

# Karnaugh map

truth-table row-number ordering

		A	
		0	1
B	0	0	2
	1	1	3

		AB			
		00	01	11	10
C	0	0	2	6	4
	1	1	3	7	5

		AB			
		00	01	11	10
CD	00	0	4	12	8
	01	1	5	13	9
	11	3	7	15	11
	10	2	6	14	10

## 4-variable Karnaugh map

CD \ AB		AB			
		00	01	11	10
CD	00	$A'B'C'D'$	$A'BC'D'$	$ABC'D'$	$AB'C'D'$
	01	$A'B'C'D$	$A'BC'D$	$ABC'D$	$AB'C'D$
	11	$A'B'CD$	$A'BCD$	$ABCD$	$AB'CD$
	10	$A'B'CD'$	$A'BCD'$	$ABCD'$	$AB'CD'$

simplifies into  $A'B$

variables C,D vary vertically across adjacent cells, and are eliminated.

## 4-variable Karnaugh map

AB \ CD	00	01	11	10
00	$A'B'C'D'$	$A'BC'D'$	$ABC'D'$	$AB'C'D'$
01	$A'B'C'D$	$A'BC'D$	$ABC'D$	$AB'C'D$
11	$A'B'CD$	$A'BCD$	$ABCD$	$AB'CD$
10	$A'B'CD'$	$A'BCD'$	$ABCD'$	$AB'CD'$

simplifies into  $= CD$

variables A,B vary horizontally across **adjacent** cells, and are eliminated.

# 4-variable Karnaugh map

CD \ AB		AB			
		00	01	11	10
CD	00	$A'B'C'D'$	$A'BC'D'$	$ABC'D'$	$AB'C'D'$
	01	$A'B'C'D$	$A'BC'D$	$ABC'D$	$AB'C'D$
	11	$A'B'CD$	$A'BCD$	$ABCD$	$AB'CD$
	10	$A'B'CD'$	$A'BCD'$	$ABCD'$	$AB'CD'$

simplifies into  $= A'B + CD$



# 4-variable Karnaugh map

		AB			
		00	01	11	10
CD	00	$A'B'C'D'$	$A'BC'D'$	$ABC'D'$	$AB'C'D'$
	01	$A'B'CD$	$A'BCD$	$ABC'D$	$AB'CD$
	11	$A'B'CD$	$A'BCD$	$ABCD$	$AB'CD$
	10	$A'B'CD'$	$A'BCD'$	$ABCD'$	$AB'CD'$

simplifies into  $= B'C' + BC$

## 4-variable Karnaugh map

		AB			
		00	01	11	10
CD	00	$A'B'C'D'$	$A'BC'D'$	$ABC'D'$	$AB'C'D'$
	01	$A'B'C'D$	$A'BC'D$	$ABC'D$	$AB'C'D$
	11	$A'B'CD$	$A'BCD$	$ABCD$	$AB'CD$
	10	$A'B'CD'$	$A'BCD'$	$ABCD'$	$AB'CD'$

simplifies into  $= BC' + AB$

always choose the **largest** sub-areas of adjacent cells, containing 2, 4, or 8 minterms

## 4-variable Karnaugh map

CD \ AB		AB			
		00	01	11	10
CD	00	$A'B'C'D'$	$A'BC'D'$	$ABC'D'$	$AB'C'D'$
	01	$A'B'C'D$	$A'BC'D$	$ABC'D$	$AB'C'D$
	11	$A'B'CD$	$A'BCD$	$ABCD$	$AB'CD$
	10	$A'B'CD'$	$A'BCD'$	$ABCD'$	$AB'CD'$

simplifies into =  $BD + AC$

# 4-variable Karnaugh map

simplifies into  $= ABD' + B'C'$

AB \ CD	00	01	11	10
00	$A'B'C'D'$	$A'BC'D'$	$ABC'D'$	$AB'C'D'$
01	$A'B'CD$	$A'BCD$	$ABC'D$	$AB'CD$
11	$A'B'CD$	$A'BCD$	$ABCD$	$AB'CD$
10	$A'B'CD'$	$A'BCD'$	$ABCD'$	$AB'CD'$

top/bottom and left/right edges **wrap** around

# 4-variable Karnaugh map

simplifies into  $= A'D' + B'C$

AB \ CD	00	01	11	10
00	$A'B'C'D'$	$A'BC'D'$	$ABC'D'$	$AB'C'D'$
01	$A'B'C'D$	$A'BC'D$	$ABC'D$	$AB'C'D$
11	$A'B'CD$	$A'BCD$	$ABCD$	$AB'CD$
10	$A'B'CD'$	$A'BCD'$	$ABCD'$	$AB'CD'$

top/bottom and left/right edges **w**rap around


# 4-variable Karnaugh map

AB \ CD	00	01	11	10
00	$A'B'C'D'$	$A'BC'D'$	$ABC'D'$	$AB'C'D'$
01	$A'B'C'D$	$A'BC'D$	$ABC'D$	$AB'C'D$
11	$A'B'CD$	$A'BCD$	$ABCD$	$AB'CD$
10	$A'B'CD'$	$A'BCD'$	$ABCD'$	$AB'CD'$

top/bottom and left/right corners **wrap** around

simplifies into  $B'D'$

# 4-variable Karnaugh map

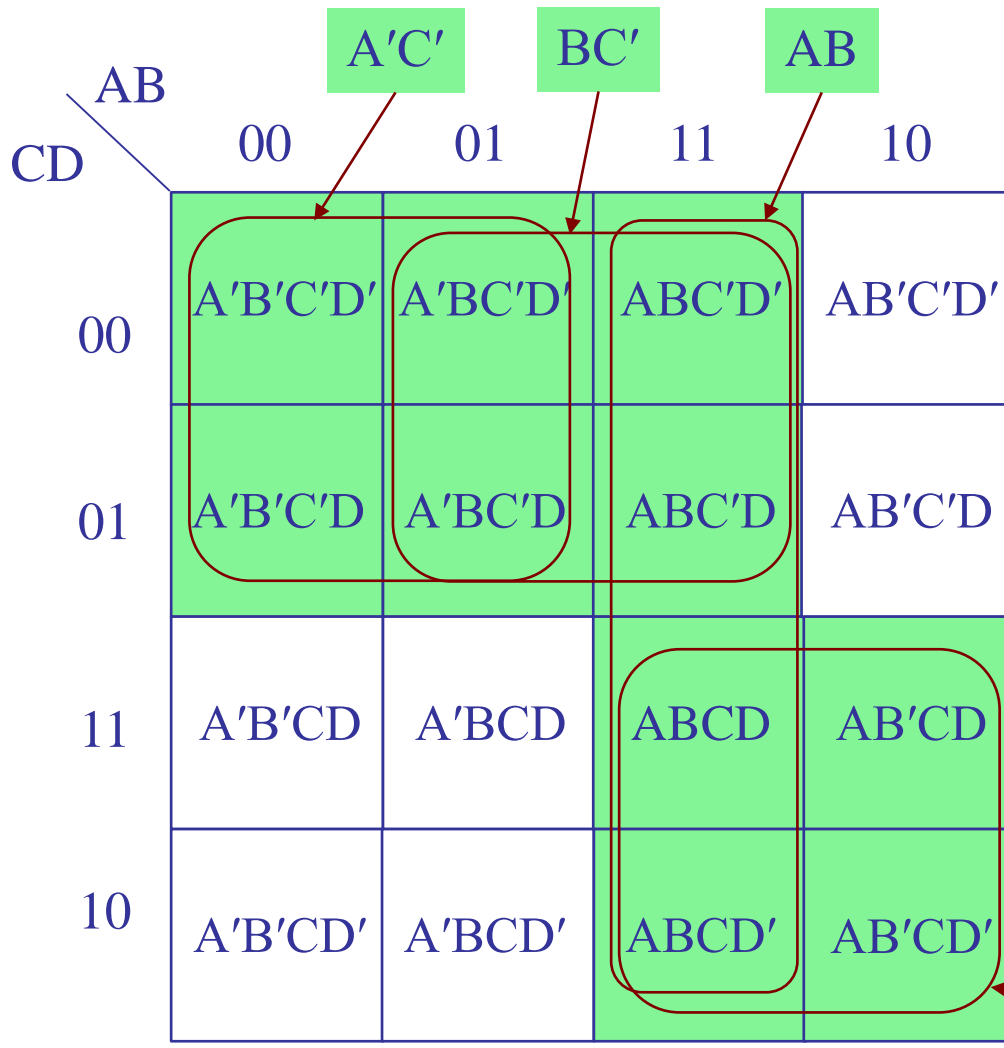

always choose the **largest** sub-areas of adjacent cells, containing 2, 4, or, 8 minterms

simplifies into  
 $= A'C' + AC + BC'$   
 or, into  
 $= A'C' + AC + AB$

the BC' and AB areas are partially **covered** by each other, and by the other areas A'C' and AC, so only one of them, BC' or AB, needs to be included – including both would be redundant

**AC**

# 4-variable Karnaugh map

AB		CD			
		00	01	11	10
CD	00	$A'B'C'D'$	$A'BC'D'$	$ABC'D'$	$AB'C'D'$
	01	$A'B'C'D$	$A'BC'D$	$ABC'D$	$AB'C'D$
	11	$A'B'CD$	$A'BCD$	$ABCD$	$AB'CD$
	10	$A'B'CD'$	$A'BCD'$	$ABCD'$	$AB'CD'$

$B'D'$  essential PI

simplifies into  
 $= B'D' + A'C + BCD$

top/bottom and left/right corners **wrap** around

$A'C$   
 $BCD$   
 essential PI

always choose the **largest** sub-areas of adjacent cells, containing 2, 4, or, 8 minterms



# 4-variable Karnaugh map

	AB			
CD	00	01	11	10
00	$A'B'C'D'$	$A'BC'D'$	$ABC'D'$	$AB'C'D'$
01	$A'B'C'D$	$A'BC'D$	$ABC'D$	$AB'C'D$
11	$A'B'CD$	$A'BCD$	$ABCD$	$AB'CD$
10	$A'B'CD'$	$A'BCD'$	$ABCD'$	$AB'CD'$

simplifies into  
 $F = B'C + CD' + BC'D + A'C$

essential PIs

simplest non-essential PI

$BC'D$  essential PI

left/right corners **wrap** around

$B'C$  essential PI

$CD'$

$A'C$

$A'BD$

essential PI

non-essential PIs

## Nomenclature

**implicant:** a minterm or sum of minterms appearing in a function  $F$ , if an implicant evaluates to 1, then so does  $F$  as a whole, i.e., if, **implicant=1**, then it implies,  **$F=1$**

**prime implicant:** a simplified implicant that cannot be combined into another implicant that has fewer number of literals.

**covers:** all implicants that account for all possible evaluations of the function into  $F=1$  (i.e., all the 1's in a Karnaugh map).


**essential prime implicant:** a prime implicant that contains an  $F=1$  minterm that is not included in any other prime implicant, all essential prime implicants **must be included** in the cover of the function.

In addition to the essential PIs, it may be necessary to include possible non-essential PIs in order to achieve a **complete cover**, (if there are several such possibilities, one could choose the one that has the smallest number of literals.

blue areas indicate a complete cover


simplifies into =  $A'D + ABD' + AC'D'$

(non-prime) implicant

 

essential prime implicants

essential prime implicants

 

simplifies into =  $A'B' + BD$   
 =  $A'B' + BD + A'D$  = with all PIs + consensus

non-essential PI, already covered by other essential PIs, consensus term

## Summary

Karnaugh map minimization steps for combinational functions of 2, 3, or, 4 Boolean variables:

1. Place 1's in the squares of the K-map for those minterms where  $F=1$ .
2. For each such minterm, find the **largest** sub-area containing that minterm – these are the **prime implicants**. The number of elements in such subareas must be a power of 2, e.g., 2,4,8,etc.
3. Identify the **essential prime implicants** covering those minterms that are not covered by any other prime implicant.
4. All of the essential prime implicants must be included in the final simplified expression, and in addition, include any other prime implicants so that **all** minterms of the function are covered.
5. Any particular minterm may be covered by more than one prime implicant, but all minterms must be covered.

## Karnaugh map examples – 1

Previously (in Example 3) we considered the simplification of the truth table function given in **Table 3-5** of the Wakerly text, and demonstrated the equivalence of the following expressions for  $F$  as a function of the Boolean variables  $X, Y, Z$ ,


$$(1) F = X'Y'Z' + XY'Z' + X'YZ + XYZ + XYZ'$$

$$(2) F = Y'Z' + YZ + XZ'$$

$$(3) F = Y'Z' + YZ + XY$$

truth table


X	Y	Z	F
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

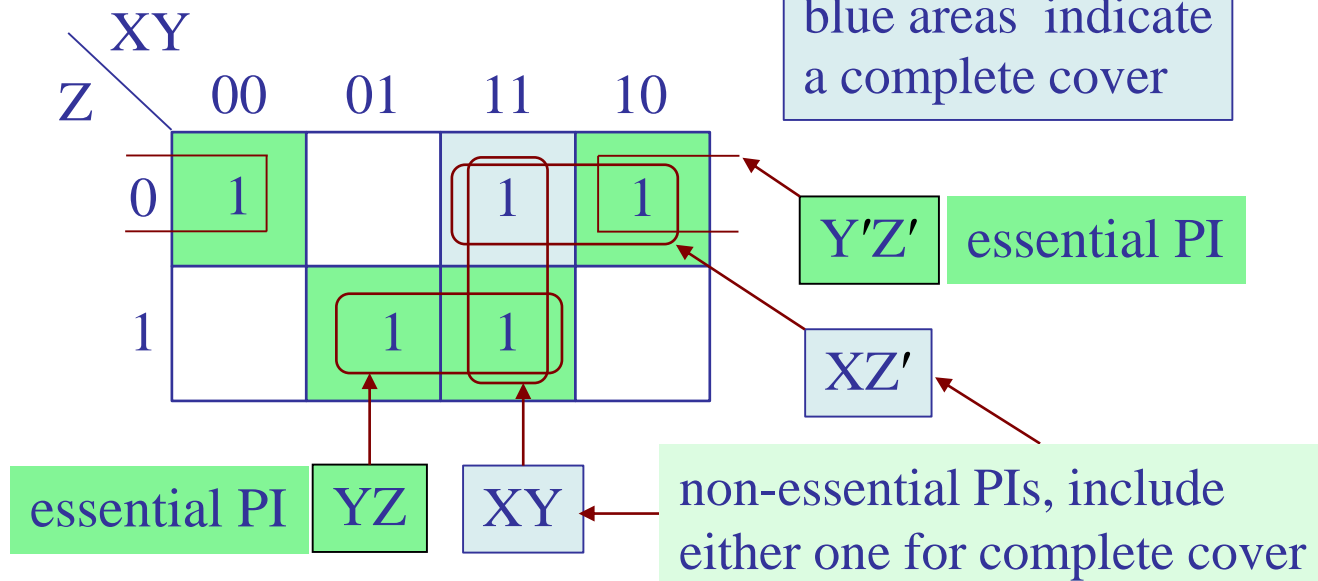

# Karnaugh map examples – 1

alternative way of arranging the variables in the K-map – the final answer is the same

truth table			
X	Y	Z	F
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

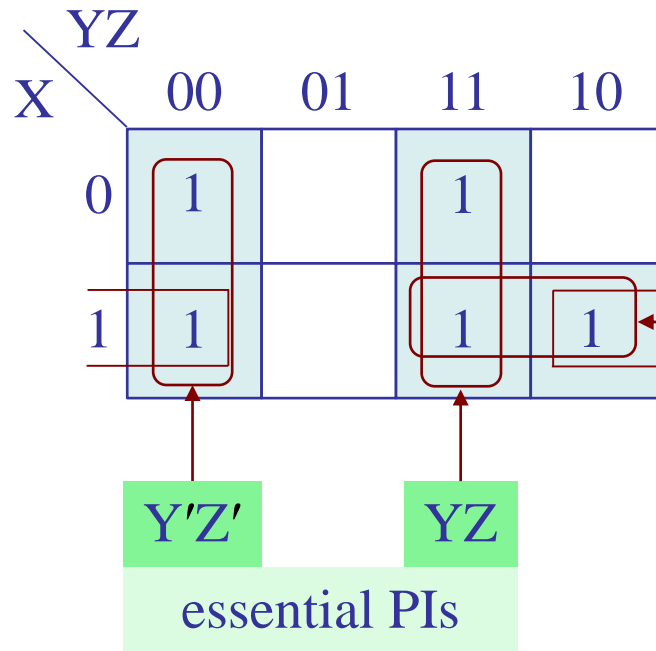

$$F = Y'Z' + YZ + XZ'$$

$$F = Y'Z' + YZ + XY$$

**XY**  
include either one  
for complete cover

**XZ'**

blue areas indicate  
a complete cover

# Karnaugh map examples – 1


yet, another way of drawing the K-map

$$F = Y'Z' + YZ + XZ'$$

$$F = Y'Z' + YZ + XY$$

truth table

X	Y	Z	F
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

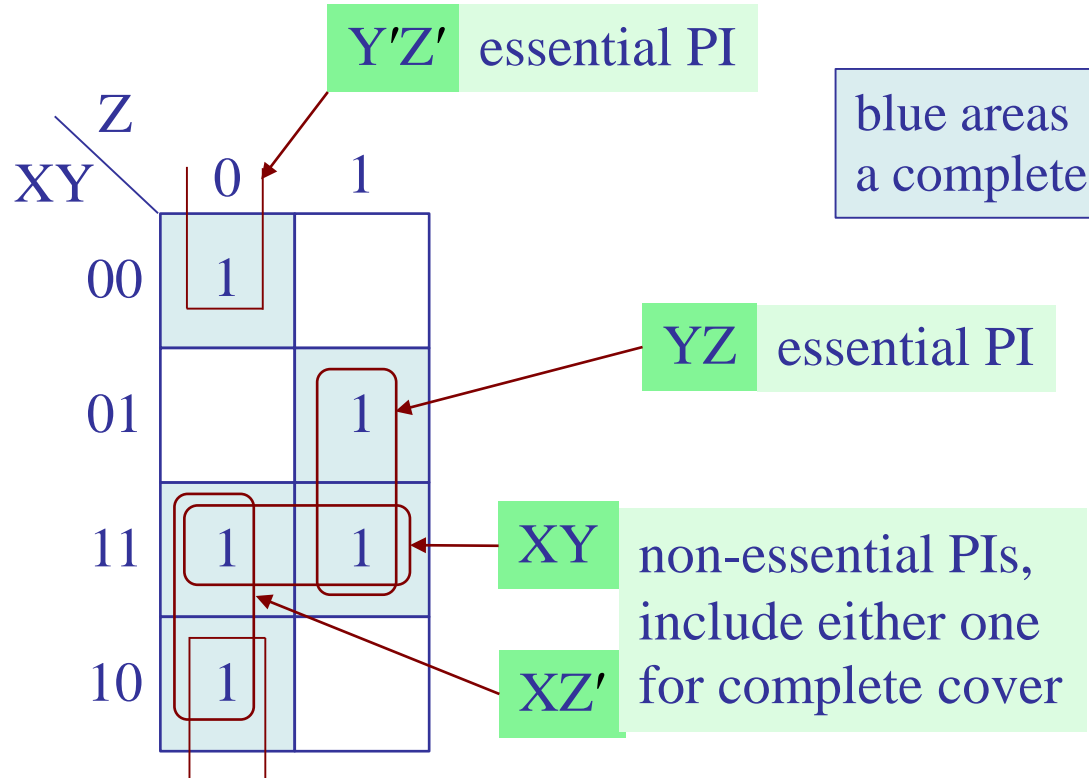

blue areas indicate a complete cover



## Karnaugh map examples – 2

Truth table of multiplexer function and its simplification:

$$Z = S' \cdot A \cdot B' + S' \cdot A \cdot B + S \cdot A' \cdot B + S \cdot A \cdot B$$

$$= S' \cdot A + S \cdot B$$

	S	A	B	Z
	0	0	0	0
	0	0	1	0
$S' \cdot A \cdot B'$	0	1	0	1
$S' \cdot A \cdot B$	0	1	1	1
	1	0	0	0
$S \cdot A' \cdot B$	1	0	1	1
	1	1	0	0
$S \cdot A \cdot B$	1	1	1	1

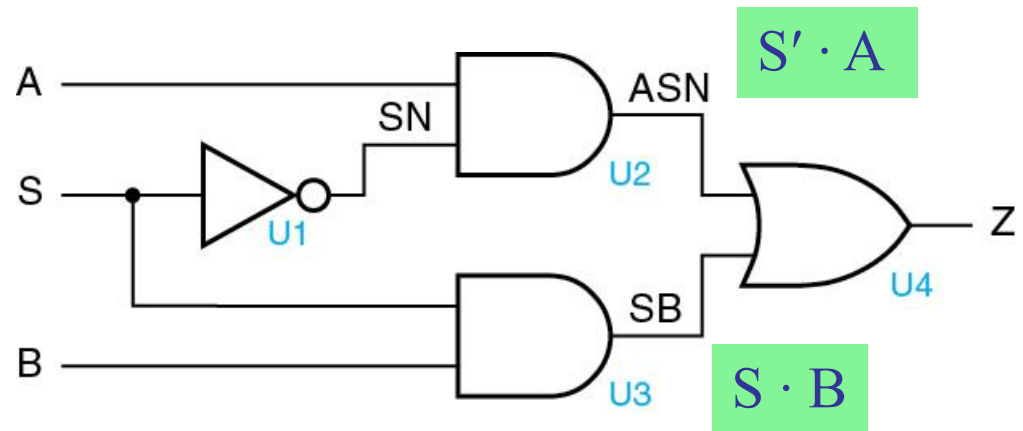 




## Karnaugh map examples – 2

Truth table of multiplexer function and its simplification:

$$Z = S' \cdot A \cdot B' + S' \cdot A \cdot B + S \cdot A' \cdot B + S \cdot A \cdot B$$

$$= S' \cdot A + S \cdot B = S' \cdot A + S \cdot B + A \cdot B$$

S	A	B	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

 

$A \cdot B$

non-essential PI,  
consensus term

$S' \cdot A$

essential PI

$S \cdot B$

essential PI

blue areas indicate  
a complete cover

## Karnaugh map examples – 3


Previously (in Example 4), we considered the truth table given below [ref. A. F. Kana], and showed the equivalence of the following expressions for F as a function of the Boolean variables X, Y, Z,

truth table			
X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$(1) F = X'YZ + XY'Z + XYZ' + XYZ$$

$$(2) F = XY + YZ + XZ$$

 F may be viewed as implementing a voting **majority gate**, that is,  $F=1$ , if **two or more** input variables are 1



blue areas indicate a complete cover

all three are essential PIs


## Karnaugh map examples – 4

Previously (in Example 5) we showed the equivalence of the following two expressions:

$$F = X'Y + XY' + XY$$

$$F = X + Y$$

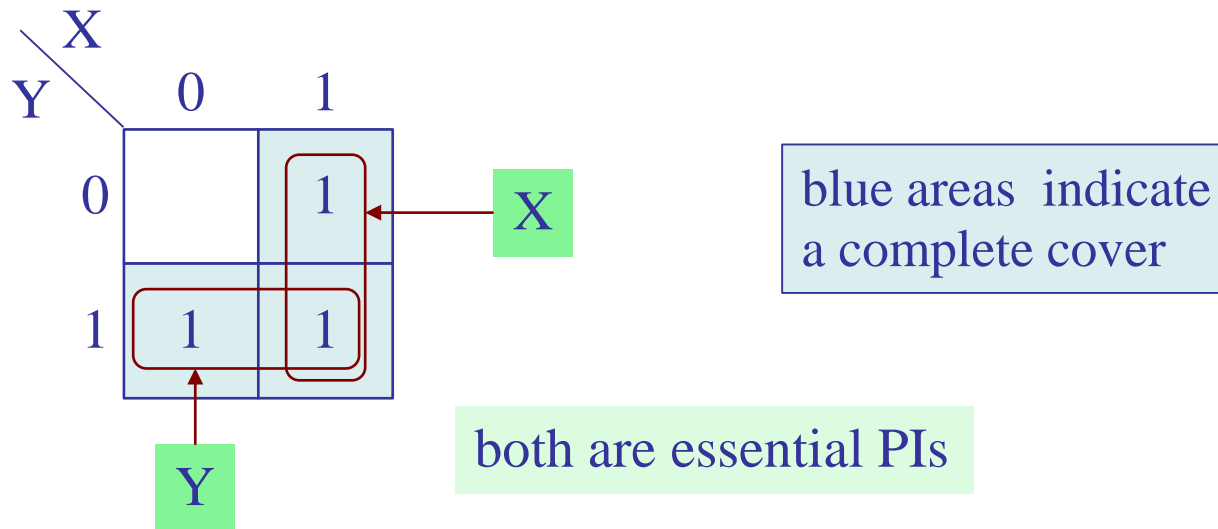It can be understood simply by a 2-variable K-map.




## Karnaugh map examples – 5

Previously (in Example 6), we showed the equivalence of the following two 4-variable expressions [ref. A. F. Kana],

$$F = A'BC'D + A'BCD + ABC'D' + ABC'D + ABCD + ABCD' + AB'CD + AB'CD'$$

$$F = BD + AB + AC$$

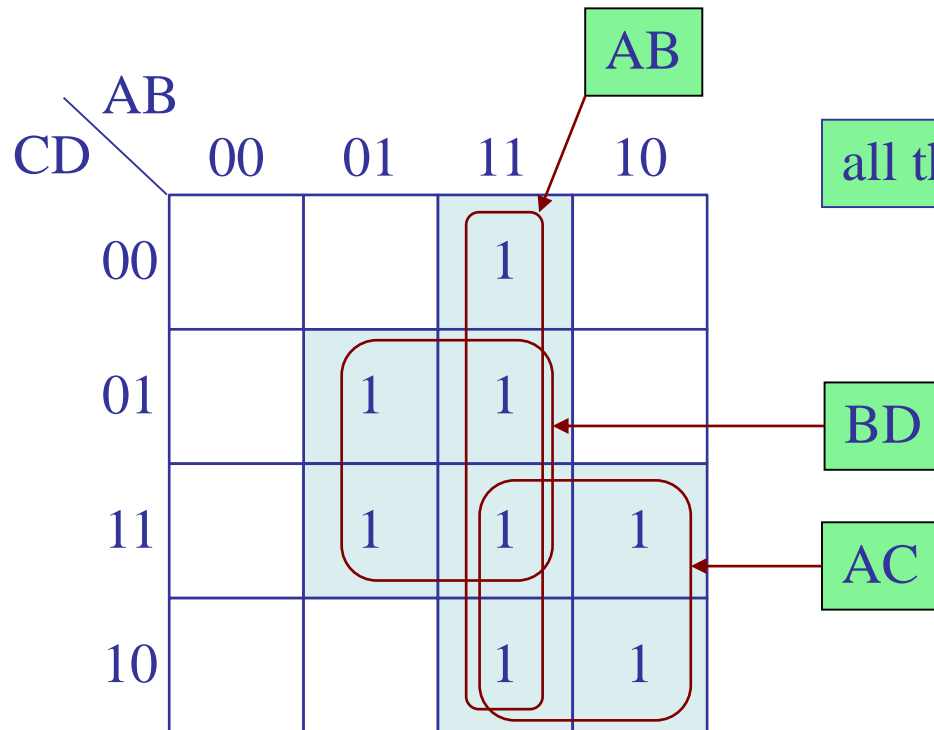

all three are essential PIs

blue areas indicate a complete cover

example of implicant

$$\begin{aligned} \text{if } AB = 1, \text{ then, } A=1, B=1, A'=0, B'=0 \\ F &= C'D' + C'D + CD + CD' \\ &= (C + C')(D + D') = 1 \cdot 1 = 1 \end{aligned}$$


## Karnaugh map examples – 6

Previously, we arrived at the following equivalent expressions for a **prime number detector**,

$$F = \sum_{A,B,C,D}(1,2,3,5,7,11,13) =$$

$$F = A'B'C'D + A'B'CD' + A'B'CD + A'BC'D + A'BCD + AB'CD + ABC'D$$


$$F = A'D + A'B'C + B'CD + BC'D$$

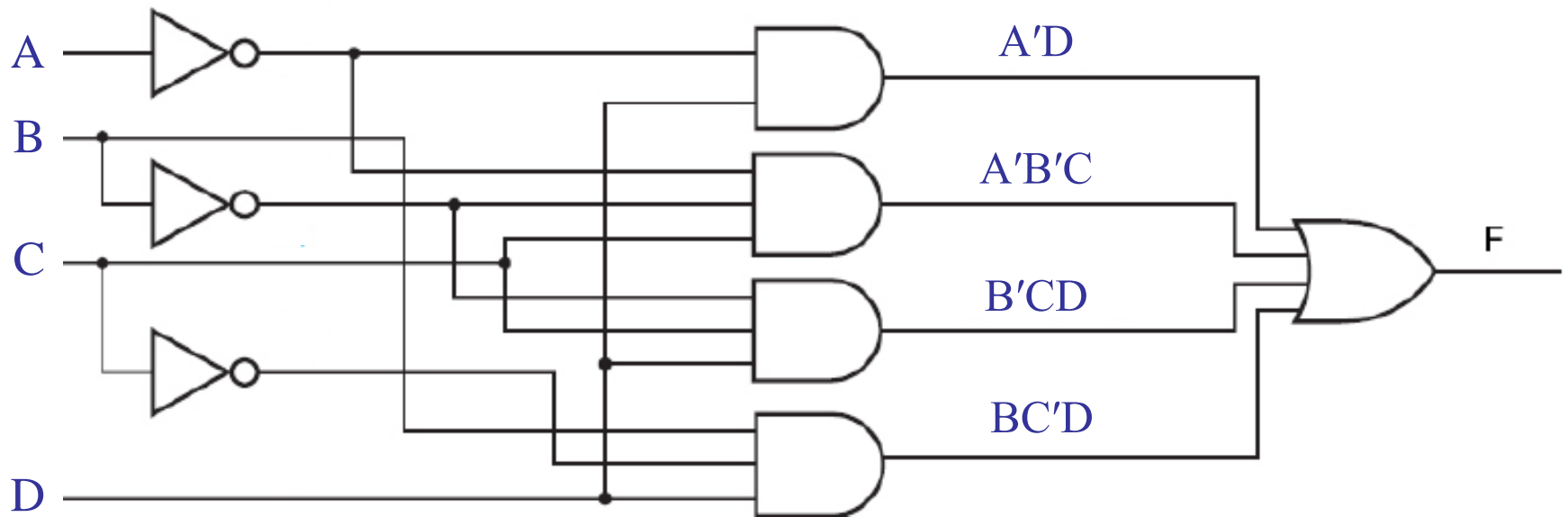

## Karnaugh map examples – 6

$$F = A'B'C'D + A'B'CD' + A'B'CD + A'BC'D + A'BCD + AB'CD + ABC'D$$


$$F = A'D + A'B'C + B'CD + BC'D$$

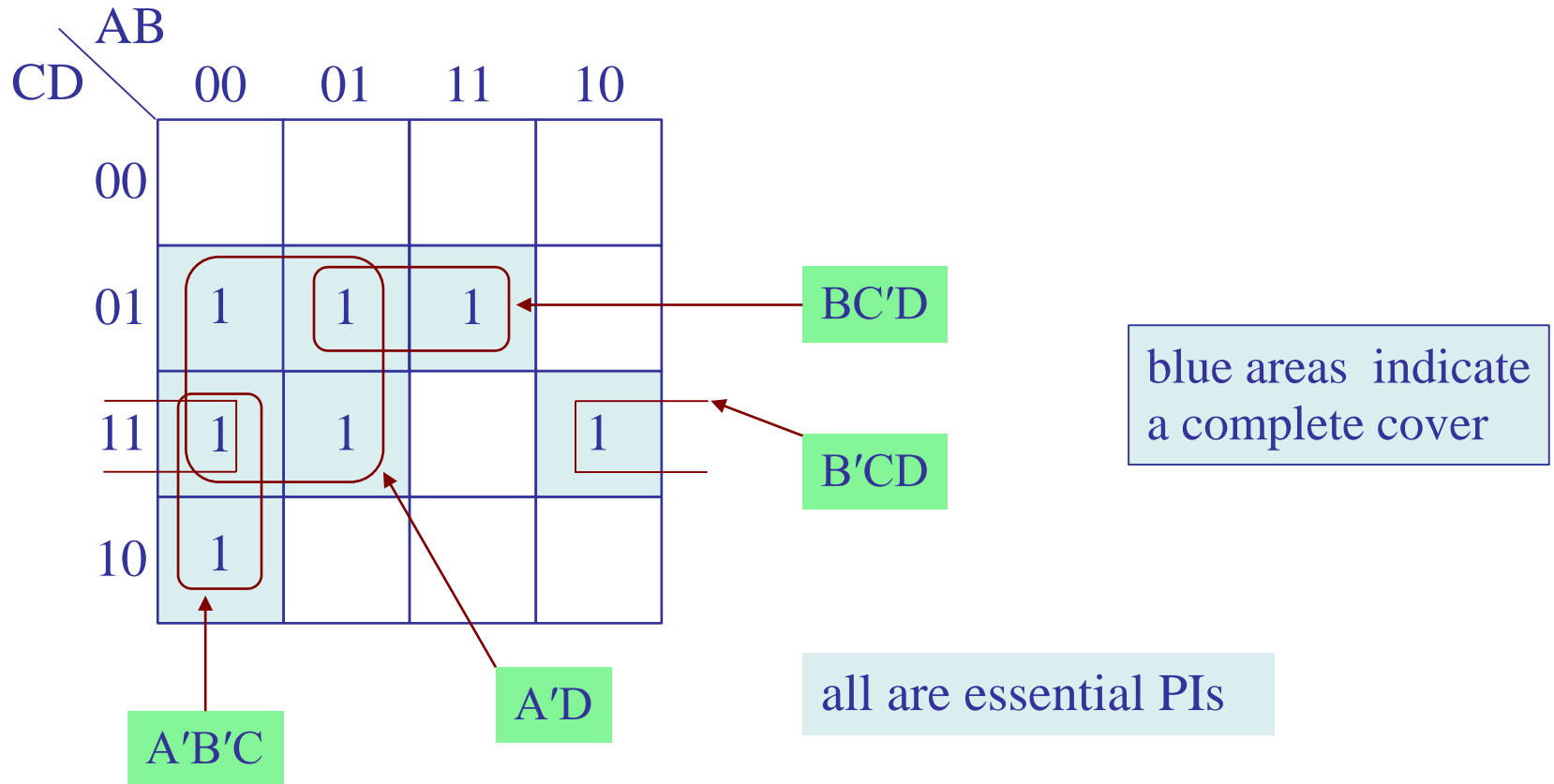

## Karnaugh map examples – 7

row	A B C D	F	F'
0	0 0 0 0	1	0
1	0 0 0 1	0	1
2	0 0 1 0	1	0
3	0 0 1 1	0	1
4	0 1 0 0	1	0
5	0 1 0 1	1	0
6	0 1 1 0	1	0
7	0 1 1 1	1	0
8	1 0 0 0	1	0
9	1 0 0 1	0	1
10	1 0 1 0	1	0
11	1 0 1 1	0	1
12	1 1 0 0	1	0
13	1 1 0 1	0	1
14	1 1 1 0	1	0
15	1 1 1 1	1	0

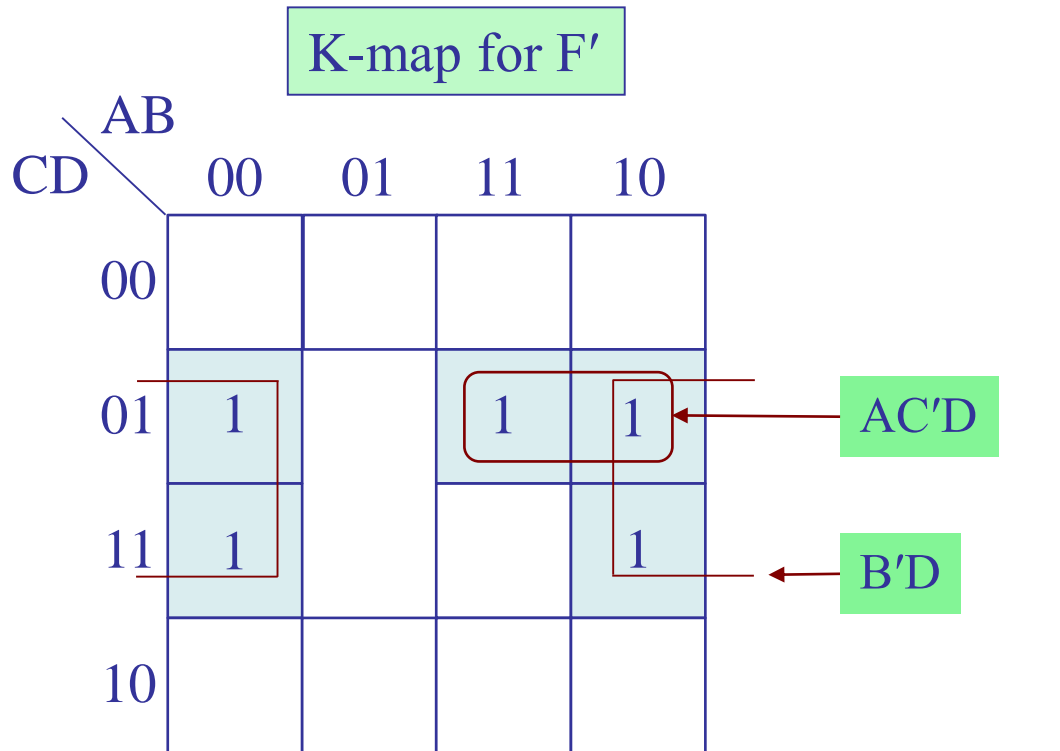Determine the minimum **product-of-sums** expression for the function F with the following truth table.



$$F' = B'D + AC'D$$

$$F = (B + D')(A' + C + D')$$

De Morgan


## Karnaugh map examples – 8

Using K-maps, determine a simplified sum-of-products form for the function,

$$F = XY + ZX' + ZY'$$

truth table

X	Y	Z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 

$$F = XY + Z$$

```
[x,y,z] = a2d(0:7,3);  
f = (x&y) | (z&~x) | (z&~y);  
[x,y,z,f]
```




## Karnaugh map examples – 9

How to handle **incompletely specified**, or **don't care**, entries in the truth table.

**rule:** treat them as 1's in the minterm form

row	A B C D	F
0	0 0 0 0	1
1	0 0 0 1	0
2	0 0 1 0	1
3	0 0 1 1	1
4	0 1 0 0	0
5	0 1 0 1	1
6	0 1 1 0	1
7	0 1 1 1	1
8	1 0 0 0	1
9	1 0 0 1	1
10	1 0 1 0	x
11	1 0 1 1	x
12	1 1 0 0	x
13	1 1 0 1	x
14	1 1 1 0	x
15	1 1 1 1	x

 


$$F = B'D' + BD + A + C$$

# Karnaugh map examples – 9

$[A,B,C,D] = \text{a2d}(0:15,4);$   
 $F = (\sim B \ \& \ \sim D) \mid (B \ \& \ D) \mid A \mid C;$   
 $[A,B,C,D,F]$

$$F = B'D' + BD + A + C$$

row	A	B	C	D	F
0	0	0	0	0	1
1	0	0	0	1	0
2	0	0	1	0	1
3	0	0	1	1	1
4	0	1	0	0	0
5	0	1	0	1	1
6	0	1	1	0	1
7	0	1	1	1	1
8	1	0	0	0	1
9	1	0	0	1	1
10	1	0	1	0	1
11	1	0	1	1	1
12	1	1	0	0	1
13	1	1	0	1	1
14	1	1	1	0	1
15	1	1	1	1	1

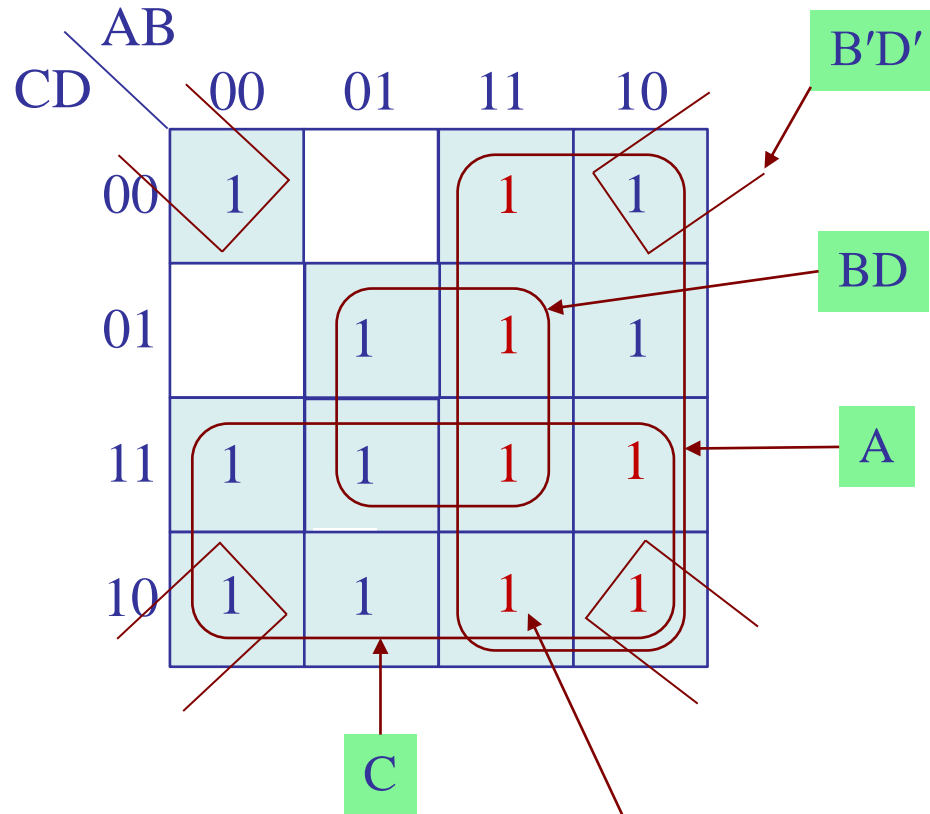

don't cares are effectively replaced by 1's


## Karnaugh map examples – 10

Car dome light example (from p.122)

The light has a 3-position switch such that the light turns on if the switch is in the ON position or if the middle switch MID is on and the door signal DOOR is also on when any door is open, otherwise the light is off when the switch is in the OFF position.

Translating this description into a Boolean algebraic expression, we have:
 
$$\text{LIGHT} = \text{ON} + \text{MID} \cdot \text{DOOR}$$




OFF	MID	ON	DOOR	LIGHT
0	0	0	0	x
0	0	0	1	x
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	x
0	1	1	1	x
1	0	0	0	0
1	0	0	1	0
1	0	1	0	x
1	0	1	1	x
1	1	0	0	x
1	1	0	1	x
1	1	1	0	x
1	1	1	1	x

x's denote **don't care or unrealizable** entries because the switch can only be at one of 3 positions

# Karnaugh map examples – 10

OFF	MID	ON	DOOR	LIGHT
0	0	0	0	x
0	0	0	1	x
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	x
0	1	1	1	x
1	0	0	0	0
1	0	0	1	0
1	0	1	0	x
1	0	1	1	x
1	1	0	0	x
1	1	0	1	x
1	1	1	0	x
1	1	1	1	x

don't cares are treated as 1's

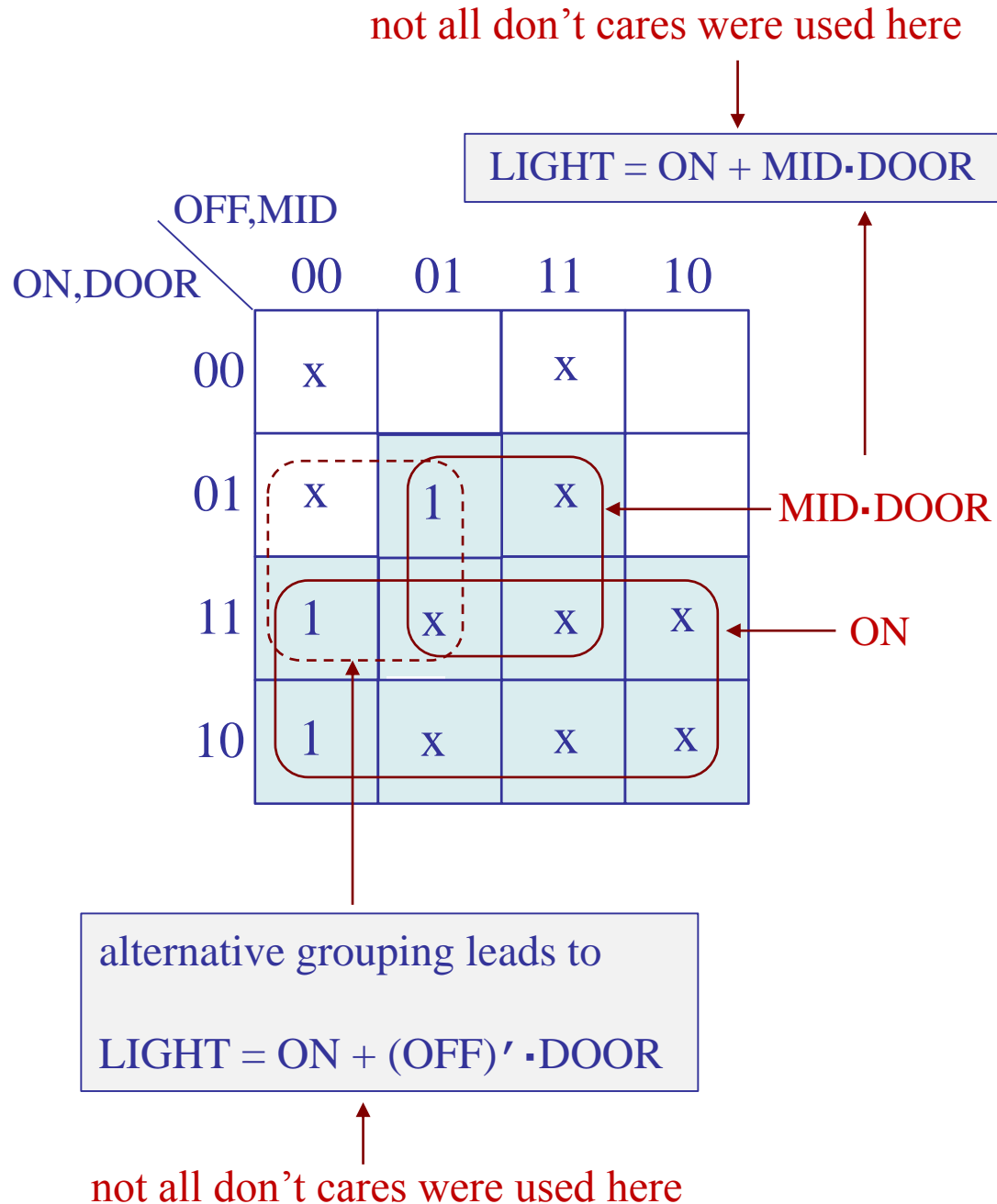

## Karnaugh map examples – 10

OFF	MID	ON	DOOR	LIGHT	L1	L2
0	0	0	0	x	0	0
0	0	0	1	x	0	1
0	0	1	0	1	1	1
0	0	1	1	1	1	1
0	1	0	0	0	0	0
0	1	0	1	1	1	1
0	1	1	0	x	1	1
0	1	1	1	x	1	1
1	0	0	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	x	1	1
1	0	1	1	x	1	1
1	1	0	0	x	0	0
1	1	0	1	x	1	0
1	1	1	0	x	1	1
1	1	1	1	x	1	1

$$L1 = ON + MID \cdot DOOR$$

$$L2 = ON + (OFF)' \cdot DOOR$$

**% MATLAB code:**

```
[off,mid,on,door] = a2d(0:15,4);
```

```
L1 = on | (mid & door);
```

```
L2 = on | (~off & door);
```

```
[off,mid,on,door,L1,L2] % print
```

don't cares are treated as 1's


because not all don't cares were used in deriving L1 and L2, the full L1 and L2 columns are different. However, they agree on the **relevant/realizable** part of the truth table (shown in red)

# Karnaugh map examples – 11

# lab-2 derivations using K-maps

row	a	b	c	d	F
0	0	0	0	0	0
1	0	0	0	1	0
2	0	0	1	0	0
3	0	0	1	1	0
4	0	1	0	0	1
5	0	1	0	1	1
6	0	1	1	0	0
7	0	1	1	1	0
8	1	0	0	0	0
9	1	0	0	1	0
10	1	0	1	0	0
11	1	0	1	1	1
12	1	1	0	0	1
13	1	1	0	1	1
14	1	1	1	0	0
15	1	1	1	1	1

$$F = bc' + acd$$

 


```
[a,b,c,d] = a2d(0:15,4);
F = (b & ~c) | (a & c & d);
[a,b,c,d,F]      % print truth table
```

# Karnaugh map examples – 11

## lab-2 derivations using K-maps

row	a	b	c	d	F
0	0	0	0	0	0
1	0	0	0	1	0
2	0	0	1	0	0
3	0	0	1	1	0
4	0	1	0	0	1
5	0	1	0	1	1
6	0	1	1	0	0
7	0	1	1	1	0
8	1	0	0	0	0
9	1	0	0	1	0
10	1	0	1	0	0
11	1	0	1	1	1
12	1	1	0	0	1
13	1	1	0	1	1
14	1	1	1	0	0
15	1	1	1	1	1

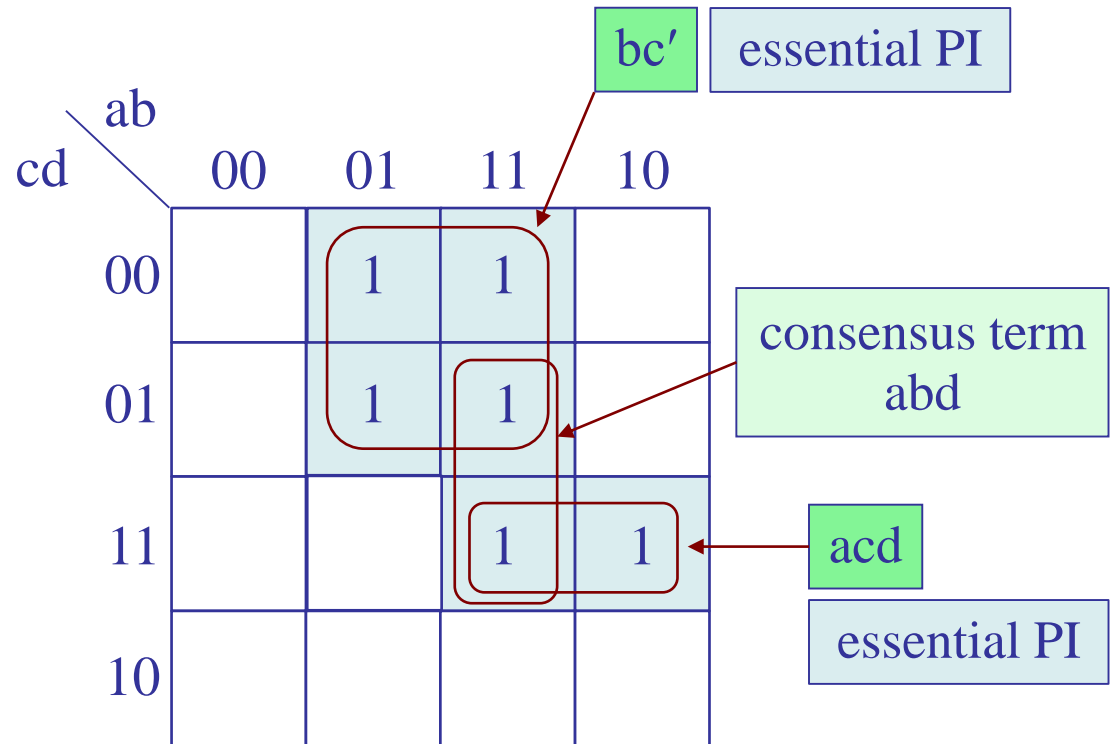

$$F = bc' + acd$$

$$F = bc' + acd + abd$$


$$F = a'bc'd' + a'bc'd + ab'cd + abc'd' + abc'd + abcd$$

canonical minterm SOP expansion

# Karnaugh map examples – 11

## lab-2 derivations using K-maps

row	a	b	c	d	F
0	0	0	0	0	0
1	0	0	0	1	0
2	0	0	1	0	0
3	0	0	1	1	0
4	0	1	0	0	1
5	0	1	0	1	1
6	0	1	1	0	0
7	0	1	1	1	0
8	1	0	0	0	0
9	1	0	0	1	0
10	1	0	1	0	0
11	1	0	1	1	1
12	1	1	0	0	1
13	1	1	0	1	1
14	1	1	1	0	0
15	1	1	1	1	1

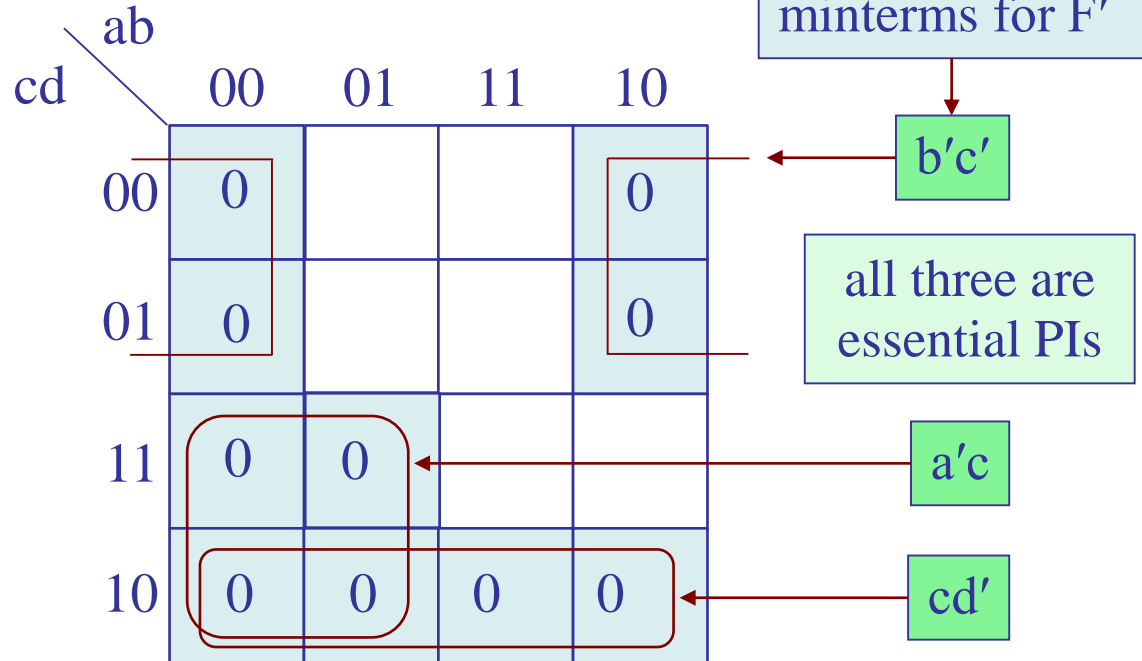

$$F' = a'c + b'c' + cd' = \text{sum-of-products for } F'$$

$$F = (a + c')(b + c)(c' + d) = \text{product-of-sums}$$

De Morgan

simplified POS expansion




## 20. Timing hazards – static hazards

effects of propagation delays

$$F = XZ' + YZ$$


$$X = 1$$
$$Y = 1$$

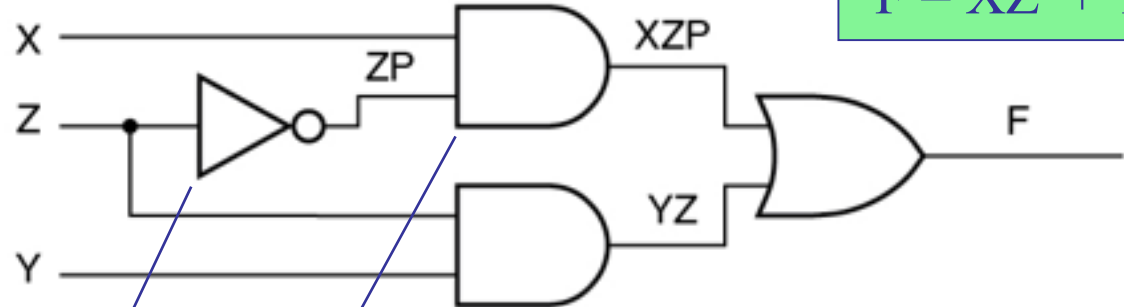

delay through inverter

delays through AND gates

delay through OR gate

 

lab 2 and Wakerly, Fig.3-26

referred to as **static-1** hazard,  
note: the dual of the above circuit  
would exhibit a **static-0** hazard,  
see also Wakerly Fig. 3-27

$$F = XZ' + YZ$$

	XY			
Z	00	01	11	10
0			1	1
1		1	1	

essential PIs

YZ

XZ'

$$F = XZ' + YZ + XY$$

	XY			
Z	00	01	11	10
0			1	1
1		1	1	

consensus term,  
non-essential PI

XY

adjacent pairs of 1's  
must be covered  
by a PI to prevent  
the timing hazard

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1


MATLAB code for generating truth table

```
[X,Y,Z] = a2d(0:7,3); % 3-bit binary pattern
F = (X & ~Z) | (Y & Z);
[X,Y,Z,F]
```


% print truth table

$$X \cdot A + X' \cdot B = X \cdot A + X' \cdot B + A \cdot B \quad (\text{consensus})$$

## 20. Timing hazards – static hazards

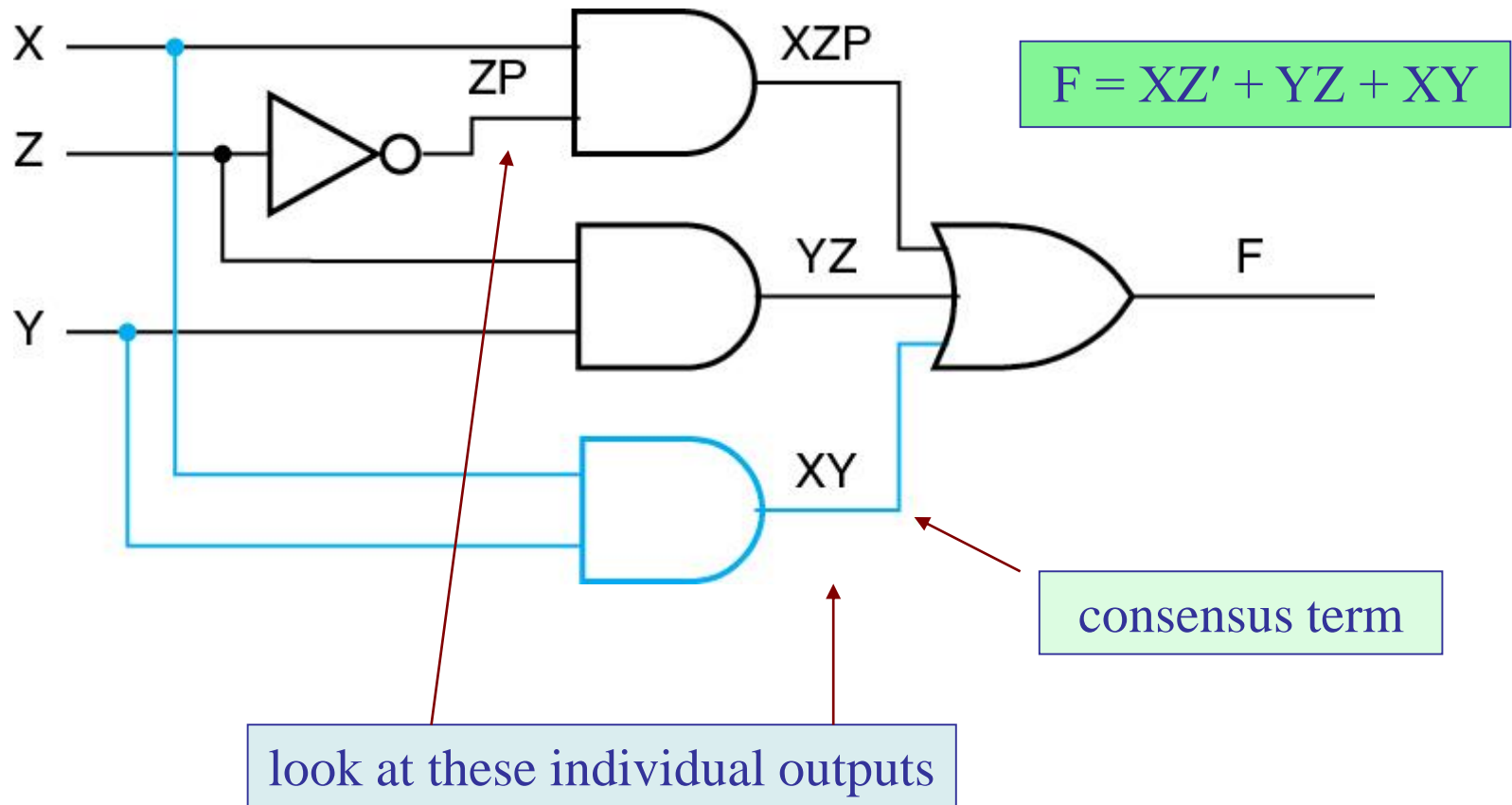

# Simulink Implementation

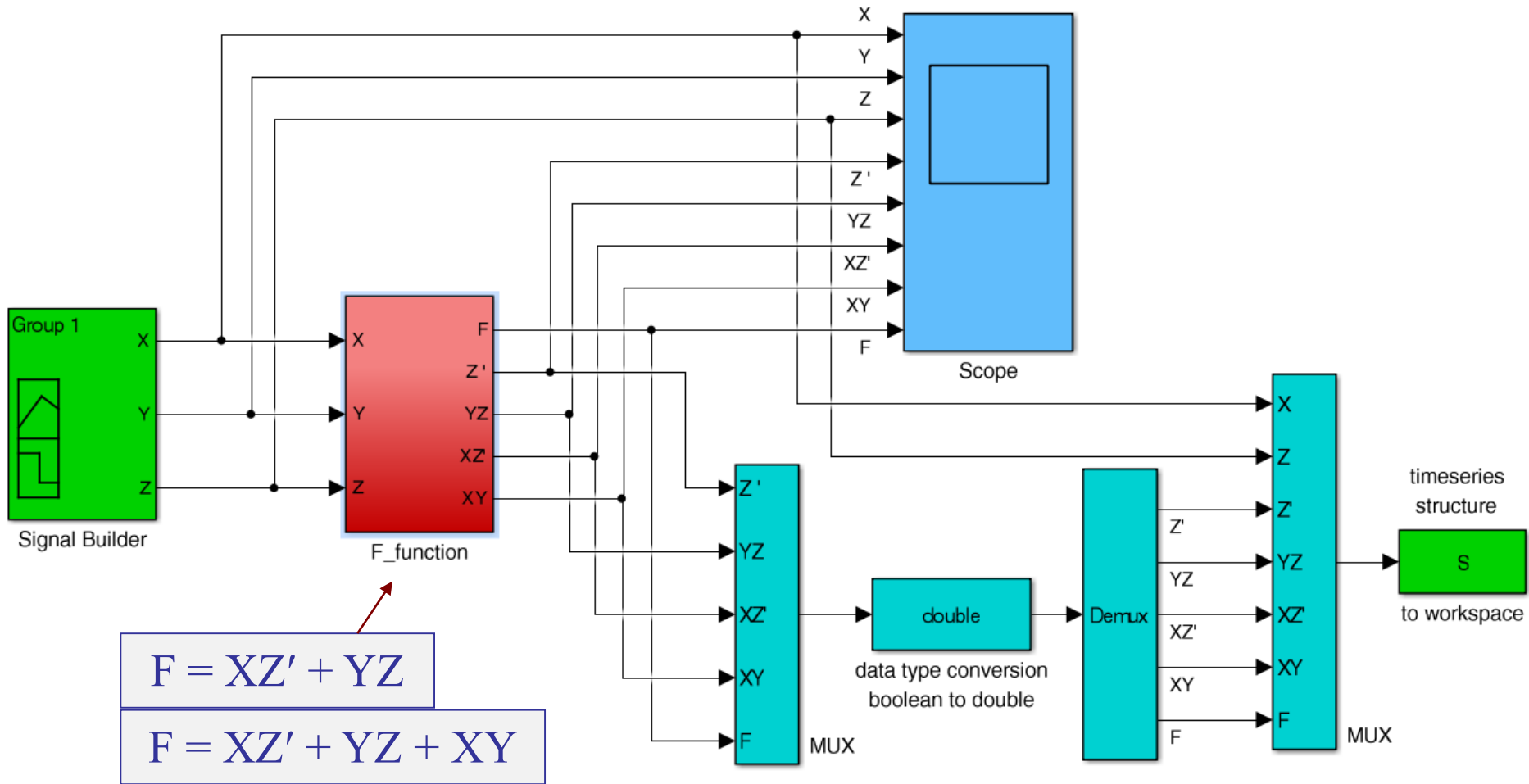


Simulink file: [fig326a.slx](#)

without delays

$$F = XZ' + YZ$$

$$F = XZ' + YZ + XY$$

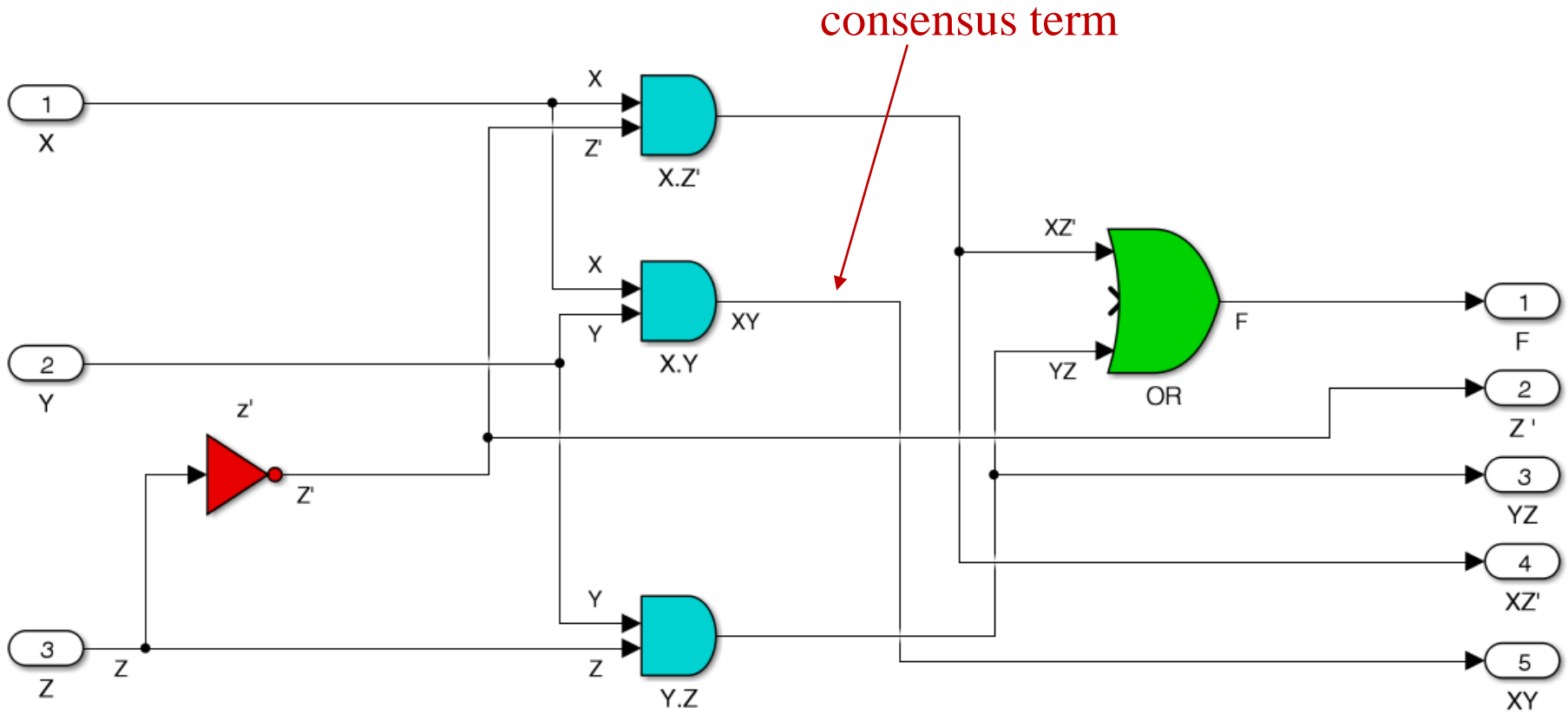

Simulink: subfunction contained in [fig326a.slx](#)

without delays

$$F = XZ' + YZ$$




no glitch

with delays

$$F = XZ' + YZ$$


subfunction contained in [fig326a.slx](#)

with consensus term  $XY$  not connected

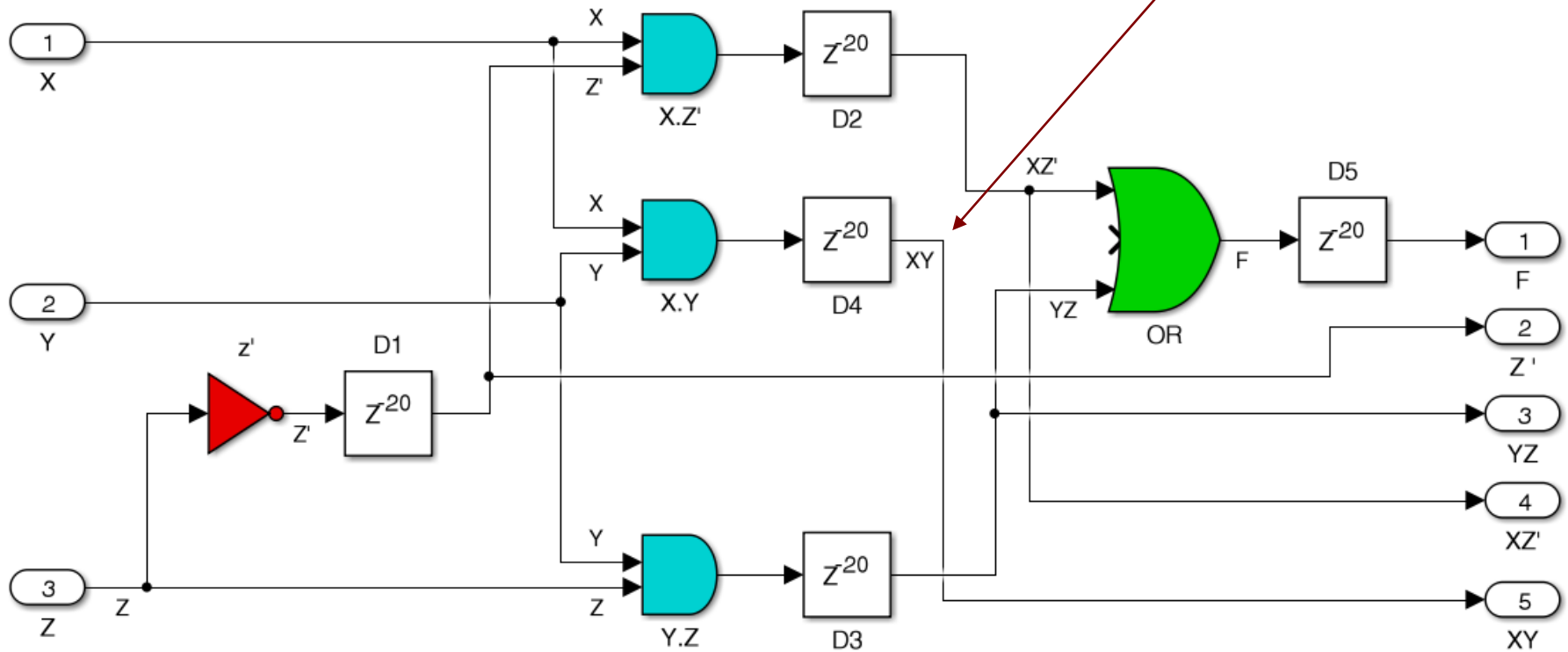

note: here, the simulation time is  $0 < t < 8$  (sec or any other time unit), and the sampling time interval is, by default,  $T_s = 0.01$  time units, so that there are 100 samples per time unit, thus, delay by 20 samples would correspond to  $20/100 = 0.2 = 1/5$  of a time unit.


with delays

 



with delays

$$F = XZ' + YZ$$

 


```
% fig326m.m - found on Canvas
% import data from Simulink into MATLAB for plotting


t    = S.time;           % time range, length 801 by default
X    = S.data(:,1);
Z    = S.data(:,2);
Zp   = S.data(:,3);
YZ   = S.data(:,4);
XZp  = S.data(:,5);
XY   = S.data(:,6);
F    = S.data(:,7);     % extract computed output

figure;
    subplot(7,1,1); stairs(t,X,'b-'); yaxis(0,2,0:2);
    subplot(7,1,2); stairs(t,Z,'b-'); yaxis(0,2,0:2);
    subplot(7,1,3); stairs(t,Zp,'g-'); yaxis(0,2,0:2);
    subplot(7,1,4); stairs(t,YZ,'m-'); yaxis(0,2,0:2);
    subplot(7,1,5); stairs(t,XZp,'m-'); yaxis(0,2,0:2);
    subplot(7,1,6); stairs(t,XY,'m-'); yaxis(0,2,0:2);
    subplot(7,1,7); stairs(t,F,'r-'); yaxis(0,2,0:2);
xlabel('\itt');
```

with consensus term XY connected

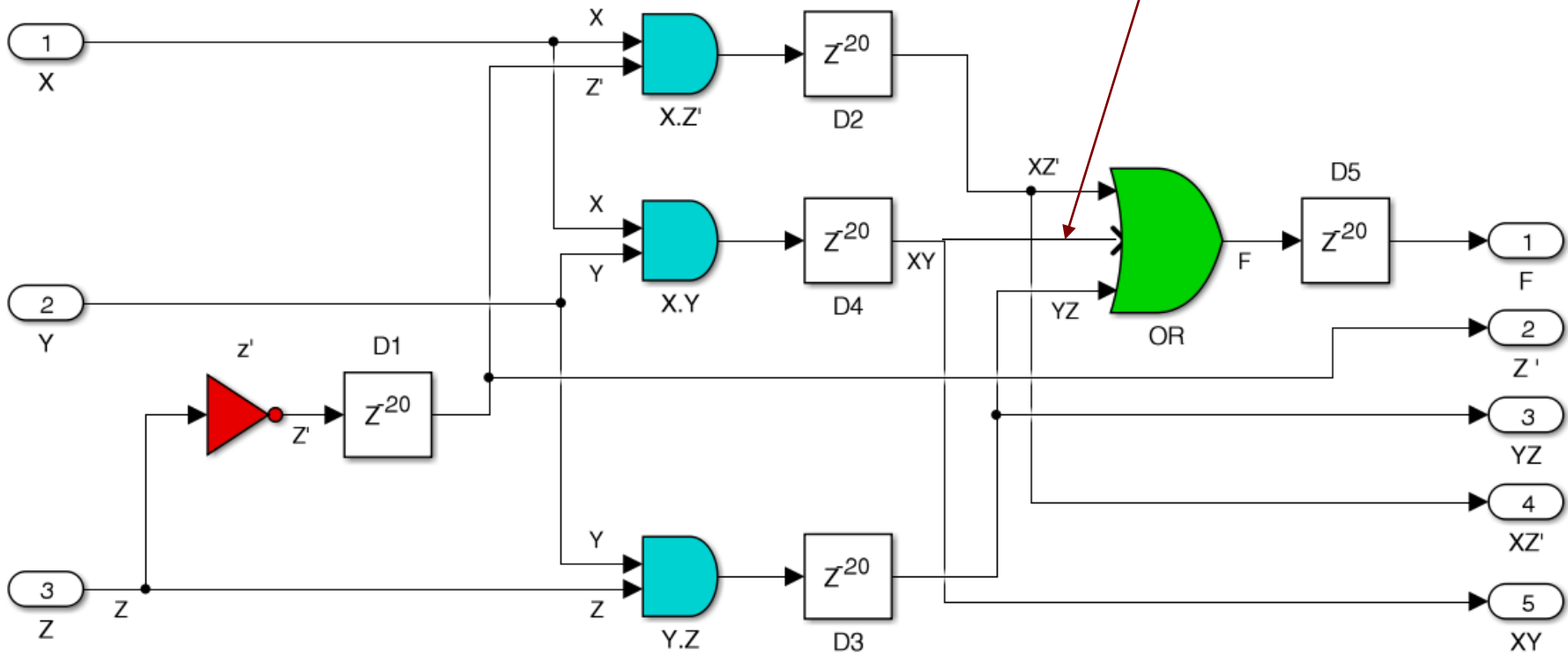


$$F = XZ' + YZ + XY$$

 

with delays and consensus term

$$F = XZ' + YZ + XY$$

 


another example – Wakerly Fig. 3-30


K-map for a sum-of-products circuit

(a) as originally designed

 (b) with extra product terms fo cover static-1 hazards


 
$$F = X \cdot Y' \cdot Z' + W' \cdot Z + W \cdot Y$$




$$F = X \cdot Y' \cdot Z' + W' \cdot Z + W \cdot Y + W' \cdot X \cdot Y' + Y \cdot Z + W \cdot X \cdot Z'$$

adjacent pairs of 1's must be covered by a PI to prevent timing hazards


two more examples [cf. Brown & Vranesic]

 adjacent pairs of 1's must be covered by a PI to prevent timing hazards



$$F = a'c + ab$$
$$= a'c + ab + bc$$


↑  
consensus term

 

$$F = a'c + ad$$
$$= a'c + ad + cd$$


↑  
consensus term

## 20. Timing hazards – dynamic hazards

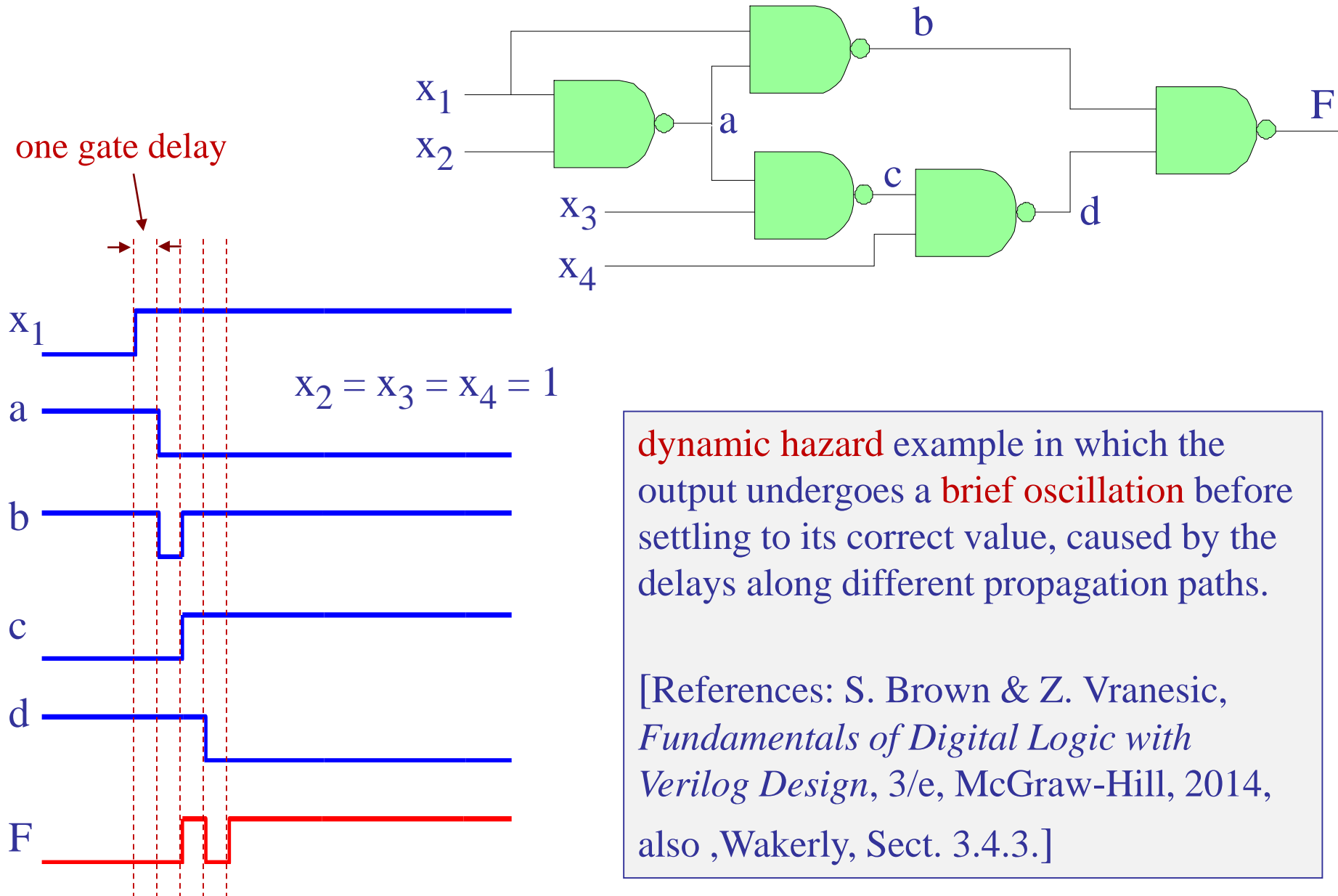




# Simulink Implementation

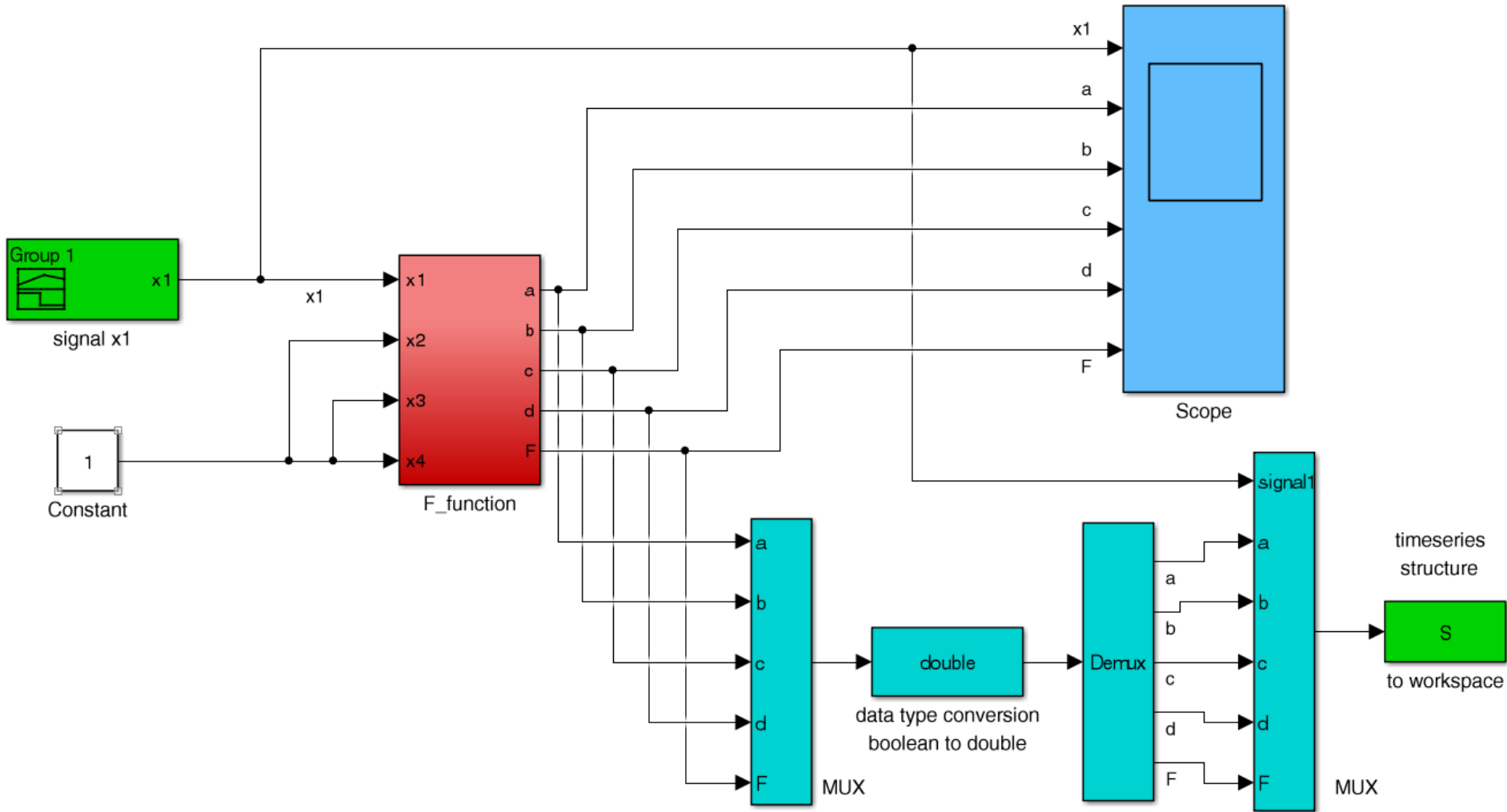

Simulink file: [dhazard1.slx](#), with delays

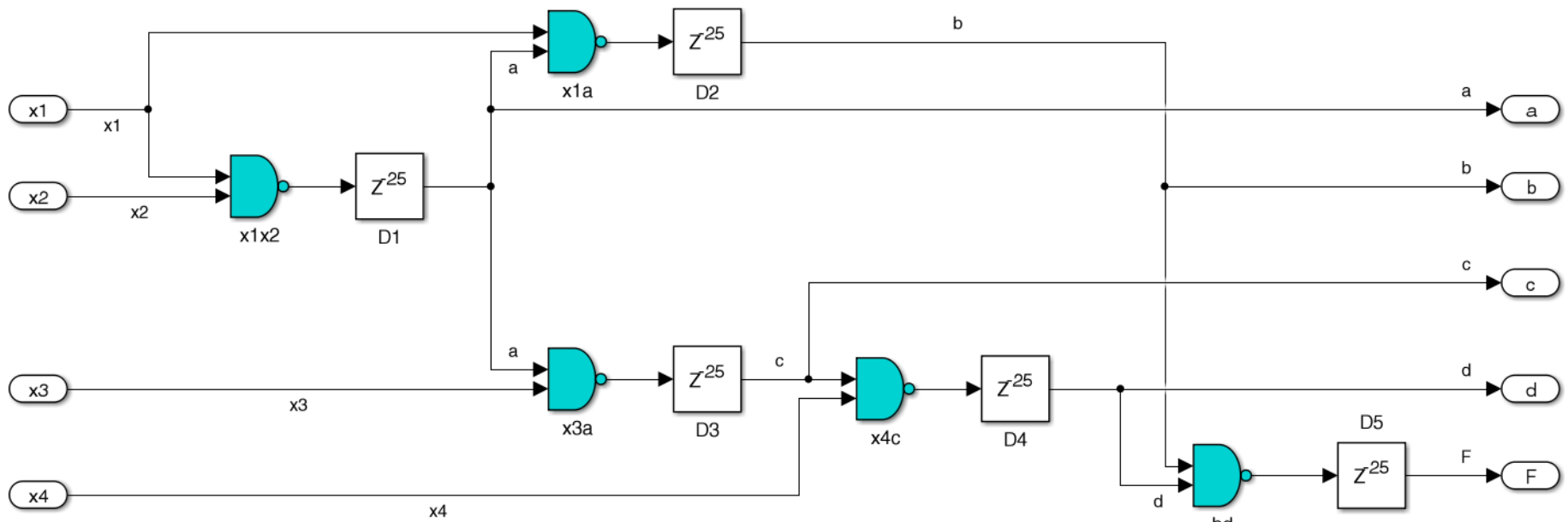Simulink file: [dhazard2.slx](#), without delays



$$x_2 = x_3 = x_4 = 1$$

$$a = (x_1 \cdot x_2)' = x_1'$$

$$b = (x_1 \cdot a)' = (x_1 \cdot a)'$$


$$c = (x_3 \cdot a)' = (1 \cdot a)' = a'$$

$$d = (x_4 \cdot c)' = (1 \cdot c)' = c' = a$$


$$F = (b \cdot d)'$$

(without delays)

with delays

 


without delays

 

```
set(0, 'DefaultAxesFontSize', 8);

t = S.time;                % extract data from timeseries S
x1 = S.data(:,1);
a = S.data(:,2);
b = S.data(:,3);
c = S.data(:,4);
d = S.data(:,5);
F = S.data(:,6);

 figure;
subplot(6,1,1); stairs(t,x1,'b-'); yaxis(0,1.5,0:1);
subplot(6,1,2); stairs(t,a,'m-'); yaxis(0,1.5,0:1);
subplot(6,1,3); stairs(t,b,'g-'); yaxis(0,1.5,0:1);
subplot(6,1,4); stairs(t,c,'b-'); yaxis(0,1.5,0:1);
subplot(6,1,5); stairs(t,d,'m-'); yaxis(0,1.5,0:1);
subplot(6,1,6); stairs(t,F,'r-'); yaxis(0,1.5,0:1);
xlabel('\itt');
```



## ideal timing diagram – truth table

```
% MATLAB code for generating truth table
```

```
[x1,x2,x3,x4] = a2d(0:15,4); % 4-bit binary pattern
```

```
a = ~(x1 & x2);
```

```
b = ~(x1 & a);
```

```
c = ~(x3 & a);
```

```
d = ~(x4 & c);
```

```
F = ~(b & d);
```

```
[x1,x2,x3,x4,a,b,c,d,F]
```

```
% print truth table
```

the operations **&** and **|** are vectorized

without delays:


$$a = (x_1 \cdot x_2)'$$

$$b = (x_1 \cdot a)'$$

$$c = (x_3 \cdot a)'$$

$$d = (x_4 \cdot c)'$$

$$F = (b \cdot d)'$$

 


# ideal timing diagram – truth table

x1	x2	x3	x4	a	b	c	d	F
0	0	0	0	1	1	1	1	0
0	0	0	1	1	1	1	0	1
0	0	1	0	1	1	0	1	0
0	0	1	1	1	1	0	1	0
0	1	0	0	1	1	1	1	0
0	1	0	1	1	1	1	0	1
0	1	1	0	1	1	0	1	0
0	1	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1	1
1	0	0	1	1	0	1	0	1
1	0	1	0	1	0	0	1	1
1	0	1	1	1	0	0	1	1
1	1	0	0	0	1	1	1	0
1	1	0	1	0	1	1	0	1
1	1	1	0	0	1	1	1	0
1	1	1	1	0	1	1	0	1


4-bit binary pattern

# ideal timing diagram – truth table

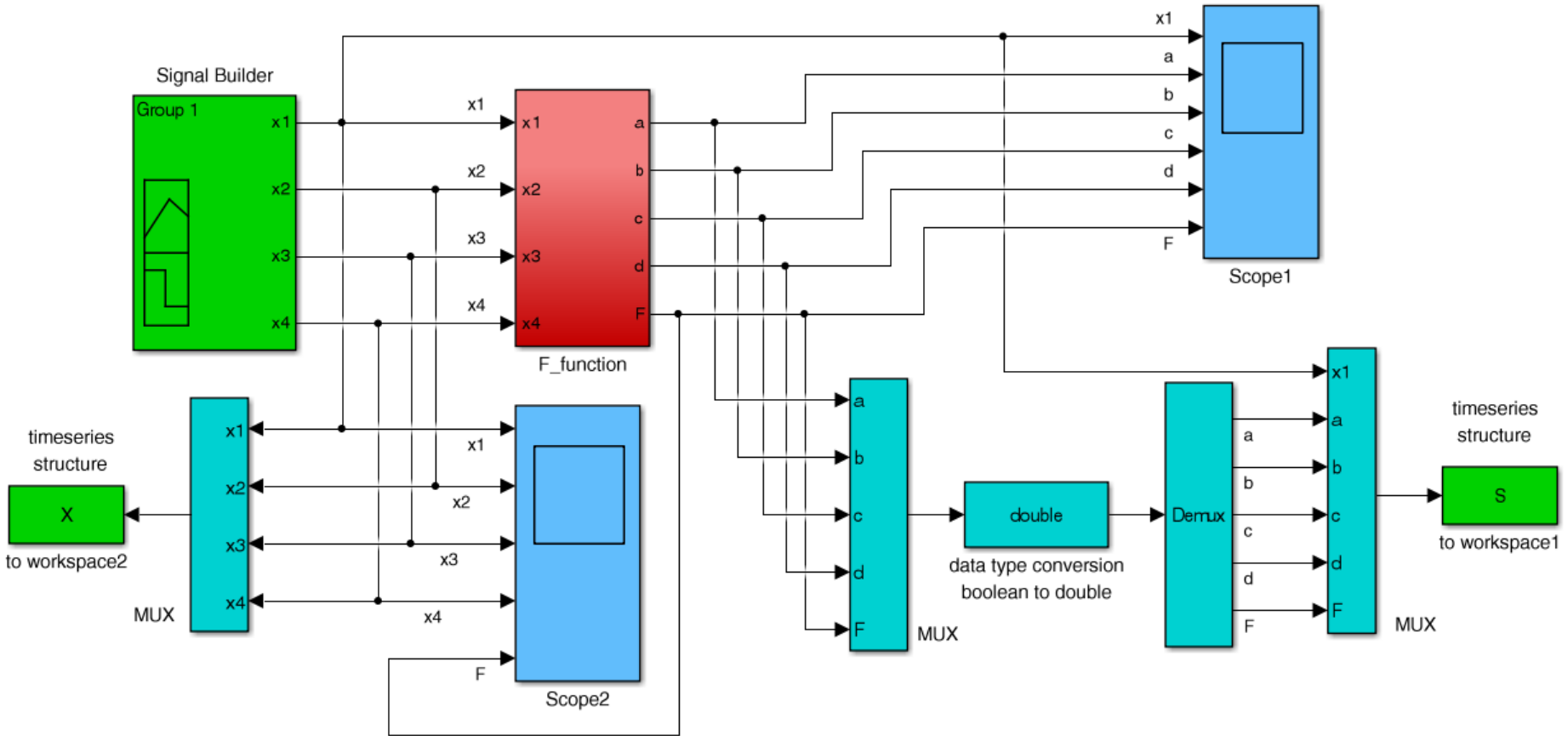


 Simulink file: [dhazard3.slx](#), without delays






$x_1, x_2, x_3, x_4, F$  signals

 


$x_1, a, b, c, d, F$  signals

$x_1, x_2, x_3, x_4, F$  signals

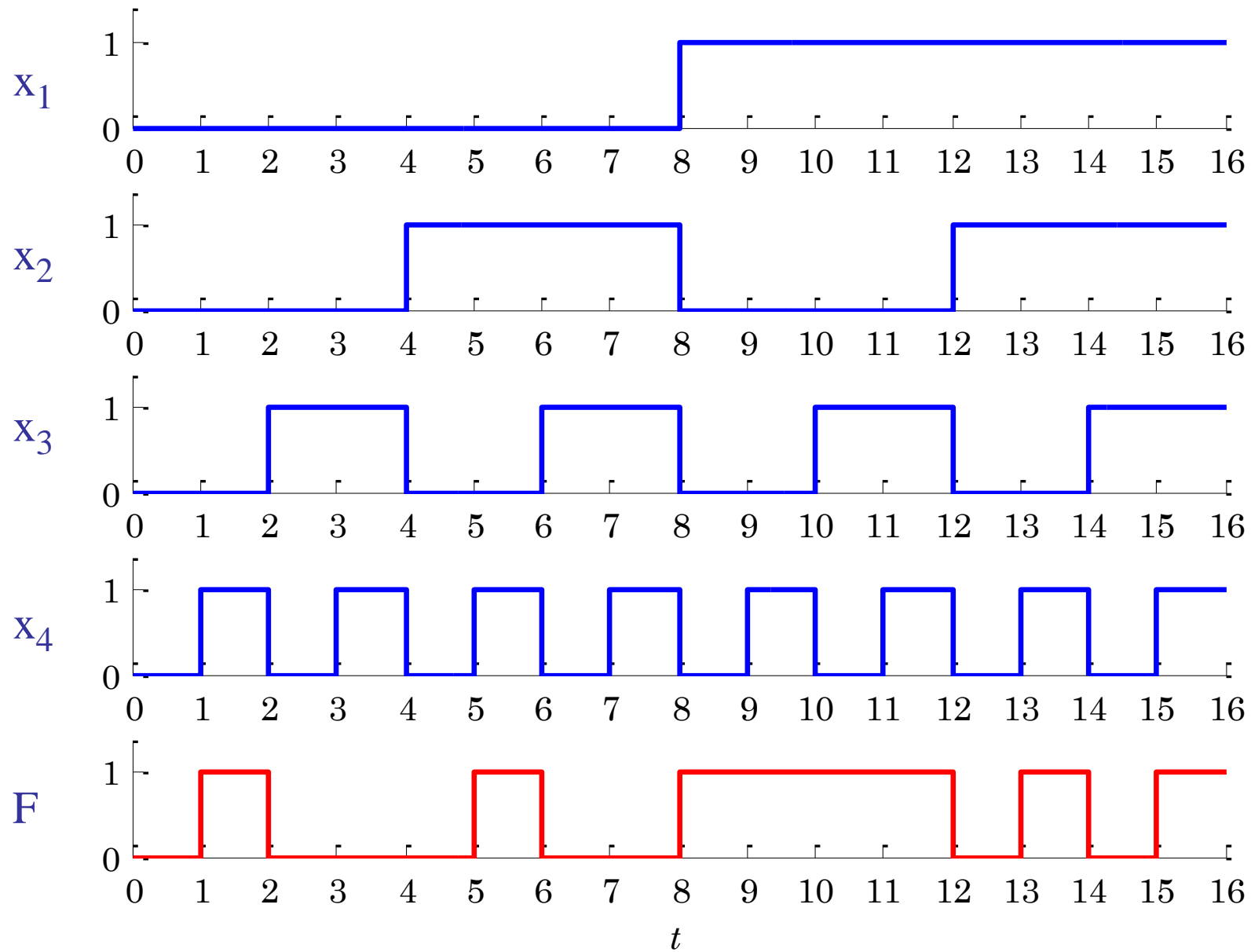

$x_1, a, b, c, d, F$  signals

 

```
t = S.time;           % extract data from structure S
a = S.data(:,2);
b = S.data(:,3);
c = S.data(:,4);
d = S.data(:,5);
F = S.data(:,6);



x1 = X.data(:,1);    % extract data from structure X
x2 = X.data(:,2);
x3 = X.data(:,3);
x4 = X.data(:,4);

figure;
subplot(5,1,1); stairs(t,x1,'b-'); yaxis(0,1.5,0:1)
subplot(5,1,2); stairs(t,x2,'b-'); yaxis(0,1.5,0:1)
subplot(5,1,3); stairs(t,x3,'b-'); yaxis(0,1.5,0:1)
subplot(5,1,4); stairs(t,x4,'b-'); yaxis(0,1.5,0:1)
subplot(5,1,5); stairs(t,F,'r-'); yaxis(0,1.5,0:1)
xlabel('\itt');

figure;
subplot(5,1,1); stairs(t,a,'b-'); yaxis(0,1.5,0:1)
subplot(5,1,2); stairs(t,b,'g-'); yaxis(0,1.5,0:1)
subplot(5,1,3); stairs(t,c,'b-'); yaxis(0,1.5,0:1)
subplot(5,1,4); stairs(t,d,'m-'); yaxis(0,1.5,0:1)
subplot(5,1,5); stairs(t,F,'r-'); yaxis(0,1.5,0:1)
xlabel('\itt');
```


x1	x2	x3	x4	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

4-bit binary pattern

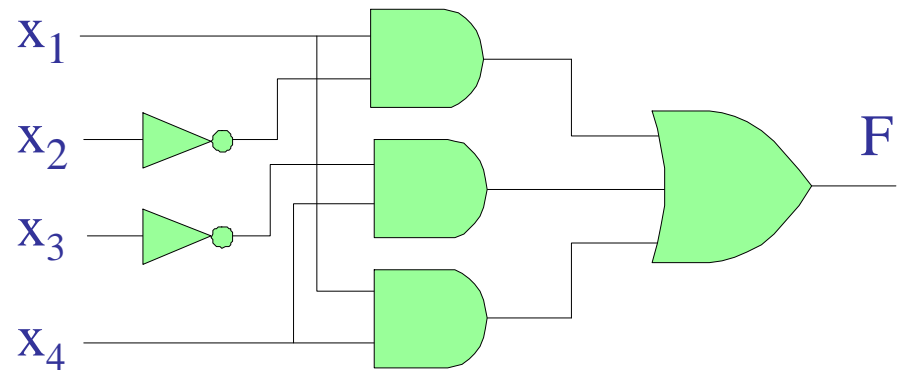 


$$F = x_1x_4 + x_1x_2' + x_3'x_4$$

$$F = x_1x_4 + x_1x_2' + x_3'x_4$$

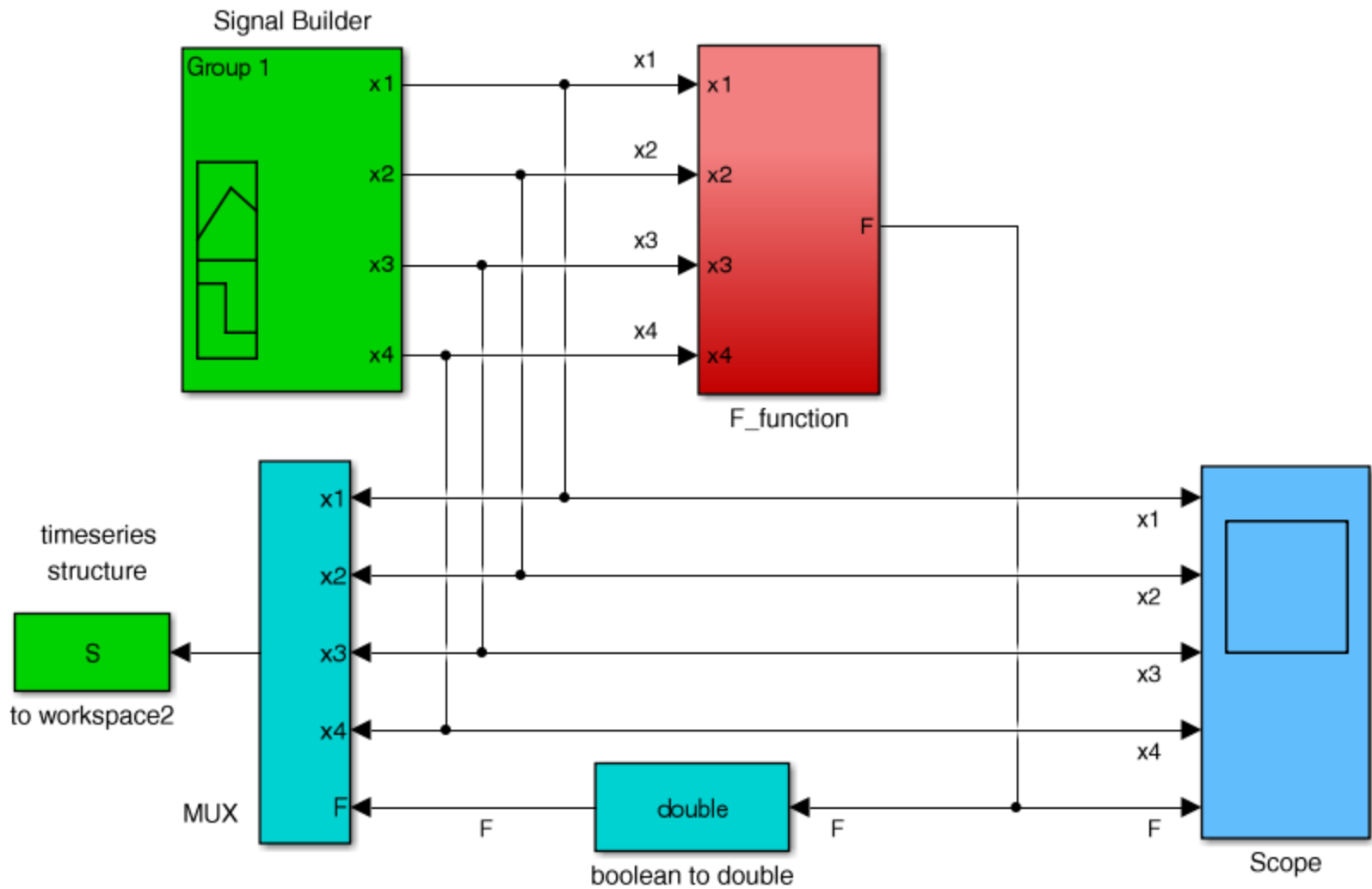



$$F = x_1x_4 + x_1x_2' + x_3'x_4$$

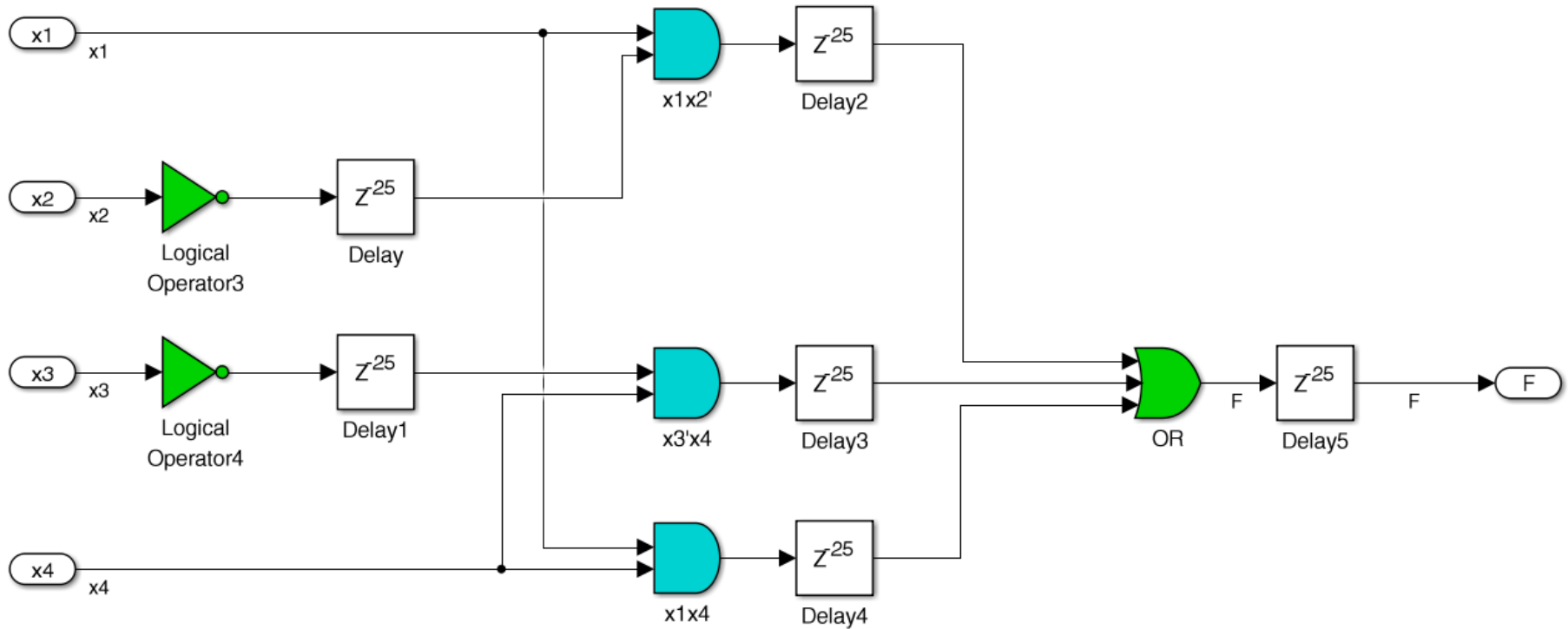

does not exhibit any static or dynamic hazards, apart from an overall delay


$$x_2 = x_3 = x_4 = 1$$

$$F = x_1 x_4 + x_1 x_2' + x_3' x_4$$

  

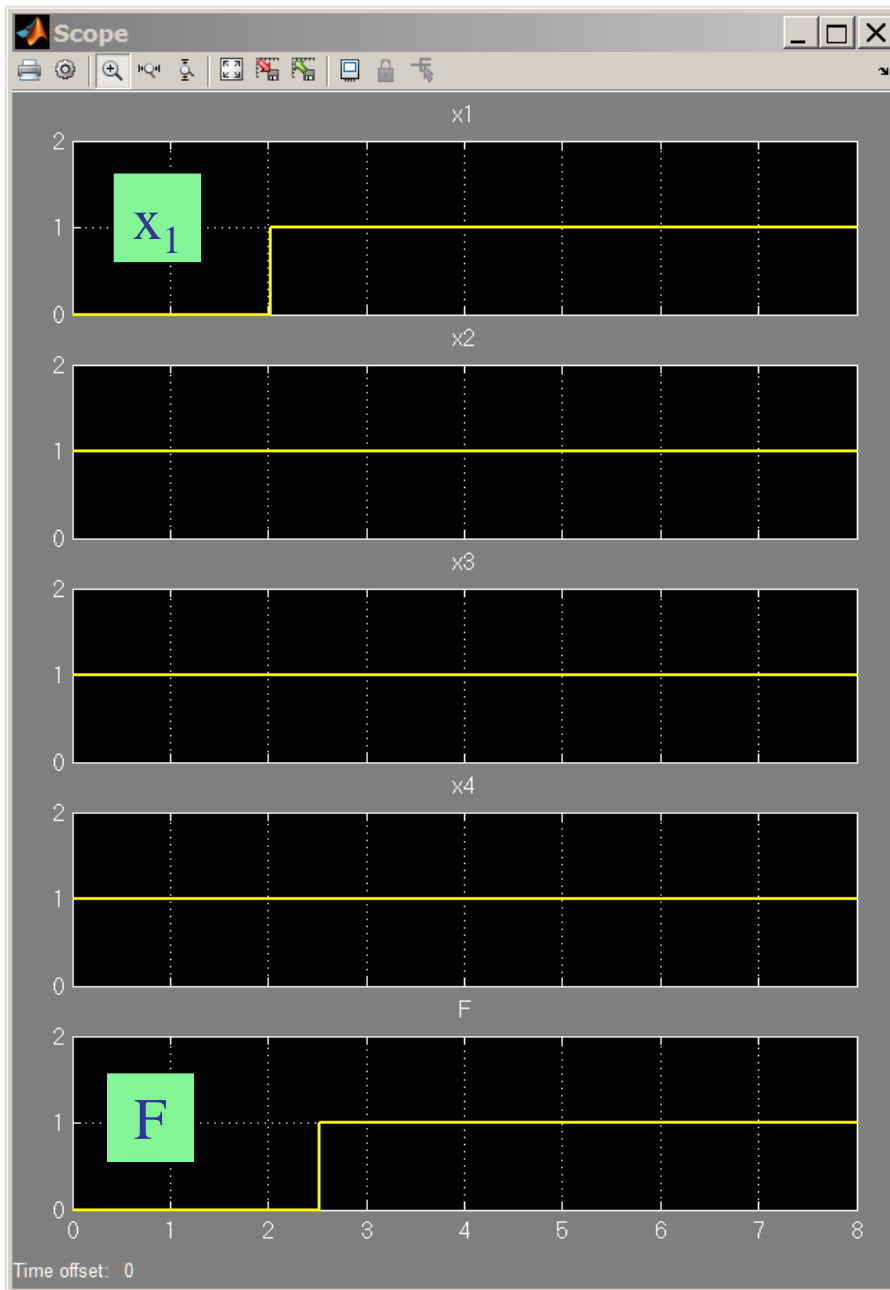overall two-gate delay, relative to  $x_1$





$$x_2 = x_3 = x_4 = 1$$

$$F = x_1 x_4 + x_1 x_2' + x_3' x_4$$