

Rutgers University
School of Engineering

Fall 2022

332:231 – Digital Logic Design

Sophocles J. Orfanidis
ECE Department
orfanidi@rutgers.edu

Unit 8 – Finite State Machines

Course Topics

1. Introduction to DLD, Verilog HDL, MATLAB/Simulink
2. Number systems
3. Analysis and synthesis of combinational circuits
4. Decoders/encoders, multiplexers/demultiplexers
5. Arithmetic systems, comparators, adders, multipliers
6. Sequential circuits, latches, flip-flops
7. Registers, shift registers, counters, LFSRs
8. Finite state machines, analysis and synthesis



Text: J. F. Wakerly, *Digital Design Principles and Practices*, 5/e, Pearson, 2018
additional references on Canvas Resources

Sequential circuits (Wakerly, Chapters 9, 10 ,11)

Topics discussed are:

Finite state machines (FSM)

Mealy vs. Moore FSMs

State diagrams

State tables

State assignment & encoding

Gate-level implementation with D flip-flops

Design Examples

Contents:

1. Finite state machines (FSM)
2. Mealy vs. Moore FSMs, design steps
3. State diagrams
4. State tables, compact and conventional forms
5. State assignment & encoding (plain binary, Gray, one-hot)
6. Gate-level implementation with D flip-flops
7. Examples:
 - design of a car alarm system
 - design of a 2-bit counter with input & output
 - analyzing FSM block diagrams
 - cruise control system, Moore & Mealy versions
 - sequence recognizers
 - state reduction
 - electronic keypad lock
 - vending machine
 - elevator controller

References

J. F. Wakerly, *Digital Design Principles and Practices*, 5/e, Pearson, 2018.

S. Brown and Z. Vranesic, *Fundamentals of Digital Logic with Verilog Design*, 3/e, McGraw-Hill, 2014.

D. M. Harris and S. L. Harris, *Digital Design and Computer Architecture*, 2/e, Elsevier, 2013.


M. Mano, C. R. Kime, and T. Martin, *Logic and Computer Design Fundamentals*, 5/e, Pearson, 2016.

A. F. Kana, *Digital Logic Design*, [on Canvas].

E. O. Hwang, *Digital Logic and Microprocessor Design with Interfacing*, 2/e, Cengage, 2018.

 C. Maxfield, *Bebop to the Boolean Boogie*, 2/e, Newnes, 2009.

sequential circuits and finite state-machines (FSM) are special cases of dynamic systems



In general, a system can be defined by specifying the **I/O computational rule** that determines the output signal $y(t)$ from the input signal $x(t)$.

The time variable t can be continuous or discrete. The system can be linear or non-linear, time-invariant or time-varying, and can be described by differential or difference equations.

State Machines

State-space realizations, also known as state-space models, have a very large number of applications in many diverse fields, such as,

digital logic design

differential equations for physical systems

system theory

electric circuits

linear systems

digital signal processing

control systems

communication systems

predictive analytics

biomedical signal processing

geophysical signal processing

aerospace engineering

military systems

statistics and time series analysis

econometrics and financial engineering

State Machines

State-space realizations are very powerful representations of systems (linear or nonlinear, time-invariant or not).

The system is described by a set of **internal states** at each time instant t , denoted for example by $Q(t)$, and these states are used to compute the current output $y(t)$ in terms of the current input $x(t)$, and then update the states to their next values, $Q(t+1)$, so that they can be used at time $t+1$ (or, more generally at, $t+\Delta t$).

In other words, the system's **time evolution** is described **iteratively** by a computational algorithm of the form,

for each time instant t , do:

$$y(t) = G(x(t), Q(t)) \quad (\text{compute output})$$

$$Q(t+1) = F(x(t), Q(t)) \quad (\text{update state})$$

[to get started, one needs to know the initial state, $Q(0)$]

State Machines

For example, in going from time t to time $t+2$, one carries out the steps:

at time t ,

$$y(t) = G(x(t), Q(t))$$

$$Q(t+1) = F(x(t), Q(t))$$

at time $t+1$,

$$y(t+1) = G(x(t+1), Q(t+1))$$

$$Q(t+2) = F(x(t+1), Q(t+1))$$

at time $t+2$,

$$y(t+2) = G(x(t+2), Q(t+2))$$

$$Q(t+3) = F(x(t+2), Q(t+2))$$

etc.

$F()$ and $G()$ depend on application
in DLD, F is referred to as
next-state logic, or **excitation logic**
and, G is referred to as **output logic**

from here on, we'll use the
simplified notation,
 x_t, y_t, Q_t
for
 $x(t), y(t), Q(t)$

State Machines

It should be emphasized that the updated state Q_{t+1} is being computed at time t , and becomes available at time t , replacing Q_t , but it is saved until it is used later at time $t+1$.

The computations can be cast as a repetitive algorithm, in which the present state is overwritten by the next state.

initialize state Q (typically at $t=0$), then,

at each time t , do,

$$y_t = G(x_t, Q)$$

$$Q = F(x_t, Q)$$

or,

at each time t , do,

$$y_t = G(x_t, Q)$$

$$Q_{\text{next}} = F(x_t, Q)$$


$$Q = Q_{\text{next}}$$

State Machines

We are assuming that time is discretized in units of 1, which means one clock period, so that $t+1$ means one clock period ahead of t .


In DLD (essentially all) sequential circuits are synchronously driven by a clock, and the state changes occur during the rising edge of the clock period (or, alternatively - but less commonly - during the falling edge.)

rising edge

 

clock period depends on application,
e.g., Emona board has 10 μ sec period

falling edge

 

clock duty cycles
are usually, 50%

State Machines

State machines in DLD fall into two general families:

Moore type:

output equation depends **only** on Q , i.e., $y = G(Q)$

Mealy type:

output equation depends on **both** x and Q , i.e., $y = G(x, Q)$

for each time instant t , do:

$$y_t = G(x_t, Q_t)$$

$$Q_{t+1} = F(x_t, Q_t)$$

simplified notation



$$y = G(x, Q)$$


$$Q_{\text{next}} = F(x, Q)$$

in general, one can have multiple inputs, multiple outputs (MIMO systems), and multiple states.


↑
changes occur at
clock rising edges

State Machines – Moore

e.g., edge-triggered D-flip-flops

 

 
$$y_t = G(Q_t) \text{ Moore}$$
$$Q_{t+1} = F(x_t, Q_t)$$




State Machines – Mealy


e.g., edge-triggered D-flip-flops

 
 
$$y_t = G(x_t, Q_t) \text{ Mealy}$$
$$Q_{t+1} = F(x_t, Q_t)$$




 A more compact way of drawing an FSM is depicted below, assuming that **D flip-flops** are used for the memory/state-holding elements. The advantage is that the next states, Q^{next} , are the excitation inputs to the flip-flops, i.e., $D = Q^{\text{next}}$. See next page for an alternative drawing.




Alternative drawing

 The next states, Q^{next} , are the excitation inputs to the flip-flops, i.e., $D = Q^{\text{next}}$. See next page on how to use other types of flip-flops.




 Using T or JK flip-flops instead of D flip-flops: (a) carry out the design using D flip-flops, and, (b) replace each D flip-flop by a T or a JK flip-flop as shown below (effectively converting them to D flip-flops).



$$T = D \oplus Q$$

$$Q_{\text{next}} = T \oplus Q = D$$

 

$$J = D$$

$$K = D'$$

$$Q_{\text{next}} = J Q' + K' Q = D$$

FSM design steps with D-flip-flops:

1. Start with **verbal description** of the system, specifying its inputs, outputs, and the number of required states, including how the states **transition** from one to another during each clock edge time instant. You may choose one of the states as the starting or **reset state**.
2. Convert the verbal description into a **state diagram**.
3. Convert the state diagram into a **state table**, that is, a truth table that includes the inputs, the present states, the next states, and the outputs.
4. Encode the symbolic states in terms of **state variables**, by making a particular **state-assignment** or **state-encoding** choice (i.e., binary or Gray coding) and re-write the state table in terms of the encoded state variables.
5. Based on the state table, develop expressions for the **next-state equations**, $Q^{\text{next}} = F(X, Q)$, in terms of the present states Q and the inputs X , and also for **output equations**, $Y = G(X, Q)$.
6. Implement step-5 as a combinational circuit with logic gates.
7. Feed back the next states Q^{next} to the D inputs of the D-flip-flops.
8. Connect a common clock signal to all the flip-flops, and also set the flip-flop “clear” inputs so that the system starts from the reset state.

analysis



synthesis



Conversely, the **FSM analysis problem** starts with a given block-diagram realization for the FSM, and proceeds backwards through the above steps, deriving the state table, and clarifying the operation of the FSM.

FSM synthesis/design steps – Summary

1. Start with verbal description and choose states and the reset state.
2. Convert the verbal description into a state diagram.
3. Convert the state diagram into a state table.
4. Encode the symbolic states with D-flip-flop state variables.
5. Derive the next-state and output equations in terms of state variables.
6. Implement the design using D-flip-flops and logic gates.
7. Simulate it with MATLAB/Simulink to verify proper operation.

analysis



synthesis




state diagrams are directed graphs that convey the same information as state tables, but in a graphical form, where the states are listed inside the circles and the arrows indicate the state transitions taking place at successive **clock-edge** time instants.

Conventions for drawing state diagrams:

Along each arrow connecting two successive states S and S^{next} , indicate the values of the inputs X that caused this transition from the current state S .

 Moreover, for **Mealy machines**, indicate along the same arrow the values of the outputs Y that resulted from the values of X and the current state S . But, for **Moore machines**, because the outputs Y depend only on the current state Q , indicate the values of Y inside the circle for the current state S .



Example 1 – To clarify the above steps, we discuss the design of a Moore FSM for a car alarm system [cf. Hwang]. The alarm has an arming signal A, and it monitors several trigger inputs T, such as opening a door, breaking a glass, car vibration, opening the trunk, and so on. If the alarm is armed (A=1), then, if one or more of the trigger inputs is set, the alarm siren will go on.


From this description we find that the siren signal will be,

$$\text{siren} = A \cdot T$$


where the overall trigger signal T is obtained from the OR-ing,

$$T = \text{door} + \text{glass} + \text{vibration} + \text{trunk} + \dots$$

 A realization is shown below. However, simple as this is, it has a major limitation: if the siren is on (A=1 and T=1), then it will go off as soon as T=0 even though A=1 (e.g., someone may break into the car and close the door and the siren will stop). This can be fixed by introducing memory into the system.



 state diagram with state assignments $Q = 0, 1$



characteristic table



A	T	Q	Q^{next}	AT
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	0	0
1	0	0	0	0
1	0	1	1	0
1	1	0	1	1
1	1	1	1	1

Q	AT	00	01	11	10
0				1	
1				1	1


next-state equation

$$Q^{\text{next}} = AQ + AT$$


realization using D flip-flops →

  


original realization
with no memory

 


fsm0s.slx on Canvas

 


input signal generator

 


 



next-state network

 


Example 1

 

scope & data export
subfunction

  


Example 1

 

scope
output

timing diagram

 

MATLAB
code

siren output
with memory

siren output
without memory

```

% fsm0m.m on Canvas - MATLAB code for generating timing diagram
% data imported from Simulink structure S from file fsm0s.slx

t = S.time; % time
CLK = S.data(:,1); % clock pulses
A = S.data(:,2); % arming signal
T = S.data(:,3); % trigger signal
Q = S.data(:,4); % siren signal with memory
AT = A & T; % siren signal without memory

figure;
subplot(5,1,1); stairs(t,CLK, 'g-', 'linewidth',2);
    xaxis(0,8,0:8); yaxis(0,1.5,0:1); ylabel('clock');
subplot(5,1,2); stairs(t,A, 'b-', 'linewidth',2);
    xaxis(0,8,0:8); yaxis(0,1.5,0:1); ylabel('A');
subplot(5,1,3); stairs(t,T, 'm-', 'linewidth',2);
    xaxis(0,8,0:8); yaxis(0,1.5,0:1); ylabel('T');
subplot(5,1,4); stairs(t,Q, 'r-', 'linewidth',2);
    xaxis(0,8,0:8); yaxis(0,1.5,0:1); ylabel('siren');
subplot(5,1,5); stairs(t,AT, 'k-', 'linewidth',2);
    xaxis(0,8,0:8); yaxis(0,1.5,0:1); ylabel('AT');
xlabel('{\itt}, clock periods')

```

Example 2 – To clarify the above steps, we discuss the design of an FSM for a **2-bit binary counter** that has an enable input, and an output.

This differs from a plain counter that we considered in unit-7 in that it is a sequential circuit with an additional input and an output.

This is the same example as that of Fig. 9-8 in Wakerly, but instead of starting with the block diagram, we will start with the verbal description and work our way through the design steps, eventually ending up with a block-diagram realization.

Step 1: Verbal description. Design a counter that counts through the sequence, 0, 1, 2, 3, of decimal numbers. The counter must have an enable input E, such that when E=1, the counting proceeds normally and repeating mod-4, but, it stops when E=0. Moreover, there should be an output Y that indicates the completion of the counting sequence every four counts, that is, Y=1, when the count reaches 3, and Y=0, otherwise. We may think of the successive numbers, 0,1,2,3, as the states of the counter, and we will denote them in the abstract as, S_0, S_1, S_2, S_3 .


The reset state will be count = 0, or, state, S_0 .

state diagrams are directed graphs that convey the same information as state tables, but in a graphical form, where the states are listed inside the circles and the arrows indicate the state transitions taking place at successive **clock-edge** time instants.


Conventions for drawing state diagrams:

Along each arrow connecting two successive states S and S^{next} , indicate the values of the inputs X that caused this transition from the current state S .

 
Moreover, for **Mealy machines**, indicate along the same arrow the values of the outputs Y that resulted from the values of X and the current state S . But, for **Moore machines**, because the outputs Y depend only on the current state Q , indicate the values of Y inside the circle for the current state S .



 Step 2: State diagram. This is a Mealy FSM because Y depends on the input E, e.g., $Y=0$ when $E=0$, but $Y=1$ when $E=1$ at state S_3



 Step 2: State diagram. Yet, another convention is to indicate the values of the input and output in the format **X / Y**, with the input written first and the output, second, along the transition arrows.



this means **X=1** and **Y=0**

Example 2

Step 3: State table. List all possible values of the input E and output Y, and all the required state transitions from present states to next states.

standard form

input E	present state	next state	output Y
0	S ₀	S ₀	0
0	S ₁	S ₁	0
0	S ₂	S ₂	0
0	S ₃	S ₃	0
1	S ₀	S ₁	0
1	S ₁	S ₂	0
1	S ₂	S ₃	0
1	S ₃	S ₀	1

compact form

present state	next state		output Y	
	E=0	E=1	E=0	E=1
S ₀	S ₀	S ₁	0	0
S ₁	S ₁	S ₂	0	0
S ₂	S ₂	S ₃	0	0
S ₃	S ₃	S ₀	0	1

← count completed
then, repeat

Step 4: State assignment. In general, for an FSM with N states, one needs

$$n = \text{ceiling}(\log_2 N)$$

state variables, each to be stored in a separate flip-flop. Thus, here, we need, $n = \log_2(4) = 2$, state variables and two flip-flops, and we may choose the state variables to be binary bits denoted by Q_1, Q_0 . The state table is now re-written in terms of the state variables.


input E	present state		next state		output Y
	Q_1	Q_0	Q_1	Q_0	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	1	0	0
0	1	1	1	1	0
1	0	0	0	1	0
1	0	1	1	0	0
1	1	0	1	1	0
1	1	1	0	0	1

state encoding	
Q_1	Q_0
$S_0 \equiv 0$	0
$S_1 \equiv 0$	1
$S_2 \equiv 1$	0
$S_3 \equiv 1$	1

← count complete / repeat


Step 5: Next-state and output equations. Use K-maps.

input E	present $Q_1\ Q_0$	next $Q_1\ Q_0$	output Y
0	0 0	0 0	0
0	0 1	0 1	0
0	1 0	1 0	0
0	1 1	1 1	0
1	0 0	0 1	0
1	0 1	1 0	0
1	1 0	1 1	0
1	1 1	0 0	1

 


$$Q_0^{\text{next}} = E' Q_0 + E Q_0' = E \oplus Q_0$$
 
$$\begin{aligned}
 Q_1^{\text{next}} &= Q_1 E' + Q_1 Q_0' + Q_1' Q_0 E \\
 &= Q_1 (E' + Q_0') + Q_1' Q_0 E \\
 &= Q_1 (E Q_0)' + Q_1' (Q_0 E) \\
 &= Q_1 \oplus (EQ_0)
 \end{aligned}$$



Step 5: Next-state and output equations. Use K-maps.

input E	present Q ₁ Q ₀		next Q ₁ Q ₀		output Y
	Q ₁	Q ₀	Q ₁	Q ₀	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	1	0	0
0	1	1	1	1	0
1	0	0	0	1	0
1	0	1	1	0	0
1	1	0	1	1	0
1	1	1	0	0	1

 

$Y = E Q_1 Q_0$

summary

equivalent form

$$Q_0^{\text{next}} = E \oplus Q_0$$

$$Q_1^{\text{next}} = Q_1 \oplus (EQ_0) = Q_1 E' + (Q_1 \oplus Q_0) E$$

Mealy FSM →

$Y = E Q_1 Q_0$

equivalent form




$$Q_1^{\text{next}} = Q_1 \oplus (EQ_0) = Q_1 E' + (Q_1 \oplus Q_0) E$$


proof:

$$\begin{aligned} Q_1^{\text{next}} &= Q_1 \oplus (EQ_0) = Q_1 (E Q_0)' + Q_1' (Q_0 E) \\ &= Q_1 (E' + Q_0') + Q_1' Q_0 E \\ &= Q_1 E' + Q_1 Q_0' + Q_1' Q_0 E \\ &= Q_1 E' + Q_1 Q_0' (E + E') + Q_1' Q_0 E \\ &= (Q_1 + Q_1 Q_0') E' + (Q_1 Q_0' + Q_1' Q_0) E \\ &= Q_1 (1 + Q_0') E' + (Q_1 \oplus Q_0) E \\ &= Q_1 E' + (Q_1 \oplus Q_0) E \end{aligned}$$

 Steps 6-8: FSM block diagram. Use two flip flops for the state variables Q_1, Q_0



 Equivalent realization from Wakerly, Fig. 9-8.




$$D_0 = E \oplus Q_0$$

$$D_1 = Q_1 E' + (Q_1 \oplus Q_0) E$$

$$Y = E Q_1 Q_0$$

 Another equivalent realization from Wakerly, Fig. 9-11.




using also the Q' outputs of the flip-flops

$$D_0 = E \oplus Q_0 = E' Q_0 + E Q_0'$$

$$D_1 = Q_1 E' + (Q_1 \oplus Q_0) E = Q_1 E' + (Q_1 Q_0' + Q_1' Q_0) E$$


$$Y = E Q_1 Q_0$$

 Example 2 - Moore FSM version of the 2-bit counter. Define an output, Z, that is independent of the input E and depends only on the current states.



Next-state and output equations for Moore version

input E	present Q ₁ Q ₀	next Q ₁ Q ₀	output Z
0	0 0	0 0	0
0	0 1	0 1	0
0	1 0	1 0	0
0	1 1	1 1	1
1	0 0	0 1	0
1	0 1	1 0	0
1	1 0	1 1	0
1	1 1	0 0	1

 

$$Z = Q_1 Q_0$$

Z is independent of E

summary


equivalent form

$$Q_0^{\text{next}} = E \oplus Q_0$$

$$Q_1^{\text{next}} = Q_1 \oplus (EQ_0) = Q_1 E' + (Q_1 \oplus Q_0) E$$


Moore FSM → Z = Q₁ Q₀ (Moore output)

 State diagram. This is a Moore FSM because Z depends only on the current states, Z is indicated inside each state circle, arrows are still labeled by the value of the input causing the transition.



FSM block diagrams – Mealy and Moore versions

$$\begin{aligned}
 Q_0^{\text{next}} &= E \oplus Q_0 \\
 Q_1^{\text{next}} &= Q_1 \oplus (EQ_0) \\
 Y &= E \ Q_1 \ Q_0 \quad (\text{Mealy output}) \\
 Z &= Q_1 \ Q_0 \quad (\text{Moore output})
 \end{aligned}$$

 

Example 2

timing diagram


$$Q_0^{\text{next}} = E \oplus Q_0$$

$$Q_1^{\text{next}} = Q_1 \oplus (EQ_0)$$


$Y = E Q_1 Q_0$ (Mealy output)

$Z = Q_1 Q_0$ (Moore output)

Wakerly – Fig. 9-12

 

 
Simulink implementation and timing diagram.



from Simulink file
fsm1eob.slx

 
Example 2

Simulink implementation and timing diagram.



next-state sub-function


output sub-function

 


Example 2

Simulink implementation and timing diagram.

signal builder – input E

 


Simulink implementation and timing diagram.

 


Example 2

scope
output


← states

 

Example 2

 


Mealy
state diagram

 

Moore
state diagram

timing diagram

 


Example 3 – Another FSM analysis example from Wakerly, Fig. 9-13.

There are two inputs, X, Y, three flip-flops (states), Q_2 , Q_1 , Q_0 , and two outputs Z_1 , Z_2 . There are 8 states corresponding to the 8 triplets, $Q_2 Q_1 Q_0$, and these will be denoted symbolically by the letters, A, B, C, D, E, F, G, H.

Analysis Procedure:

 1. The output equations for Z_1 , Z_2 , and the flip-flop excitation equations for the flip-flop inputs, D_2 , D_1 , D_0 , are read off from the logic diagram.
2. These become the transition equations for the next states, $Q_2^{\text{next}}, Q_1^{\text{next}}, Q_0^{\text{next}}$, denoted in Wakerly with the notation, Q_2^* , Q_1^* , Q_0^* .
3. The state-table can be evaluated for all possible valuations of the inputs and the states, and then, converted into a more readable version using the symbolic state letter-names.
4. Finally, a state diagram is drawn, using a slightly different and more efficient drawing convention in this example.

Wakerly, Fig. 9-13. A State Machine with Three Flip-Flops and Eight States



$$D_0 = Q_1' X + Q_0 X' + Q_2$$

$$D_1 = Q_2' Q_0 X + Q_1 X' + Q_2 Q_1$$

$$D_2 = Q_2 Q_0' + Q_0' X' Y$$

flip-flop excitation equations



$$Q_0^{\text{next}} = Q_1' X + Q_0 X' + Q_2$$

$$Q_1^{\text{next}} = Q_2' Q_0 X + Q_1 X' + Q_2 Q_1$$

$$Q_2^{\text{next}} = Q_2 Q_0' + Q_0' X' Y$$

next-state transition equations

$$Z_1 = Q_2 + Q_1' + Q_0'$$

$$Z_2 = Q_2 Q_1 + Q_2 Q_0'$$

output equations – Moore type

state table

				XY				
<i>Q2</i>	<i>Q1</i>	<i>Q0</i>		<i>00</i>	<i>01</i>	<i>10</i>	<i>11</i>	<i>Z1Z2</i>
000	000	100	001	001	10			
001	001	001	011	011	10			
010	010	110	000	000	10			
011	011	011	010	010	00			
100	101	101	101	101	11			
101	001	001	001	001	10			
110	111	111	111	111	11			
111	011	011	011	011	11			


Q2* Q1* Q0*

symbolic state table

				XY	
<i>S</i>	<i>00</i>	<i>01</i>	<i>10</i>	<i>11</i>	<i>Z1Z2</i>
A	A	E	B	B	10
B	B	B	D	D	10
C	C	G	A	A	10
D	D	D	C	C	00
E	F	F	F	F	11
F	B	B	B	B	10
G	H	H	H	H	11
H	D	D	D	D	11

S*

 next states
for all valuations
of input pairs XY



new drawing convention:

use **input expressions** to
label the transitions


transition	inputs	new label
$A \rightarrow A$	$XY = 00$	$X' Y'$
$A \rightarrow E$	$XY = 01$	$X' Y$
$A \rightarrow B$	$XY = 10, 11$	$X Y' + XY = X$

FSM – analysis / synthesis / design steps – Summary

1. Start with verbal description and choose states and the reset state.
2. Convert the verbal description into a state diagram.
3. Convert the state diagram into a state table.
4. Encode the symbolic states with D-flip-flop state variables.
5. Derive the next-state and output equations in terms of state variables.
6. Implement the design using D-flip-flops and logic gates.
7. Simulate it with Simulink or HDL to verify proper operation.

analysis

synthesis

 

Example 4 – Sequence recognizer – Moore version. It is desired to design an FSM to detect the particular sequence of three or more consecutive ones, 111, in an incoming input stream X of 0s and 1s, measured at the positive edges of the clock signal. At each time instant, upon detecting three ones in the three immediately preceding time instants, the FSM should produce an output, $Y = 1$, otherwise, it should output, $Y = 0$. All changes should occur at the positive edges of the clock signal.

To put this in some context, one can think of a car **cruise control system** in which the speed is **sampled** at regular clock-edge time instants, and an indicator binary signal X indicates whether the speed is within acceptable limits ($X=0$), or, that the speed has become too excessive ($X=1$), and in that case, a control signal, $Y = 1$, must be asserted to cause the car to slow down to the acceptable range. The control signal should remain at $Y = 0$ while the speed is within the acceptable range.

Thus, the design requirement is that when the speed is measured to be excessive ($X=1$) in three consecutive time instants, a control action must be taken to slow the car down, otherwise, no action is required.

[cf. Brown & Vranesic]

example input signal and output

clock edge: $t_0 \ t_1 \ t_2 \ t_3 \ t_4 \ t_5 \ t_6 \ t_7 \ t_8 \ t_9 \ t_{10} \ t_{11} \ t_{12} \ t_{13} \ t_{14} \ t_{15}$

input X: 0 1 0 1 1 1 0 1 1 0 1 1 1 0 0 0 1 1 0 0

output Y: 0 0 0 0 0 0 1 0 0 0 0 0 1 1 1 0

three consecutive 1s at t_3, t_4, t_5

will cause an output Y=1
at the next clock edge t_6


three consecutive 1s at t_{10}, t_{11}, t_{12}

will cause an output Y=1
at the next clock edge t_{13}


continuing with another
set of three 1s at t_{11}, t_{12}, t_{13}
will cause another output Y=1
at the next clock edge t_{14}

example input signal, state transition, and output

clock edge:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}	t_{11}	t_{12}	t_{13}	t_{14}	t_{15}
input X:	0	1	0	1	1	1	0	1	1	0	1	1	1	1	0	0
state:	S_0	S_0	S_1	S_0	S_1	S_2	S_3	S_0	S_1	S_2	S_0	S_1	S_2	S_3	S_3	S_0
output Y:	0	0	0	0	0	0	1	0	0	0	0	0	0	1	1	0

 

 based on the current X, state transitions take place at the next active clock



state table

Moore FSM

	present state	next state	output Y
	X=0	X=1	
S ₀	S ₀	S ₁	0
S ₁	S ₀	S ₂	0
S ₂	S ₀	S ₃	0
S ₃	S ₀	S ₃	1

Moore FSM – state table

compact form


present state	next state		output Y
	X=0	X=1	
S ₀	S ₀	S ₁	0
S ₁	S ₀	S ₂	0
S ₂	S ₀	S ₃	0
S ₃	S ₀	S ₃	1

conventional form

X	present state	next state	Y
0	S ₀	S ₀	0
0	S ₁	S ₀	0
0	S ₂	S ₀	0
0	S ₃	S ₀	1
1	S ₀	S ₁	0
1	S ₁	S ₂	0
1	S ₂	S ₃	0
1	S ₃	S ₃	1

State assignment. With $N=4$ states, we need, $n = \text{ceiling}(\log_2 N) = 2$, state variables, say, A,B, and two D flip-flops, with inputs, say, D_A, D_B .

 The overall system will be as shown below.



State encoding. With two state variables, say, A,B, we have two options for state encoding, i.e., associating A,B with the four states, S_0, S_1, S_2, S_3 ,

- (1) plain binary, or,
- (2) Gray coding

First, consider **plain binary**, and re-write the state table in conventional form.


Moore FSM – state table

X	present state			next state			Y
		A	B		A	B	
0	S_0	0	0	S_0	0	0	0
0	S_1	0	1	S_0	0	0	0
0	S_2	1	0	S_0	0	0	0
0	S_3	1	1	S_0	0	0	1
1	S_0	0	0	S_1	0	1	0
1	S_1	0	1	S_2	1	0	0
1	S_2	1	0	S_3	1	1	0
1	S_3	1	1	S_3	1	1	1



binary encoding	
A	B
$S_0 \equiv$	0 0
$S_1 \equiv$	0 1
$S_2 \equiv$	1 0
$S_3 \equiv$	1 1

Moore FSM – binary encoding

X	present		next		Y
	A	B	A	B	
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	0	0	0
0	1	1	0	0	1
1	0	0	0	1	0
1	0	1	1	0	0
1	1	0	1	1	0
1	1	1	1	1	1

 

$$Y = A B \quad (\text{Moore output})$$

  


Moore FSM realization binary encoding

$$D_A = A^{\text{next}} = X(A + B)$$

$$D_B = B^{\text{next}} = X(A + B')$$

$$Y = AB \quad (\text{Moore output})$$

 


Simulink implementation and timing diagram

$$D_A = A^{\text{next}} = X(A + B)$$

$$D_B = B^{\text{next}} = X(A + B')$$

$$Y = AB \quad (\text{Moore output})$$

 


next-states & output sub-function


$$D_A = A^{\text{next}} = X(A + B)$$

$$D_B = B^{\text{next}} = X(A + B')$$


$$Y = AB \quad (\text{Moore output})$$

 


scope & data export sub-function

 


signal builder – input X

 

 

timing diagram

 

timing diagram

```
% MATLAB code for generating the timing diagram
% with data imported from the Simulink structure S

t = S.time;          % time
P = S.data(:,1);    % clock pulse
A = S.data(:,2);
B = S.data(:,3);
X = S.data(:,4);
Y = S.data(:,5);

figure;
subplot(5,1,1); stairs(t,P, 'g-','linewidth',2);
subplot(5,1,2); stairs(t,A, 'm-','linewidth',2);
subplot(5,1,3); stairs(t,B, 'm-','linewidth',2);
subplot(5,1,4); stairs(t,X, 'b-','linewidth',2);
subplot(5,1,5); stairs(t,Y, 'r-','linewidth',2);
xlabel('{\itt}, clock periods')
```

State encoding. Next, consider Gray encoding, and re-write the state table in conventional form.

Moore FSM – state table


X	present			next			Y
	state	A	B	state	A	B	
0	S ₀	0	0	S ₀	0	0	0
0	S ₁	0	1	S ₀	0	0	0
0	S ₂	1	1	S ₀	0	0	0
0	S ₃	1	0	S ₀	0	0	1
1	S ₀	0	0	S ₁	0	1	0
1	S ₁	0	1	S ₂	1	1	0
1	S ₂	1	1	S ₃	1	0	0
1	S ₃	1	0	S ₃	1	0	1

Gray encoding



$$\begin{array}{c}
 \text{A} \quad \text{B} \\
 \hline
 S_0 \equiv 0 \quad 0 \\
 S_1 \equiv 0 \quad 1 \\
 S_2 \equiv 1 \quad 1 \\
 S_3 \equiv 1 \quad 0
 \end{array}$$

Moore FSM – Gray encoding

X	present		next		Y
	A	B	A	B	
0	0	0	0	0	0
0	0	1	0	0	0
0	1	1	0	0	0
0	1	0	0	0	1
1	0	0	0	1	0
1	0	1	1	1	0
1	1	1	1	0	0
1	1	0	1	0	1

 

$$Y = AB' \quad (\text{Moore output})$$

  


Example 4

Moore FSM realization Gray encoding

$$D_A = A^{\text{next}} = X(A + B)$$

$$D_B = B^{\text{next}} = X A'$$

$$Y = A B' \quad (\text{Moore output})$$

 


Simulink implementation and timing diagram


$$D_A = A^{\text{next}} = X(A + B)$$

$$D_B = B^{\text{next}} = X A'$$

$$Y = A B' \quad (\text{Moore output})$$

 


next-states & output sub-function

 

$$D_A = A^{\text{next}} = X(A + B)$$

$$D_B = B^{\text{next}} = X A'$$


$$Y = A B' \quad (\text{Moore output})$$

 

scope
output


Example 4

Moore FSM – timing diagram

 


Moore FSM – timing diagram

binary encoding

 

Gray encoding

 

$$D_A = A^{\text{next}} = X(A + B)$$

$$D_B = B^{\text{next}} = X(A + B')$$

$$Y = AB \quad (\text{Moore output})$$

$$D_A = A^{\text{next}} = X (A + B)$$

$$D_B = B^{\text{next}} = X A'$$

$$Y = AB' \quad (\text{Moore output})$$

Example 5 – Sequence (111) recognizer – Mealy version. It is desired to design a Mealy FSM for the previous example. In the previous Moore version, the output was, $Y=1$, in the clock cycle that follows the observation of a third consecutive $X=1$.

In the present Mealy version, we require that $Y=1$ in the **same clock cycle** when the third occurrence of $X=1$ is observed.

This requirement makes Y dependent on both the input and the present state, hence, a Mealy machine.

(When a third $X=1$ is observed, the output Y is not instantaneously set equal to $Y=1$, but it requires a small delay, which we will ignore in the present discussion.)

example input signal and output

clock edge: $t_0 \ t_1 \ t_2 \ t_3 \ t_4 \ t_5 \ t_6 \ t_7 \ t_8 \ t_9 \ t_{10} \ t_{11} \ t_{12} \ t_{13} \ t_{14} \ t_{15}$

input X: 0 1 0 1 1 1 0 1 1 0 1 1 1 0 0 0 1 1 0 0

output Y: 0 0 0 0 0 1 0 0 0 0 0 1 1 0 0


three consecutive 1s at t_3, t_4, t_5
will cause an output Y=1
at the present clock edge t_5

three consecutive 1s at t_{10}, t_{11}, t_{12}
will cause an output Y=1
at the present clock edge t_{12}

continuing with another
set of three 1s at t_{11}, t_{12}, t_{13}
will cause another output Y=1
at the last clock edge t_{13}


example input signal, state transition, and output

clock edge:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}	t_{11}	t_{12}	t_{13}	t_{14}	t_{15}
input X:	0	1	0	1	1	1	0	1	1	0	1	1	1	1	0	0
state:	S_0	S_0	S_1	S_0	S_1	S_2	S_2	S_0	S_1	S_2	S_0	S_1	S_2	S_2	S_0	
output Y:	0	0	0	0	0	0	1	0	0	0	0	0	0	1	1	0

 

state transitions take place at the next active clock, but X, Y are at the present cycle

state diagram

 

state table

Mealy FSM

present state	next state		output Y	
	X=0	X=1	X=0	X=1
S_0	S_0	S_1	0	0
S_1	S_0	S_2	0	0
S_2	S_0	S_2	0	1

Mealy FSM – state table

compact form

present state	next state		output Y	
	X=0	X=1	X=0	X=1
S ₀	S ₀	S ₁	0	0
S ₁	S ₀	S ₂	0	0
S ₂	S ₀	S ₂	0	1

conventional form


X	present state	next state	Y
0	S ₀	S ₀	0
0	S ₁	S ₀	0
0	S ₂	S ₀	0
1	S ₀	S ₁	0
1	S ₁	S ₂	0
1	S ₂	S ₂	1

State assignment. With $N=3$ states, we need,

$$n = \text{ceiling}(\log_2 N) = \text{ceiling}(\log_2 3) = \text{ceiling}(1.5850) = 2,$$

state variables, say, A,B, and two D flip-flops, with inputs, say, D_A, D_B .

 The overall system will be as shown below.



State encoding. With two state variables, say, A,B, we have two options for state encoding, associating A,B with the three states, S_0, S_1, S_2 ,

- (1) plain binary, or,
- (2) Gray coding

We will use **Gray coding** with don't care entries for the unused pair, and re-write the state table in conventional form.

Mealy FSM - state table

X	present state		next state		Y
	A	B	A	B	
0	S_0	0 0	S_0	0 0	0
0	S_1	0 1	S_0	0 0	0
0	S_2	1 1	S_0	0 0	0
0	x	1 0	x	x x	x
1	S_0	0 0	S_1	0 1	0
1	S_1	0 1	S_2	1 1	0
1	S_2	1 1	S_2	1 1	1
1	x	1 0	x	x x	x

Gray encoding

A	B
0	0
0	1
1	1

don't cares




Mealy FSM – state table

X	present		next		Y
	A	B	A	B	
0	0	0	0	0	0
0	0	1	0	0	0
0	1	1	0	0	0
0	1	0	x	x	x
1	0	0	0	1	0
1	0	1	1	1	0
1	1	1	1	1	1
1	1	0	x	x	x

AB
X \ /

	00	01	11	10
0				x
1		1	1	x

$$D_A = A^{\text{next}} = X B$$

AB
X \ /

	00	01	11	10
0				x
1		1	x	

$$Y = X A \quad (\text{Mealy output})$$

AB
X \ /

	00	01	11	10
0				x
1	1	1	1	x

$$D_B = B^{\text{next}} = X$$


Mealy FSM – full state table

A B	X	next		Y
		A	B	
0 0	0	0	0	0
0 0	1	0	1	0
0 1	0	0	0	0
0 1	1	1	1	0
1 0	0	x0	x0	x0
1 0	1	x0	x1	x1
1 1	0	0	0	0
1 1	1	1	1	1

1,0 are unused states since they do not appear as next states, thus, they can be removed, or treated as don't cares

Gray encoding

A	B
S ₀	0 0
S ₁	0 1
S ₂	1 1

 

$$D_A = A^{\text{next}} = XB$$

$$D_B = B^{\text{next}} = X$$

$$Y = XA \quad (\text{Mealy output})$$

Mealy FSM – full state table

		next			
A	B	X	A	B	Y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	1	0
1	0	0	x0	x0	x0
1	0	1	x0	x1	x1
1	1	0	0	0	0
1	1	1	1	1	1



[a,b,x] = a2d(0:7, 3);

da = x & b;

db = x;

y = x & a;

[a,b,x,da,db,y]

%	a	b	x	da	db	y
%	0	0	0	0	0	0
%	0	0	1	0	1	0
%	0	1	0	0	0	0
%	0	1	1	1	1	0
%	1	0	0	0	0	0
%	1	0	1	0	1	1
%	1	1	0	0	0	0
%	1	1	1	1	1	1

1,0 are unused states since they do not appear as next states, thus, they can be removed, or treated as don't care entries

$$D_A = A^{\text{next}} = XB$$

$$D_B = B^{\text{next}} = X$$


$$Y = XA \quad (\text{Mealy output})$$

Mealy FSM realization Gray encoding

$$D_A = A^{\text{next}} = XB$$

$$D_B = B^{\text{next}} = X$$

$$Y = XA \quad (\text{Mealy output})$$

 


Simulink implementation and timing diagram


$$D_A = A^{\text{next}} = XB$$

$$D_B = B^{\text{next}} = X$$

$$Y = XA \quad (\text{Mealy output})$$

 

next-states & output sub-function

 


why is this necessary?

$$D_A = A^{\text{next}} = XB$$

$$D_B = B^{\text{next}} = X$$


$$Y = XA \quad (\text{Mealy output})$$

scope
output

 


Example 5

Mealy FSM – timing diagram

 


Mealy vs. Moore

Mealy - Gray encoding

 

Moore - Gray encoding

 

$$D_A = A^{\text{next}} = XB$$

$$D_B = B^{\text{next}} = X$$

$Y = XA$ (Mealy output)

$$D_A = A^{\text{next}} = X(A + B)$$

$$D_B = B^{\text{next}} = X A'$$

$Y = A B'$ (Moore output)

Example 6 – Another sequence recognizer – Mealy version. It is desired to design a Mealy FSM circuit to detect the particular sequence of consecutive bits, **1101**, in an incoming input stream X of zeros and ones, measured at the positive edges of the clock signal.

At each time instant, upon detecting the pattern 110 in the **previous** three inputs, and the **current** input is $X=1$, then, the FSM should produce an output, $Y = 1$, otherwise, it should produce, $Y = 0$.

We may assume also that there is a Reset input that initially resets all states to zero.


[cf. Mano, Kime, Martin]

The number of required states can be determined by imagining the following successive sequence of occurrences of input bits:

reset → 1 → 11 → 110

Thus, we may use 4 states, denoted symbolically as, S_0, S_1, S_2, S_3 .

state diagram

 


state table

Mealy FSM

present	next state		output Y	
	X=0	X=1	X=0	X=1
S_0	S_0	S_1	0	0
S_1	S_0	S_2	0	0
S_2	S_3	S_2	0	0
S_3	S_0	S_1	0	1

State assignment. With $N=4$ states, we need, $n = \text{ceiling}(\log_2 N) = 2$, state variables, say, A,B, and two D flip-flops, with inputs, say, D_A, D_B .

 The overall system will be as shown below.



State encoding. With two state variables, say, A,B, we have two options for state encoding, associating A,B with the 4 states, S_0, S_1, S_2, S_3 ,

- (1) plain binary, or,
- (2) Gray encoding

We will start with **Gray encoding** and rewrite the state table in terms of the state variables A, B.

Mealy FSM - state table

present states		next states			
		A ^{next}	B ^{next}	output Y	
A B		X=0	X=1	X=0	X=1
S_0	0 0	S_0	0 0	S_1	0 1
S_1	0 1	S_0	0 0	S_2	1 1
S_2	1 1	S_3	1 0	S_2	1 1
S_3	1 0	S_0	0 0	S_1	0 1

Gray encoding

A	B
$S_0 \equiv 0$	0
$S_1 \equiv 0$	1
$S_2 \equiv 1$	1
$S_3 \equiv 1$	0

Mealy FSM – state table

present states	next states A^{next} B^{next}				output Y
	X=0		X=1		
A B	X=0	X=1	X=0	X=1	
S ₀ 0 0	S ₀ 0 0	S ₁ 0 1	0	0	
S ₁ 0 1	S ₀ 0 0	S ₂ 1 1	0	0	
S ₂ 1 1	S ₃ 1 0	S ₂ 1 1	0	0	
S ₃ 1 0	S ₀ 0 0	S ₁ 0 1	0	1	

AB

X \ AB	00	01	11	10
0			1	
1		1	1	

$$D_A = A^{next} = X B + A B'$$

AB

X \ AB	00	01	11	10
0				
1	1	1	1	1

$$Y = X A B'$$


$$D_B = B^{next} = X$$

Block diagram realization


$$D_A = A^{\text{next}} = (X + A) B$$

$$D_B = B^{\text{next}} = X$$

$$Y = X A B'$$

 

Simulink implementation

 


$$D_A = A^{\text{next}} = (X + A) B$$

$$D_B = B^{\text{next}} = X$$

$$Y = X A B'$$


next-state & output sub-function

 


why is this necessary?

Example 6

signal builder – input X

 

 sequence recognizer – 1101 – Mealy version – Gray encoding



State encoding. With plain **binary** encoding, we obtain a more complex realization, requiring more gates.

Mealy FSM – state table – binary encoding

present states A B	next states A ^{next} B ^{next}		output Y	
	X=0	X=1	X=0	X=1
	S ₀ 0 0	S ₀ 0 0	S ₁ 0 1	0 0
S ₁ 0 1	S ₀ 0 0	S ₂ 1 0	0 0	
S ₂ 1 0	S ₃ 1 1	S ₂ 1 0	0 0	
S ₃ 1 1	S ₀ 0 0	S ₁ 0 1	0 1	



$$D_A = A^{\text{next}} = AB' + XA'B$$

$$D_B = B^{\text{next}} = X'AB' + XAB + XA'B'$$

$$Y = XAB$$

binary encoding


$$D_A = A^{\text{next}} = (X + A)B$$

$$D_B = B^{\text{next}} = X$$

$$Y = XAB'$$

Gray encoding

sequence recognizer – 1101 – Mealy version – binary encoding

 

Example 7 – Sequence recognizer – 1101 – Moore version. Here, we summarize without derivations the Moore version of the previous example.

The number of required states is five, corresponding to the sequence of occurrences of input bits:

reset → 1 → 11 → 110 → 1101

We may denote the states symbolically as, S_0, S_1, S_2, S_3, S_4 . Thus, we will need three **flip-flops**, A, B, C, and may use (partial) Gray encoding.


state table
Moore FSM

present state	next state		output Y
	X=0	X=1	
S_0	S_0	S_1	0
S_1	S_0	S_2	0
S_2	S_3	S_2	0
S_3	S_0	S_4	0
S_4	S_0	S_2	1

state encoding

	A	B	C
S_0	0	0	0
S_1	0	0	1
S_2	0	1	1
S_3	0	1	0
S_4	1	0	0

state diagram

 

present	next ABC		Y
ABC	X=0	X=1	
S ₀ 0 0 0	S ₀ 0 0 0 S ₁ 0 0 1		0
S ₁ 0 0 1	S ₀ 0 0 0 S ₂ 0 1 1		0
S ₂ 0 1 1	S ₃ 0 1 0 S ₂ 0 1 1		0
S ₃ 0 1 0	S ₀ 0 0 0 S ₄ 1 0 0		0
S ₄ 1 0 0	S ₀ 0 0 0 S ₂ 0 1 1		1
1 0 1	X X X	X X X	X
1 1 1	X X X	X X X	X
1 1 0	X X X	X X X	X

AB
CX

00	01	11	10
00		x	
01		x	
11		x	x
10		x	x

↓


$$D_A = A^{\text{next}} = B C' X$$

$$D_B = B^{\text{next}} = C X + A X + B C$$


$$D_C = C^{\text{next}} = C X + B' X$$

$$Y = A$$

next states & output equations

 

Simulink implementation

 


next-states & output sub-function

$$D_A = A^{\text{next}} = B C' X$$

$$D_B = B^{\text{next}} = C X + A X + B C$$


$$D_C = C^{\text{next}} = C X + B' X$$

$$Y = A$$

 


Example 7

scope
output


 


 Example 7

sequence recognizer – 1101 – Moore version



Mealy vs. Moore

  

$$D_A = A^{\text{next}} = (X + A) B$$

$$D_B = B^{\text{next}} = X$$

$$Y = X A B'$$

$$D_A = A^{\text{next}} = B C' X$$

$$D_B = B^{\text{next}} = C X + A X + B C$$

$$D_C = C^{\text{next}} = C X + B' X$$

$$Y = A$$

Gray encoding for both cases

Note on State Assignment

With n flip-flops, there are 2^n possible n -bit patterns, or states. If our FSM only needs k coded states, (with $k \leq 2^n$), then, the number of different ways to choose such k coded states from the 2^n available ones is given by the binomial coefficient:

$$\binom{2^n}{k} = \frac{(2^n)!}{k! (2^n - k)!}$$

Moreover, there are $k!$ ways (permutations) to assign the chosen k coded n -bit states to k symbolic-named states, therefore, the total number of ways to assign k symbolic states to k , n -bit patterns is,

$$\binom{2^n}{k} \cdot k! = \frac{(2^n)!}{k! (2^n - k)!} \cdot k! = \frac{(2^n)!}{(2^n - k)!}$$

For our example, we have $n = 3$ and $k = 5$, which gives, $2^n = 8$, and,

$$\binom{8}{5} \cdot 5! = 56 \cdot 120 = 6720$$

Example 8 – Yet, another sequence recognizer – Mealy version. It is desired to design a Mealy FSM circuit to detect the particular sequence of consecutive bits, 0001, in an incoming input stream X of zeros and ones, measured at the positive edges of the clock signal.

At each time instant, upon detecting the pattern 000 in the previous three inputs, and the current input is $X=1$, then, the FSM should produce an output, $Y = 1$, otherwise, it should produce, $Y = 0$.

Based on the above description, determine: (a) the state diagram, (b) state table, (c) state assignment with both Gray and binary encodings, (d) next-state and output equations, (e) build a realization using D flip-flops, and (f) simulate the operation of the system by sending in the following test sequence of binary inputs and verifying the expected outputs:


$$X = [0 \ 1 \ 1 \ 0 \ 0 \ 0 \ 1 \ 0 \ 0 \ 0 \ 0 \ 1 \ 1 \ 1 \ 0 \ 0]$$

$$Y = [0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 1 \ 0 \ 0 \ 0 \ 0 \ 1 \ 0 \ 0 \ 0 \ 0]$$

only incomplete answers are given below.

recognized sequence 0001

state diagram

 

state table


Mealy FSM

present	next state		output Y	
	X=0	X=1	X=0	X=1
S_0	S_1	S_0	0	0
S_1	S_2	S_0	0	0
S_2	S_3	S_0	0	0
S_3	S_3	S_0	0	1

 Example 8

State assignment. With $N=4$ states, we need, $n = \text{ceiling}(\log_2 N) = 2$, state variables, say, A,B, and two D flip-flops, with inputs, say, D_A, D_B .

The overall system will be as shown below.



State encoding. Using K-maps, show the following next-state and output equations for the cases of plain binary and Gray encodings.

$$D_A = A^{\text{next}} = X' (A + B)$$

$$D_B = B^{\text{next}} = X' (A + B')$$

$$Y = X A B$$

binary encoding

binary encoding

	A	B
S_0	0	0
S_1	0	1
S_2	1	0
S_3	1	1

$$D_A = A^{\text{next}} = X' (A + B)$$

$$D_B = B^{\text{next}} = X' A'$$


$$Y = X A B'$$

Gray encoding


Gray encoding

	A	B
S_0	0	0
S_1	0	1
S_2	1	1
S_3	1	0

 sequence recognizer – 0001 – Mealy version – binary encoding



 sequence recognizer – 0001 – Mealy version – Gray encoding



Example 9 – State reduction. It is often possible to reduce the number of states by identifying redundant states. Consider the following state table of a Mealy FSM, with one input X and one output Y [cf. Kana],

present	next state		output Y	
	X=0	X=1	X=0	X=1
S ₀	S ₂	S ₃	1	0
S ₁	S ₄	S ₂	0	0
S ₂	S ₂	S ₁	1	1
S ₃	S ₂	S ₅	0	1
S ₄	S ₂	S ₃	1	0
S ₅	S ₀	S ₂	0	0

S₀ and S₄ are equivalent states,
can keep S₀, and eliminate S₄,
replacing references to S₄ by S₀

two states are equivalent if they produce the same outputs for the same inputs

note also that if a state **does not appear as a next state**, then it can be eliminated from the state table and state diagram


present	next state		output Y	
	X=0	X=1	X=0	X=1
S ₀	S ₂	S ₃	1	0
S ₁	S ₀	S ₂	0	0
S ₂	S ₂	S ₁	1	1
S ₃	S ₂	S ₅	0	1
S ₅	S ₀	S ₂	0	0

kept S₀, eliminated S₄,
replaced S₄ by S₀
now S₁ and S₅ are equivalent,
so, keep S₁, and eliminate S₅,
replace references to S₅ by S₁


present	next state		output Y	
	X=0	X=1	X=0	X=1
S ₀	S ₂	S ₃	1	0
S ₁	S ₀	S ₂	0	0
S ₂	S ₂	S ₁	1	1
S ₃	S ₂	S ₁	0	1

simplified state table,
next, assign flip-flop state variables,
A,B, and derive the next-state and
output equations


present states	next states A^{next}, B^{next}				output Y	
A B	X=0		X=1		X=0 X=1	
	S ₀ 0 0	S ₂ 1 0	S ₃ 1 1	S ₀ 0 0	S ₂ 1 0	1 0
S ₁ 0 1	S ₀ 0 0	S ₂ 1 0	S ₁ 0 1	S ₂ 1 0	S ₁ 0 1	0 0
S ₂ 1 0	S ₂ 1 0	S ₁ 0 1	S ₂ 1 0	S ₁ 0 1	S ₂ 1 0	1 1
S ₃ 1 1	S ₂ 1 0	S ₁ 0 1	S ₂ 1 0	S ₁ 0 1	S ₂ 1 0	0 1

 


$$A^{next} = A' B' + X A' + X' A$$

 

$$B^{next} = X B' + X A$$

 

$$Y = A B' + X A + X' B'$$

 


$$D_A = A^{\text{next}} = A' B' + X A' + X' A$$

$$D_B = B^{\text{next}} = X B' + X A$$

$$Y = A B' + X A + X' B'$$

 Example 10 – Electronic keypad lock [cf. Harris & Harris].

Your DLD classmates give you a two-digit keypad lock as a birthday present, but when you open the box, you discover that instead of user instructions, they have included the following schematic.



You recognize this as a **Moore FSM**, and you will attempt to analyze it and eventually arrive at a state diagram, which will help you determine the unlocking combination.

The keypad accepts as input X the decimal digits, 0,1,2,3, and converts them to binary through an A/D converter, that is, each decimal $X = 0,1,2,3$ is represented by the bits, $X_1 X_0 = 00, 01, 10, 11$, so that there are two binary inputs to the FSM. There is also an output, $Y=A$, but you don't know its purpose yet, and you suspect it might be the "unlock" signal.

From the block diagram, you determine the next-state and flip-flop excitation equations and output equations:

$$D_A = A^{\text{next}} = BX_1' X_0$$

$$D_B = B^{\text{next}} = A' B' X_1 X_0$$

$$Y = A$$

Using these equations, you generate a possible state table that includes all possible evaluations of the flip-flop variables A, B for all inputs X_1, X_0 , including also the above next states and output.

A	B	X ₁	X ₀	A ^{next}	B ^{next}	Y
0	0	0	0	0	0	0
0	0	0	1	0	0	0
0	0	1	0	0	0	0
0	0	1	1	0	1	0
0	1	0	0	0	0	0
0	1	0	1	1	0	0
0	1	1	0	0	0	0
0	1	1	1	0	0	0
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	0	0	1
1	0	1	1	0	0	1
1	1	0	0	0	0	1
1	1	0	1	1	0	1
1	1	1	0	0	0	1
1	1	1	1	0	0	1

% MATLAB code

```
[A,B,X1,X0] = a2d(0:15,4);

Anext = B & (~X1) & X0;
Bnext = (~A) & (~B) & X1 & X0;
Y = A;

[A,B,X1,X0, Anext,Bnext,Y]
```

Next, carry out state reduction by removing unused states, noticing that the state, **AB = 11**, does not appear as a next state, so it can be removed,

also noticing that the state, **AB=10**, always results in the same next-state, **00**, and the same, output **Y=1**, regardless of the input, so these rows can be combined replacing the inputs by “don’t cares”.

$$D_A = A^{\text{next}} = BX_1' X_0$$

$$D_B = B^{\text{next}} = A' B' X_1 X_0$$

$$Y = A$$

reduced state table

A	B	X ₁	X ₀	A ^{next}	B ^{next}	Y
0	0	0	0	0	0	0
0	0	0	1	0	0	0
0	0	1	0	0	0	0
0	0	1	1	0	1	0
0	1	0	0	0	0	0
0	1	0	1	1	0	0
0	1	1	0	0	0	0
0	1	1	1	0	0	0
1	0	x	x	0	0	1

Next, carry out state assignment,
replacing the state variables A,B using
symbolic names, say, S₀, S₁, S₂,

	A	B
S ₀	0	0
S ₁	0	1
S ₂	1	0

and re-write the reduced state table using
the symbolic names, and also replace the
binary inputs X₁,X₀ by their decimal
values X

$$D_A = A^{\text{next}} = BX_1' X_0$$

$$D_B = B^{\text{next}} = A' B' X_1 X_0$$

$$Y = A$$

	A	B
S ₀	0	0
S ₁	0	1
S ₂	1	0

reduced state table


A	B	X ₁	X ₀	A ^{next}	B ^{next}	Y
0	0	0	0	0	0	0
0	0	0	1	0	0	0
0	0	1	0	0	0	0
0	0	1	1	0	1	0
0	1	0	0	0	0	0
0	1	0	1	1	0	0
0	1	1	0	0	0	0
0	1	1	1	0	0	0
1	0	x	x	0	0	1

symbolic state table

state	X	next	Y
S ₀	0	S ₀	0
S ₀	1	S ₀	0
S ₀	2	S ₀	0
S ₀	3	S ₁	0
S ₁	0	S ₀	0
S ₁	1	S ₂	0
S ₁	2	S ₀	0
S ₁	3	S ₀	0
S ₂	x	S ₀	1



 
next, convert the state table into an equivalent **state diagram**



unlock combination is 31,
 moving you to state S_2 , and issuing the “unlock” signal $Y=1$,
 and the FSM, then, moves to the reset/lock state S_0

next, test the FSM operation with Simulink

Simulink implementation

 


key = 31
Moore version


X1 = [0 0 0 1 0 0 0 0 0 1 0 0 0 1 0 0]
X0 = [1 0 0 1 1 0 1 1 1 1 1 0 0 1 1 0]

X = [1 0 0 3 1 0 1 1 1 3 1 0 0 3 1 0]
Y = [0 0 0 0 0 1 0 0 0 0 0 1 0 0 0 1]





next-states & output sub-function

why is this necessary?



 


 

Example 10

    


Example 10

   


Example 10

 Example 11 – Electronic keypad lock. Having figured out the operation of your Moore FSM padlock, you now wish to derive a **Mealy** version. Since you know that the unlock combination is 31, you may start with a Mealy state diagram. Only two states are needed now because the system issues the unlock output, $Y=1$, as soon as it has recognized the second digit, $X=1$. The system unlocks, and then moves to the reset state.



state diagram

 

symbolic state table

present state	next state				output Y			
	X=0	X=1	X=2	X=3	X=0	X=1	X=2	X=3
S ₀	S ₀	S ₀	S ₀	S ₁	0	0	0	0
S ₁	S ₀	S ₀	S ₀	S ₁	0	1	0	0

State encoding. With two states, we need one state variables, say, A, and one D flip-flop, and represent the states as follows:

$$\begin{array}{c} \text{A} \\ \hline \text{S}_0 \equiv 0 \\ \text{S}_1 \equiv 1 \end{array}$$


and also, replace the decimal X with its binary 2-bit representation, X_1X_0

encoded state table


present state	next state A^{next}				output Y			
A	X=00	X=01	X=10	X=11	X=00	X=01	X=10	X=11
0	0	0	0	1	0	0	0	0
1	0	0	0	1	0	1	0	0

next-state & output equations

present state	next state A^{next}				output Y			
A	$X=00$	$X=01$	$X=10$	$X=11$	$X=00$	$X=01$	$X=10$	$X=11$
0	0	0	0	1	0	0	0	0
1	0	0	0	1	0	1	0	0

 

$$A^{\text{next}} = X_1 X_0$$

 


$$Y = A X_1' X_0$$


block diagram realization

$$A^{\text{next}} = X_1 \ X_0$$

$$Y = A \ X_1' \ X_0$$

 


Simulink implementation

 


next-state & output sub-function

$$A^{\text{next}} = X_1 \ X_0$$

$$Y = A \ X_1' \ X_0$$

 




 


scope
display

decimal X
input

unlock
output

 

   

Example 12 – Electronic keypad lock. Having enjoyed analyzing the 2-digit padlock, you now wish to build your own electronic keypad lock with a 3-digit combination and program the unlocking combination to be the course number of your favorite ECE course, that is, 231!


As before, the keypad accepts as input X only the decimal digits, 0,1,2,3, and converts them to binary through an A/D converter, that is, each decimal $X = 0,1,2,3$ is represented by the bits, $X_1X_0 = 00, 01, 10, 11$, so that there are two binary inputs to the FSM.

As the user enters a sequence of decimal numbers X into the keypad, the FSM should generate an “unlock” signal, $Y=1$, whenever the previous two decimal inputs were, $X=2,3$, and the current input is, $X=1$. Otherwise, the system should remain locked at, $Y=0$. Because the output Y depends on the input X , this will be a **Mealy FSM**.


Based on the above description, determine: (a) the state diagram, (b) state table, (c) next-state and output equations, (d) build a realization using D flip-flops, and (e) simulate the operation of the system by sending in the following test sequence of decimal inputs and verifying the expected outputs:

$$X = [\textcolor{red}{1} \textcolor{blue}{0} \textcolor{red}{2} \textcolor{blue}{3} \textcolor{red}{1} \textcolor{blue}{0} \textcolor{red}{1} \textcolor{blue}{1} \textcolor{red}{2} \textcolor{blue}{3} \textcolor{red}{1} \textcolor{blue}{2} \textcolor{red}{2} \textcolor{blue}{3} \textcolor{red}{1} \textcolor{blue}{0}]$$
 
$$Y = [\textcolor{blue}{0} \textcolor{red}{0} \textcolor{blue}{0} \textcolor{red}{0} \textcolor{blue}{1} \textcolor{red}{0} \textcolor{blue}{0} \textcolor{red}{0} \textcolor{blue}{0} \textcolor{red}{0} \textcolor{blue}{1} \textcolor{red}{0} \textcolor{blue}{0} \textcolor{red}{0} \textcolor{blue}{1} \textcolor{red}{0}]$$



 got 23, which unlocks, and then moves to reset state



state table

present state	next state				output Y			
	X=0	X=1	X=2	X=3	X=0	X=1	X=2	X=3
S ₀	S ₀	S ₀	S ₁	S ₀	0	0	0	0
S ₁	S ₀	S ₀	S ₁	S ₂	0	0	0	0
S ₂	S ₀	S ₀	S ₁	S ₀	0	1	0	0

State encoding. With three states, we need two state variables, say, A,B, and we will use plain binary encoding to represent the states:

$$\begin{array}{c}
 \begin{array}{cc} A & B \\ \hline \end{array} \\
 S_0 \equiv 0 \ 0 \\
 S_1 \equiv 0 \ 1 \\
 S_2 \equiv 1 \ 0
 \end{array}$$

encoded state table

present state A B	next states $A^{\text{next}}, B^{\text{next}}$				output Y			
	X=0	X=1	X=2	X=3	X=0	X=1	X=2	X=3
0 0	0 0	0 0	0 1	0 0	0	0	0	0
0 1	0 0	0 0	0 1	1 0	0	0	0	0
1 0	0 0	0 0	0 1	0 0	0	1	0	0

binary X


	A	B	x_1	x_0	A^{next}	B^{next}	Y
S_0	0	0	0	0	0	0	0
	0	0	0	1	0	0	0
	0	0	1	0	0	1	0
	0	0	1	1	0	0	0
S_1	0	1	0	0	0	0	0
	0	1	0	1	0	0	0
	0	1	1	0	0	1	0
	0	1	1	1	1	0	0
S_2	1	0	0	0	0	0	0
	1	0	0	1	0	0	1
	1	0	1	0	0	1	0
	1	0	1	1	0	0	0
	1	1	0	0	x	x	x
	1	1	0	1	x	x	x
	1	1	1	0	x	x	x
	1	1	1	1	x	x	x

conventional state table


← don't cares

Example 12

K-map simplifications

 


$$D_B = B^{\text{next}} = X_1 X_0'$$

 

$$D_A = A^{\text{next}} = B X_1 X_0$$

K-map simplifications

 

$$Y = A X_1' X_0$$

$$D_A = A^{\text{next}} = B X_1 X_0$$

$$D_B = B^{\text{next}} = X_1 X_0'$$

$$Y = A X_1' X_0$$

```
[A,B,x1,x0] = a2d(0:15,4);
```

```
Anext = B & x1 & x0;
```

```
Bnxt = x1 & ~x0;
```

```
Y = A & ~x1 & x0;
```


```
[A,B,x1,x0,Anext,Bnxt,Y]
```

block diagram realization


$$D_A = A^{\text{next}} = B X_1 X_0$$

$$D_B = B^{\text{next}} = X_1 X_0'$$


$$Y = A X_1' X_0$$

 


Simulink implementation

 

next states & output sub-function

 


scope & date export sub-function

 


input X = 1 0 2 3 1 0 1 1 2 3 1 2 2 3 1 0

scope
display



 


 Example 12

input X = 1 0 2 3 1 0 1 1 2 3 1 2 2 3 1 0



   input X = 1 0 2 3 1 0 1 1 2 3 1 2 2 3 1 0



```

t = S.time;
P = S.data(:,1);
X1 = S.data(:,2);
X0 = S.data(:,3);
Y = S.data(:,4);

set(0,'DefaultAxesFontSize',10);
figure;
subplot(4,1,1); stairs(t,P, 'g-'); yaxis(0,2); ylabel('clock');
subplot(4,1,2); stairs(t,X1,'b-'); yaxis(0,2); ylabel('X1');
subplot(4,1,3); stairs(t,X0,'b-'); yaxis(0,2); ylabel('X0');
subplot(4,1,4); stairs(t,Y, 'r-'); yaxis(0,2); ylabel('Y');
xlabel('{\itt}, clock periods')

X = d2a([X1,X0],+1);      % decimal version of [X1,X0]

set(0,'DefaultAxesFontSize',10);
figure;
subplot(3,1,1); stairs(t,P, 'g-'); yaxis(0,2); ylabel('clock');
subplot(3,1,2); stairs(t,X,'b-'); yaxis(0,4); ylabel('X');
subplot(3,1,3); stairs(t,Y,'r-'); yaxis(0,2); ylabel('Y');
xlabel('{\itt}, clock periods')

```

Example 13 – Vending machine. We consider the design of a Moore FSM for a simple vending machine that accepts nickels or dimes as inputs, deposited one at a time, and dispenses some candy that costs 15 cents, and also returns some change, if necessary [cf. Maxfield].

Five states will be needed:

S_{00} - 0-cent state, also the reset state (entered upon power-up)


S_{05} - 5-cent state

S_{10} - 10-cent state


S_{15} - 15-cent state

S_{20} - 20-cent state

 The state diagram is shown on the next page using the arrow convention explained on p. 59 that displays input expressions instead of values.



state diagram

 

note: the possible input combinations are N D', N' D, N' D'

Example 13

main part of state table – with don't care inputs at S₁₅ and S₂₀

present	A	B	C	N	D	next	A	B	C	Y	Z
S ₀₀	1	0	0	0	0	S ₀₀	1	0	0	0	0
S ₀₀	1	0	0	1	0	S ₀₅	1	0	1	0	0
S ₀₀	1	0	0	0	1	S ₁₀	0	0	0	0	0
S ₀₅	1	0	1	0	0	S ₀₅	1	0	1	0	0
S ₀₅	1	0	1	1	0	S ₁₀	0	0	0	0	0
S ₀₅	1	0	1	0	1	S ₁₅	0	0	1	0	0
S ₁₀	0	0	0	0	0	S ₁₀	0	0	0	0	0
S ₁₀	0	0	0	1	0	S ₁₅	0	0	1	0	0
S ₁₀	0	0	0	0	1	S ₂₀	0	1	1	0	0
S ₁₅	0	0	1	0	0	S ₀₀	1	0	0	1	0
S ₁₅	0	0	1	1	0	S ₀₀	1	0	0	1	0
S ₁₅	0	0	1	0	1	S ₀₀	1	0	0	1	0
S ₂₀	0	1	1	0	0	S ₀₀	1	0	0	1	1
S ₂₀	0	1	1	1	0	S ₀₀	1	0	0	1	1
S ₂₀	0	1	1	0	1	S ₀₀	1	0	0	1	1

state encoding

	A	B	C
--	---	---	---

S ₀₀	1	0	0
S ₀₅	1	0	1
S ₁₀	0	0	0
S ₁₅	0	0	1
S ₂₀	0	1	1

rest of state table with unsused or don't care states

A B C present			N	D	A B C next			Y	Z
1	0	0	1	1	0	0	1	0	0
1	0	1	1	1	0	0	0	0	0
0	0	0	1	1	0	1	1	0	0
0	0	1	1	1	1	0	0	1	0
0	1	1	1	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1
1	1	0	1	1	0	0	1	0	1
1	1	1	1	1	0	0	0	0	1
0	1	0	0	0	0	0	0	0	1
0	1	0	0	1	0	1	1	0	1
0	1	0	1	0	0	0	1	0	1
1	1	0	0	0	1	0	0	0	1
1	1	0	0	1	0	0	0	0	1
1	1	0	1	0	1	0	1	0	1
1	1	1	0	0	1	0	1	0	1
1	1	1	0	1	0	0	1	0	1
1	1	1	1	0	0	0	0	0	1

17 rows

some used states,
some unused states,
but, the inputs, N=1, D=1,
are not allowed

all are unused states

next-state & output equations are obtained from the state table
after taking advantage of all unused don't care entries.



next states & output equations

$$A^{next} = A' C + A N' D' + A C' D'$$

$$B^{next} = A' C' D$$

$$C^{next} = A' C' D + A C N' + C' N$$

$$Y = A' C$$

$$Z = B$$

MATLAB code
for producing the main part of the stable on p.171 →
and the rest of the state table on p.172

```

% MATLAB code used to generate the state table

% generate main part of state table
n = [16 18 17 20 22 21 0 2 1 4 6 5 12 14 13];

% generate rest of state table
% n = [19 23 3 7 15 11 27 31 8 9 10 24 25 26 28 29 30];

[A,B,C,N,D] = a2d(n,5); % generate states & inputs

Anext = (~A & C) | (A & ~N & ~D) | (A & ~C & ~D);

Bnext = ~A & ~C & D;


Cnext = (~A & ~C & D) | (A & C & ~N) | (~C & N);

Y = ~A & C;

Z = B;

[A,B,C,N,D,Anext,Bnext,Cnext,Y,Z] % print state table

```

 

Example 13

Example 14 – Elevator controller. [this is a simplified version of a DLD lab from earlier years.] Consider the design of a simple elevator controller for a three-story building. There are three states F_1 , F_2 , F_3 defined so that,

F_1 = elevator is at floor 1

F_2 = elevator is at floor 2

F_3 = elevator is at floor 3

The input to the controller is the (decimal) variable X , defined so that,

$X = 0$, no request (i.e., stay on the current floor)

$X = 1$, move to floor 1


$X = 2$, move to floor 2

$X = 3$, move to floor 3

There is also a reset input R , such that $R=1$ will cause the elevator to move to floor 1 from any floor, regardless of X . Otherwise, $R=0$ has no effect, and the input X will determine the action.

There is also an output Y taking the (decimal) values $Y=1, 2, 3$, that are generated when the elevator is moving to floors 1, 2, 3, respectively.

notation: X / Y

 

present state	next state					output Y			
	R=0	X=0	X=1	X=2	X=3	X=0	X=1	X=2	X=3
F ₁		F ₁	F ₁	F ₂	F ₃	1	1	2	3
F ₂		F ₂	F ₁	F ₂	F ₃	2	1	2	3
F ₃		F ₃	F ₁	F ₂	F ₃	3	1	2	3
	R=1	X=0	X=1	X=2	X=3	X=0	X=1	X=2	X=3
F ₁ , F ₂ , F ₃		F ₁	F ₁	F ₁	F ₁	1	1	1	1

state table

Example 14

input & output encoding

$$X = X_1 X_0 \quad Y = Y_1 Y_0$$

$$\begin{array}{ll} 0 = 0 0 & \\ 1 = 0 1 & 1 = 0 1 \\ 2 = 1 0 & 2 = 1 0 \\ 3 = 1 1 & 3 = 1 1 \end{array}$$

state encoding

F A B

	0 0	unused
F1	0 1	
F2	1 0	
F3	1 1	

three states
require two
D flip-flops
 D_A & D_B

binary ordering


K-maps for
 A_{next} , B_{next}

K-maps for
 Y_1 , Y_0
are similar


		AB	$X_1 X_0$	00	01	11	10
				xx	xx	xx	xx
F_1	01		F_1 01	F_1 01	F_3 11	F_2 10	
			F_3 11	F_1 01	F_3 11	F_2 10	
F_2	10		F_2 10	F_1 01	F_3 11	F_2 10	
			F_1 01	F_3 11	F_2 10		

don't'cares

K-maps

 

$$A^{\text{next}} = X_1 + X_0' A$$

 

$$Y_1 = A^{\text{next}}$$

$$Y_0 = B^{\text{next}}$$

$$Y = 2Y_1 + Y_0 \text{ (decimal)}$$

$$X = 2X_1 + X_0 \text{ (decimal)}$$

$$B^{\text{next}} = X_0 + X_1' (A + B')$$

needed to make the state $A, B = 0, 0$ redundant

adding the reset input R and the output Y (in decimal)


$$A^{\text{next}} = R' (X_1 + X_0' A)$$

$$B^{\text{next}} = R + X_0 + X_1' (A + B')$$

$$Y = 2A^{\text{next}} + B^{\text{next}} \text{ (decimal)}$$

← resets to state $F_1 = AB = 01$, if $R=1$,
and normal operation, if $R=0$

requires two D flip-flops

 

computed state table

$$A^{\text{next}} = R' (X_1 + X_0' A)$$

$$Y = 2A^{\text{next}} + B^{\text{next}}$$

$$B^{\text{next}} = R + X_0 + X_1'(A + B')$$

$$X = 2X_1 + X_0$$

decimal

R	X ₁	X ₀	A	B	D _A	D _B	X	Y
0	0	0	0	0	0	1	0	1
0	0	0	0	1	0	1	0	1
0	0	0	1	0	1	0	0	2
0	0	0	1	1	1	1	0	3
0	0	1	0	0	0	1	1	1
0	0	1	0	1	0	1	1	1
0	0	1	1	0	0	1	1	1
0	0	1	1	1	0	1	1	1
0	1	0	0	0	1	0	2	2
0	1	0	0	1	1	0	2	2
0	1	0	1	0	1	0	2	2
0	1	0	1	1	1	0	2	2
0	1	1	0	0	1	1	3	3
0	1	1	0	1	1	1	3	3
0	1	1	1	0	1	1	3	3
0	1	1	1	1	1	1	3	3
0	1	1	1	1	1	1	3	3

decimal

R	X ₁	X ₀	A	B	D _A	D _B	X	Y
1	0	0	0	0	0	1	0	1
1	0	0	0	1	0	1	0	1
1	0	0	1	0	0	1	0	1
1	0	0	1	1	0	1	0	1
1	0	1	0	0	0	1	1	1
1	0	1	0	1	0	1	1	1
1	0	1	1	0	0	1	1	1
1	0	1	1	1	0	1	1	1
1	1	0	0	0	0	1	2	1
1	1	0	0	1	0	1	2	1
1	1	0	1	0	0	1	2	1
1	1	0	1	1	0	1	2	1
1	1	1	0	0	0	1	3	1
1	1	1	0	1	0	1	3	1
1	1	1	1	0	0	1	3	1
1	1	1	1	1	1	0	3	1

state A,B=0,0 does not appear as a next state, so it can be removed

Example 14

computed state table

$$A^{\text{next}} = R' (X_1 + X_0' A)$$

$$Y = 2A^{\text{next}} + B^{\text{next}}$$

$$B^{\text{next}} = R + X_0 + X_1' (A + B')$$

$$X = 2X_1 + X_0$$

reduced state table

R	X ₁	X ₀	A	B	D _A	D _B	X	Y
0	0	0	0	1	0	1	0	1
0	0	0	1	0	1	0	0	2
0	0	0	1	1	1	1	0	3
0	0	1	0	1	0	1	1	1
0	0	1	1	0	0	1	1	1
0	0	1	1	1	0	1	1	1
0	1	0	0	1	1	0	2	2
0	1	0	1	0	1	0	2	2
0	1	0	1	1	1	0	2	2
0	1	1	0	1	1	1	3	3
0	1	1	1	0	1	1	3	3
0	1	1	1	1	1	1	3	3

R	X ₁	X ₀	A	B	D _A	D _B	X	Y
1	0	0	0	1	0	1	0	1
1	0	0	1	0	0	1	0	1
1	0	0	1	1	0	1	0	1
1	0	1	0	1	0	1	1	1
1	0	1	1	0	0	1	1	1
1	0	1	1	1	0	1	1	1
1	1	0	0	1	0	1	2	1
1	1	0	1	0	0	1	2	1
1	1	0	1	1	0	1	2	1
1	1	1	0	1	0	1	3	1
1	1	1	1	0	0	1	3	1
1	1	1	1	1	0	1	3	1

next, replace states by their symbolic names →

Example 14

symbolic state table

$$A^{\text{next}} = R' (X_1 + X_0' A)$$

$$Y = 2A^{\text{next}} + B^{\text{next}}$$

$$B^{\text{next}} = R + X_0 + X_1'(A + B')$$

$$X = 2X_1 + X_0$$

R	X ₁	X ₀	A	B	D _A	D _B	X	Y
0	0	0	F1		F1		0	1
0	0	0	F2		F2		0	2
0	0	0	F3		F3		0	3
0	0	1	F1		F1		1	1
0	0	1	F2		F1		1	1
0	0	1	F3		F1		1	1
0	1	0	F1		F2		2	2
0	1	0	F2		F2		2	2
0	1	0	F3		F2		2	2
0	1	1	F1		F3		3	3
0	1	1	F2		F3		3	3
0	1	1	F3		F3		3	3


R	X ₁	X ₀	A	B	D _A	D _B	X	Y
1	0	0	F1		F1		0	1
1	0	0	F2		F1		0	1
1	0	0	F3		F1		0	1
1	0	1	F1		F1		1	1
1	0	1	F2		F1		1	1
1	0	1	F3		F1		1	1
1	1	0	F1		F1		2	1
1	1	0	F2		F1		2	1
1	1	0	F3		F1		2	1
1	1	1	F1		F1		3	1
1	1	1	F2		F1		3	1
1	1	1	F3		F1		3	1

1	x	x	Fx	F1	x	1
---	---	---	----	----	---	---


equivalent to the table on p. 177

compact form

Simulink implementation

 

 
Simulink implementation input subfunction




Simulink implementation next-states subfunction

$$D_A = A^{\text{next}} = R' (X_1 + X_0'A)$$
 
$$D_B = B^{\text{next}} = R + X_0 + X_1'(A+B')$$



 Simulink implementation scope & data export subfunction



Simulink implementation


scope output


state encoding

F	A	B	
0	0	0	unused
F_1	0	1	
F_2	1	0	
F_3	1	1	


```
x = [ 0 2 3 1 2 0 3 3 2 ]
x1 = [ 0 1 1 0 1 0 1 1 1 ]
x0 = [ 0 0 1 1 0 0 1 1 0 ]
R = [ 1 0 0 0 0 0 1 0 0 ]
y = [ 1 2 3 1 2 2 1 3 2 ]
```

reset

 


 

Example 14

 

Example 14

 

Example 14